



VSM COLLEGE OF ENGINEERING AUTONOMOUS

Accredited by NAAC with 'A' Grade - 3.23/4.00 CGPA
(Approved by AICTE, New Delhi and Permanently affiliated to JNTUK, Kakinada)
Recognised under 2(f) and 12(B) of UGC, Certified by ISO 9001:2015 Sponsored by
The Ramchandrapuram Education Society (Estd. 1965)



Department of ELECTRICAL & ELECTRONICS ENGINEERING

ELECTRICAL CIRCUIT ANALYSIS-II

SUBJECT MATERIAL

YEAR : II SEMESTER : I

Regulation: VR23

Subject Code: VR2321202

Prepared by

Mrs. T. ASHA KRANTHI
Assistant Professor

EEE Department



β

η

ϕ

ζ

ϵ

\ae



Σ

$\acute{a} \acute{e} \acute{i} \acute{o} \acute{u}$





\ae

\acute{a}

\ddot{o}

$t\ddot{s}$

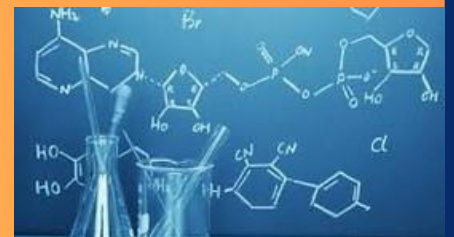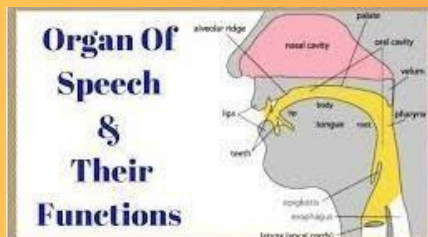

**ELECTRICAL CIRCUIT
ANALYSIS-II**

II B.TECH II SEM

FOR

EEE

(AUTONOMOUS)

(R23)

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING



V S M COLLEGE OF ENGINEERING

RAMCHANDRAPURAM

E.G. Dt. - 533255



JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY KAKINADA

KAKINADA – 533 003, Andhra Pradesh, India

**ELECTRICAL AND ELECTRONICS ENGINEERING
(R23-IInd YEAR COURSE STRUCTURE & SYLLABUS)**

II Year –I SEMESTER

L	T	P	C
3	0	0	3

ELECTRICAL CIRCUIT ANALYSIS-II

Pre-requisite: Analysis of DC and Single phase AC Circuits, Concepts of differentiation and integration.

Course Objectives:

- To understand three phase circuits
- To analyse transients in electrical systems
- To evaluate network parameters of given electrical network
- To apply Fourier analysis to electrical systems
- To understand graph theory for circuit analysis and to understand the behaviour of filters

Course Outcomes:

At the end of the course, student will be able to,

CO1: Analyse the balanced and unbalanced 3 phase circuits for power calculations.

CO2: Analyse the transient behaviour of electrical networks in different domains.

CO3: Estimate various Network parameters.

CO4: Apply the concept of Fourier series to electrical systems.

CO5: Analyse the filter circuit for electrical circuits.

UNIT - I

Analysis of three phase balanced circuits:

Phase sequence, star and delta connection of sources and loads, relation between line and phase quantities, analysis of balanced three phase circuits, measurement of active and reactive power.

Analysis of three phase unbalanced circuits:

Loop method, Star-Delta transformation technique, two-wattmeter method for measurement of three phase power.

UNIT – II

Laplace transforms – Definition and Laplace transforms of standard functions– Shifting theorem – Transforms of derivatives and integrals, Inverse Laplace transforms and applications.

Transient Analysis: Transient response of R-L, R-C and R-L-C circuits (Series and parallel combinations) for D.C. and sinusoidal excitations – Initial conditions - Solution using differential equation approach and Laplace transform approach.



JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY KAKINADA

KAKINADA – 533 003, Andhra Pradesh, India

ELECTRICAL AND ELECTRONICS ENGINEERING (R23-IInd YEAR COURSE STRUCTURE & SYLLABUS)

UNIT - III

Network Parameters: Impedance parameters, Admittance parameters, Hybrid parameters, Transmission (ABCD) parameters, conversion of Parameters from one form to other, Conditions for Reciprocity and Symmetry, Interconnection of Two Port networks in Series, Parallel and Cascaded configurations- problems.

UNIT - IV

Analysis of Electric Circuits with Periodic Excitation: Fourier series and evaluation of Fourier coefficients, Trigonometric and complex Fourier series for periodic waveforms, Application to Electrical Systems – Effective value and average value of non-sinusoidal periodic waveforms, power factor, effect of harmonics

UNIT - V

Filters: Classification of filters-Low pass, High pass, Band pass and Band Elimination filters, Constant-k filters -Low pass and High Pass, Design of Filters.

Textbooks:

1. Engineering Circuit Analysis, William Hayt and Jack E. Kemmerly, 8th Edition McGraw-Hill, 2013
2. Fundamentals of Electric Circuits, Charles K. Alexander, Mathew N. O. Sadiku, 3rd Edition, Tata McGraw-Hill, 2019

Reference Books:

1. Network Analysis, M. E. Van Valkenburg, 3rd Edition, PHI, 2019.
2. Network Theory, N. C. Jagan and C. Lakshminarayana, 1st Edition, B. S. Publications, 2012.
3. Circuits and Networks Analysis and Synthesis, A. Sudhakar, Shyam Mohan S. Palli, 5th Edition, Tata McGraw-Hill, 2017.
4. Engineering Network Analysis and Filter Design (Including Synthesis of One Port Networks)- Durgesh C. Kulshreshtha Gopal G. Bhise, Prem R. Chadha ,Umesh Publications 2012.
5. Circuit Theory: Analysis and Synthesis, A. Chakrabarti, Dhanpat Rai & Co., 2018, 7th Revised Edition.

Online Learning Resources:

1. <https://archive.nptel.ac.in/courses/117/106/117106108/>
2. <https://archive.nptel.ac.in/courses/108/105/108105159/>

UNIT-1

Balanced and unbalanced three phase circuits

Analysis of three phase balanced circuits:-

phase sequence, star and delta connection of source & loads, relation between line and phase voltage and currents, analysis of balanced three phase circuits, measurement of active and reactive power

Analysis of three phase unbalanced circuits

loop method, star-delta transformation technique, two-wattmeter method for measurement of three phase power.

UNIT-II

Transient response of first order (R-L, R-C) & second order (R-L-C) circuit using differential equations

Transient response of first order (R-L, R-C) & second order (R-L-C) using Laplace transforms

UNIT-III

Transient response of first order (R-L, R-C) & second order (R-L-C) circuits using diff eqns

Transient response of first order (R-L, R-C) & second order (R-L-C) circuit using Laplace transforms

UNIT-IV

Two port network parameters - Z, Y, ABCD & Hybrid parameters & their relations, cascaded networks

UNIT-V

Need of filters - classification - characteristic impedance - low pass filter, high pass filter, band pass filter, band stop or band elimination filter, m-derived filter, design of filters

UNIT - I


BALANCED AND UNBALANCED 3 ϕ CIRCUITS

phase sequence:-

The sequence in which the voltages in three phases reach their maximum values is called phase sequence

Generally the phase sequence are R, Y, B

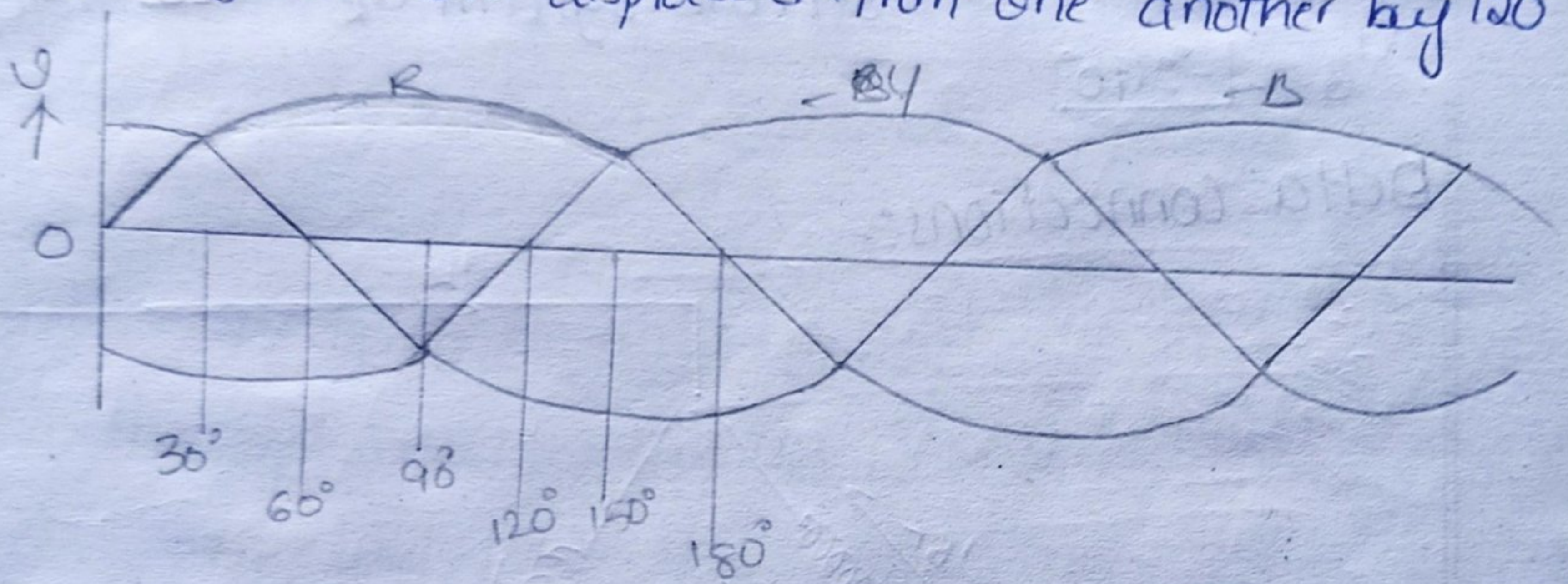
Generally the voltages are same magnitude & frequency but are displaced from one another by 120



The 3 phase system are either (Y) star or delta (Δ)

Connections

Star Connections:-

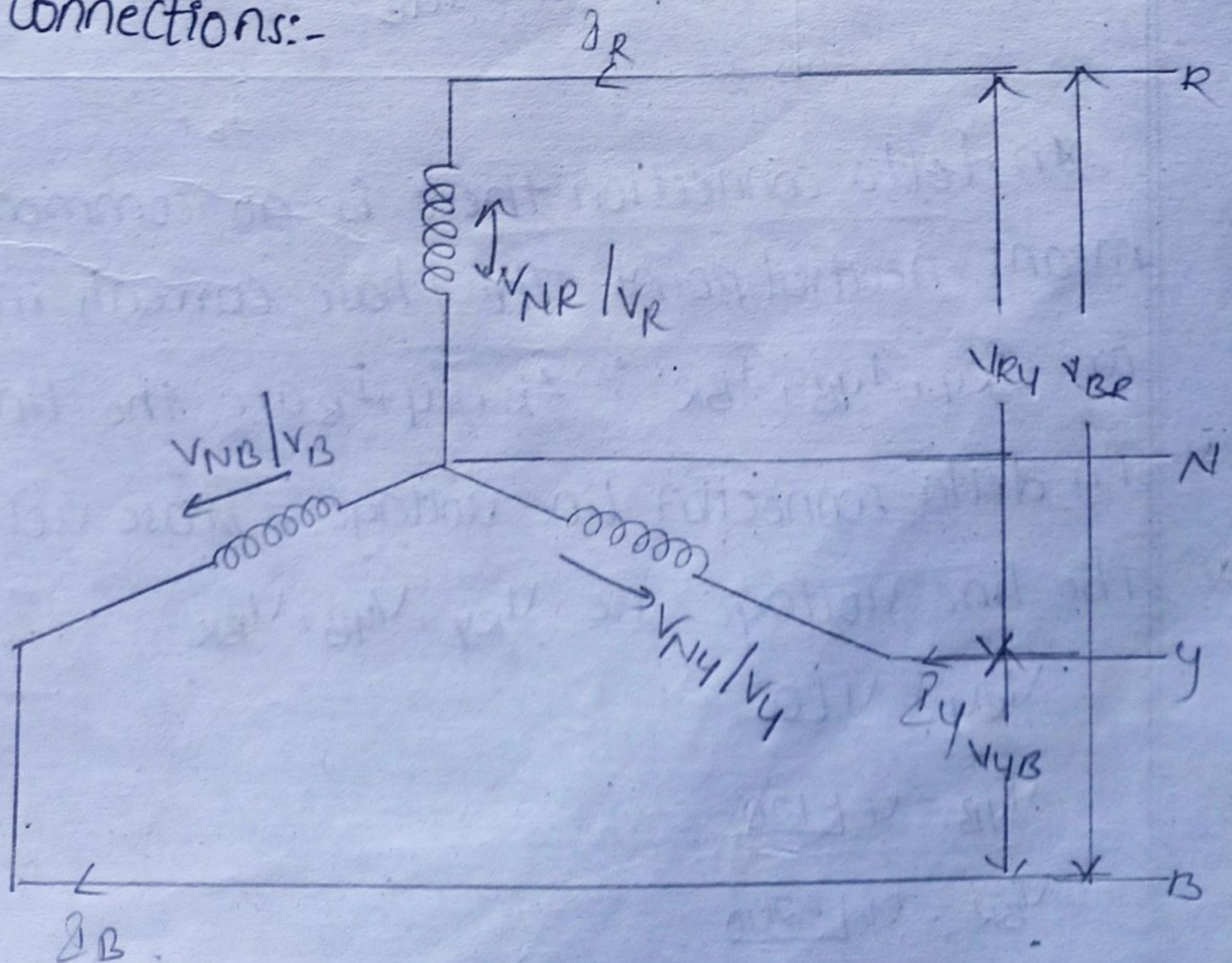


The star connection, the phases connected in star
 N be the neutral point.

V_{NR}, V_{Ny}, V_{NB} are represented by the phase voltages
 & simple denoted by V_R, V_Y, V_B

The voltage between lines i.e. V_{RY}, V_{YB}, V_{BR} are the
 voltage E

In a balanced 3-phase system $V_R = V \angle 0^\circ; V_Y = V \angle -120^\circ$
 $V_B = V \angle -240^\circ$

Delta connections:-

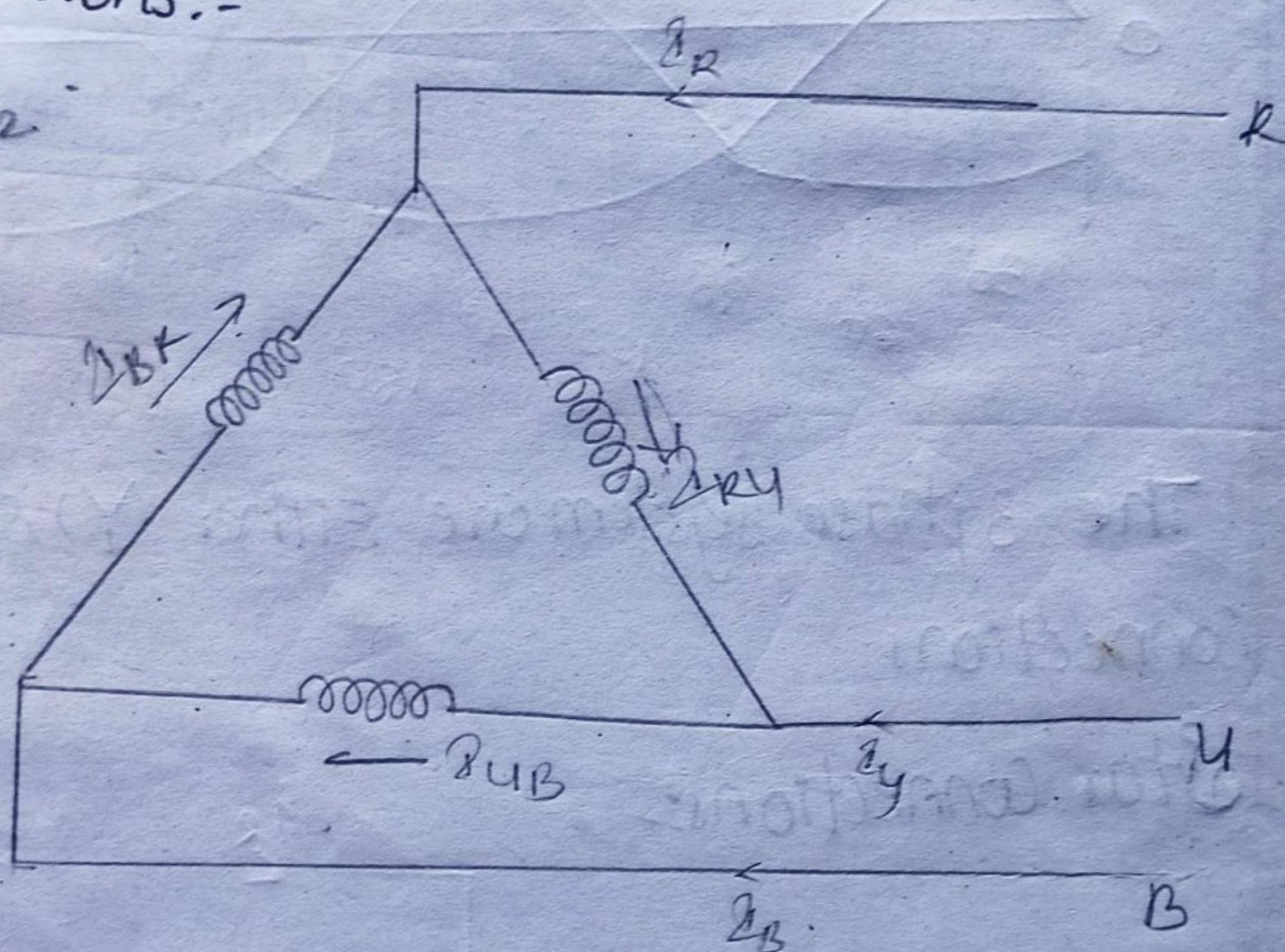

In delta connection there is no common point
 means neutral point. The phase currents in delta
 are I_{RY}, I_{YB}, I_{BR} ; I_R, I_Y, I_B are the line currents

* In delta connection line voltage = phase voltage


* The line voltages are V_{RY}, V_{YB}, V_{BR}

$$V_{RY} = V \angle 0^\circ$$

$$V_{YB} = V \angle -120^\circ$$

$$V_{BR} = V \angle -240^\circ$$

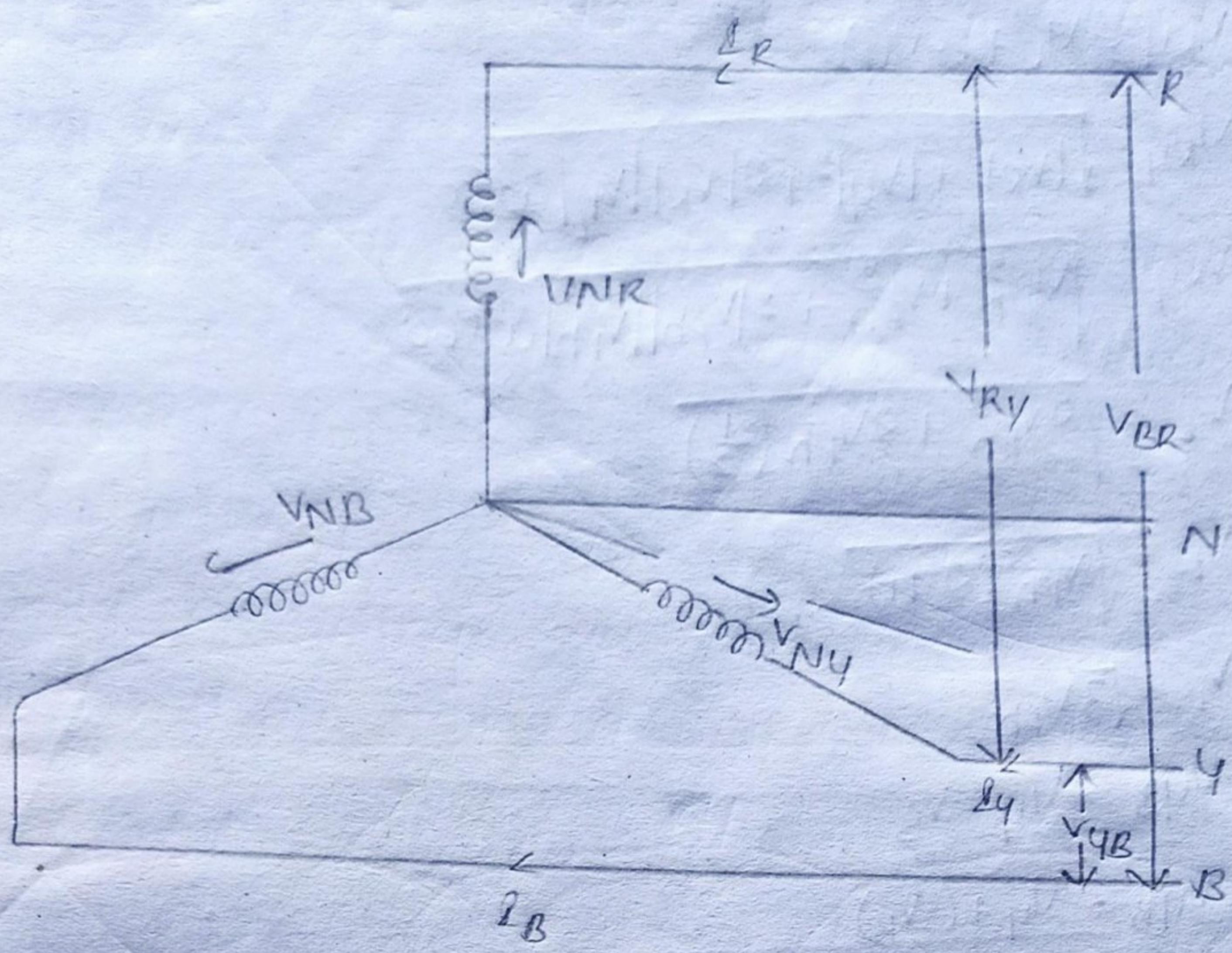
The relation between line & phase voltages



Let V_R, V_B, V_Y be the represents the phase voltages and the line voltages are V_{RY}, V_{YB}, V_{BR}

Let $|V_R| = |V_Y| = |V_B| = V_{ph}$

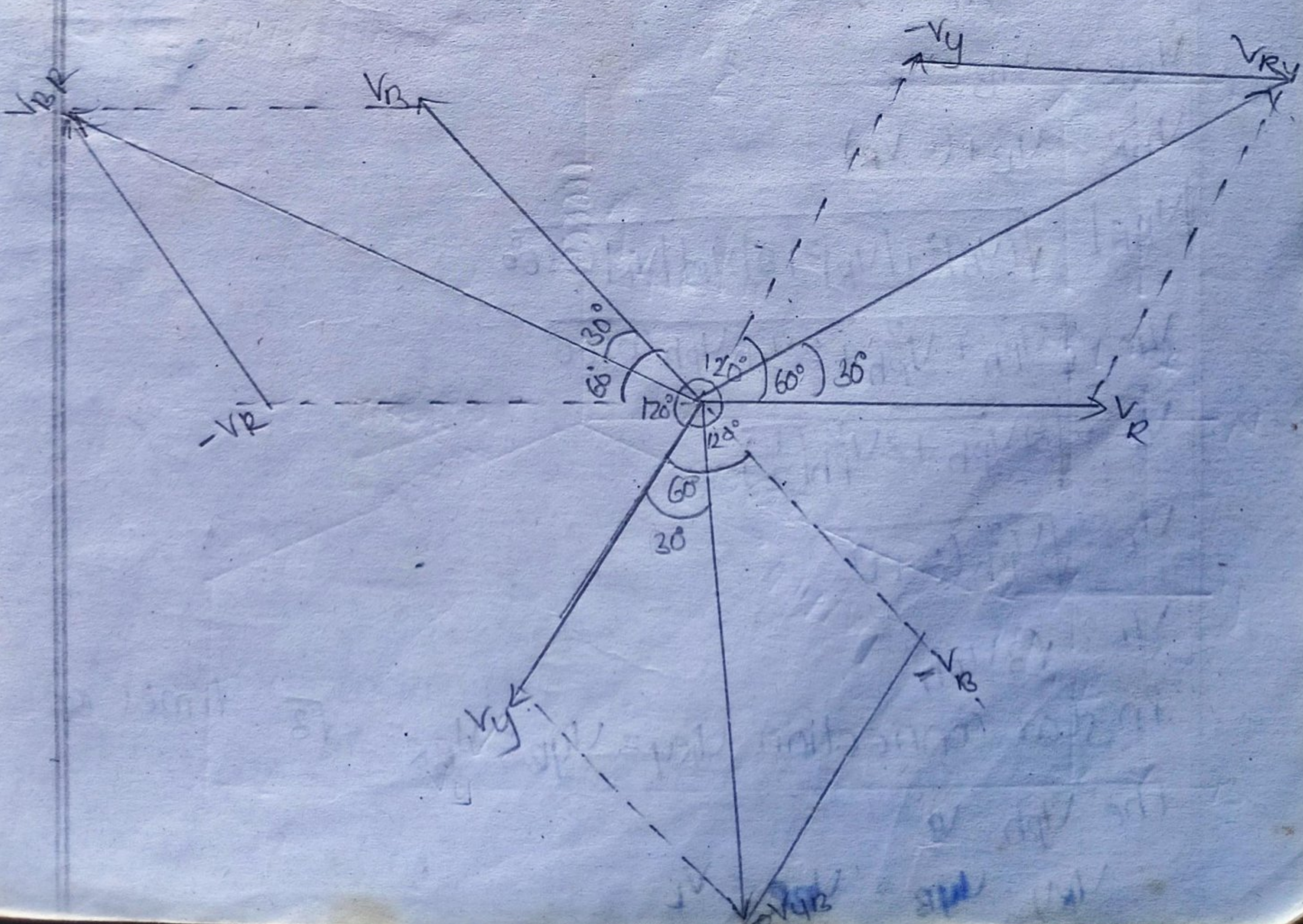The line voltage V_{RY} is the vector difference of the V_R & V_Y or the vector sum of V_R & V_Y (reversed)



$$V_{RY} = V_R - V_Y$$

$$V_{RY} = V_R + (-V_Y)$$

$$V_{RY} = \sqrt{|V_R|^2 + |V_Y|^2 + 2|V_R||V_Y|\cos 0}$$

$$V_{RY} = \sqrt{V_{ph}^2 + V_{ph}^2 + 2|V_{ph}||V_{ph}|\cos 60^\circ}$$

$$V_L = \sqrt{2V_{ph}^2 + 2V_{ph}^2\left(\frac{1}{2}\right)}$$

$$V_L = \sqrt{V_{ph}^2(2+1)}$$

$$V_L = \sqrt{3}V_{ph}$$

$$V_{YB} = V_Y - V_B$$

$$V_{YB} = V_Y + (-V_B)$$

$$|V_{YB}| = \sqrt{|V_Y|^2 + |V_B|^2 + 2|V_Y||V_B|\cos 0}$$

$$V_L = \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph}V_{ph}\cos 60^\circ}$$

$$V_L = \sqrt{2V_{ph}^2 + 2V_{ph}^2\left(\frac{1}{2}\right)}$$

$$V_L = \sqrt{V_{ph}^2(2+1)}$$

$$V_L = \sqrt{3}V_{ph}$$

$$V_{BR} = V_B - V_R$$

$$V_{BR} = V_B + (-V_R)$$

$$|V_{BR}| = \sqrt{|V_B|^2 + |V_R|^2 + 2|V_B||V_R|\cos 0}$$

$$V_L = \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph}V_{ph}\cos 60^\circ}$$

$$V_L = \sqrt{2V_{ph}^2 + 2V_{ph}^2\left(\frac{1}{2}\right)}$$

$$V_L = \sqrt{V_{ph}^2(2+1)}$$

$$V_L = \sqrt{3}V_{ph}$$

In star connection $V_{RY} = V_{YB} = V_{BR} = \sqrt{3}$ times of the V_{ph} &


$$V_{RY} = V_{YB} = V_{BR} = V_L$$

$$\therefore V_L = \sqrt{3} V_{ph}$$

- * In star connection each line is in series with its individual phase winding
- * Hence the line current in each line is same that current in the each phase winding
- * Let current in the line R be I_R ;
current in the line Y be I_Y , current in the line B be I_B
- * $I_R = I_Y = I_B = I_{ph}$
- * $\therefore I_L = I_{ph}$
- * \therefore The line current = phase current
- * The line voltages are 120° apart from each other & phase voltage also 120° apart from each other
- * In balance star connection

$$I_R + I_Y + I_B = 0$$

Delta connection:-

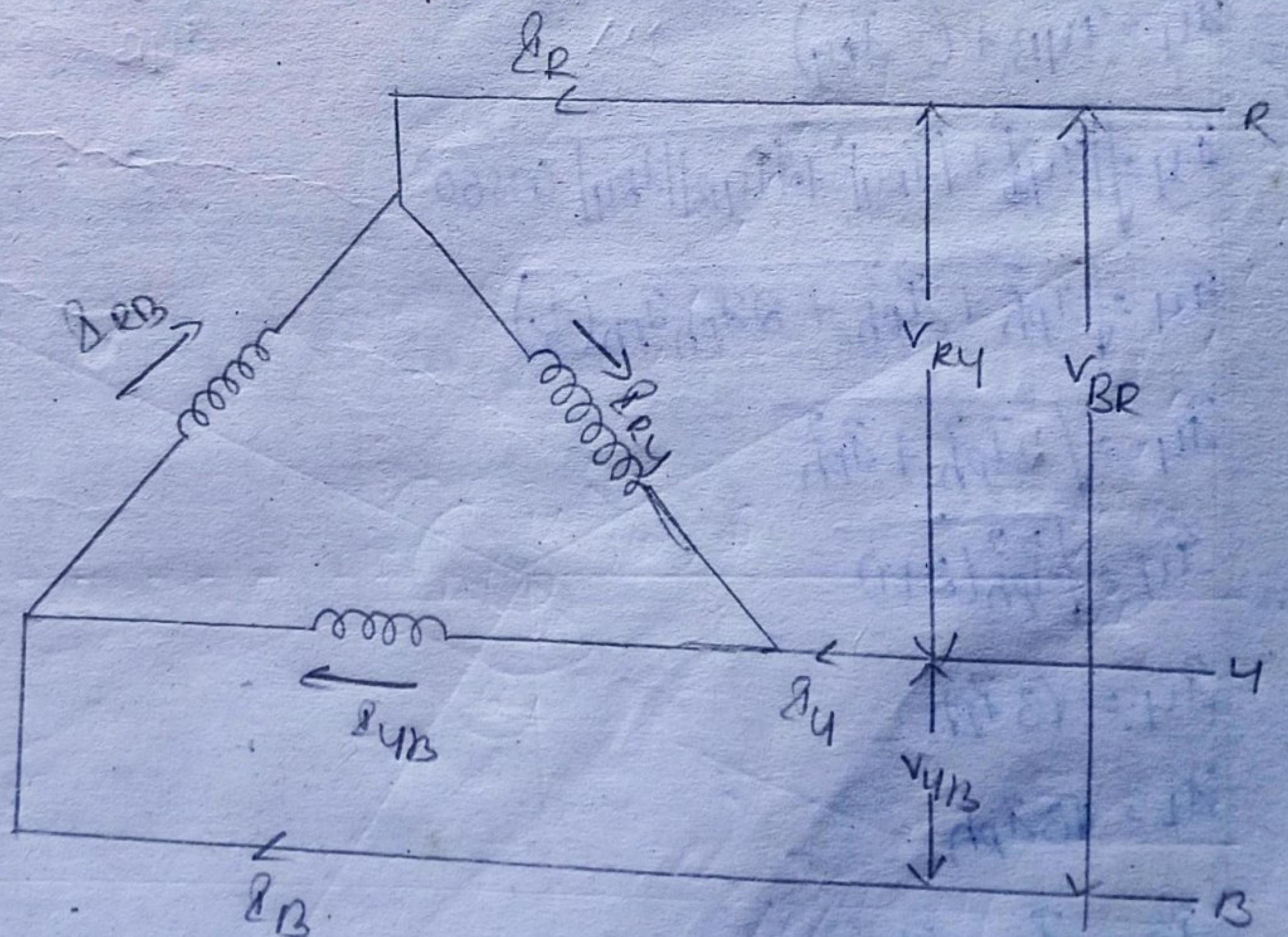

In delta connection the current in each line is the vector difference two phase currents flowing through the line

- * The vector difference of corresponding phase currents
- * Assume the three phase currents in delta are I_{RY}, I_{YB}, I_{BR} and the line current I_R, I_Y, I_B in

* In delta connection

$$|I_{RY}| = |I_{YB}| = |I_{BR}| = I_{ph}$$

- * The line current I_R is vector difference of the I_{RY} & I_{BR}

$$I_R = I_{RY} - I_{BR}$$

$$I_R = I_{RY} + (-I_{BR})$$

$$I_R = \sqrt{|I_{RY}|^2 + |I_{BR}|^2 + 2|I_{RY}||I_{BR}|\cos 60^\circ}$$

$$I_R = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph}I_{ph}\cos 60^\circ}$$

$$I_R = \sqrt{2I_{ph}^2 + 2I_{ph}^2\left(\frac{1}{2}\right)}$$

$$I_R = \sqrt{I_{ph}^2(2+1)}$$

$$I_R = \sqrt{3}I_{ph}$$

$$I_Y = I_{YB} - I_{RY}$$

$$I_Y = I_{YB} + (-I_{RY})$$

$$I_Y = \sqrt{|I_{YB}|^2 + |I_{RY}|^2 + 2|I_{YB}||I_{RY}|\cos 60^\circ}$$

$$I_Y = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph}I_{ph}\left(\frac{1}{2}\right)}$$

$$I_Y = \sqrt{2I_{ph}^2 + I_{ph}^2}$$


$$I_Y = \sqrt{I_{ph}^2(2+1)}$$

$$I_Y = \sqrt{3}I_{ph}$$

$$I_L = \sqrt{3}I_{ph}$$

$$I_B = I_{BR} - I_{YB}$$

$$I_B = \sqrt{|I_{BR}|^2 + |I_{YB}|^2 + 2|I_{BR}||I_{YB}|\cos 60^\circ}$$

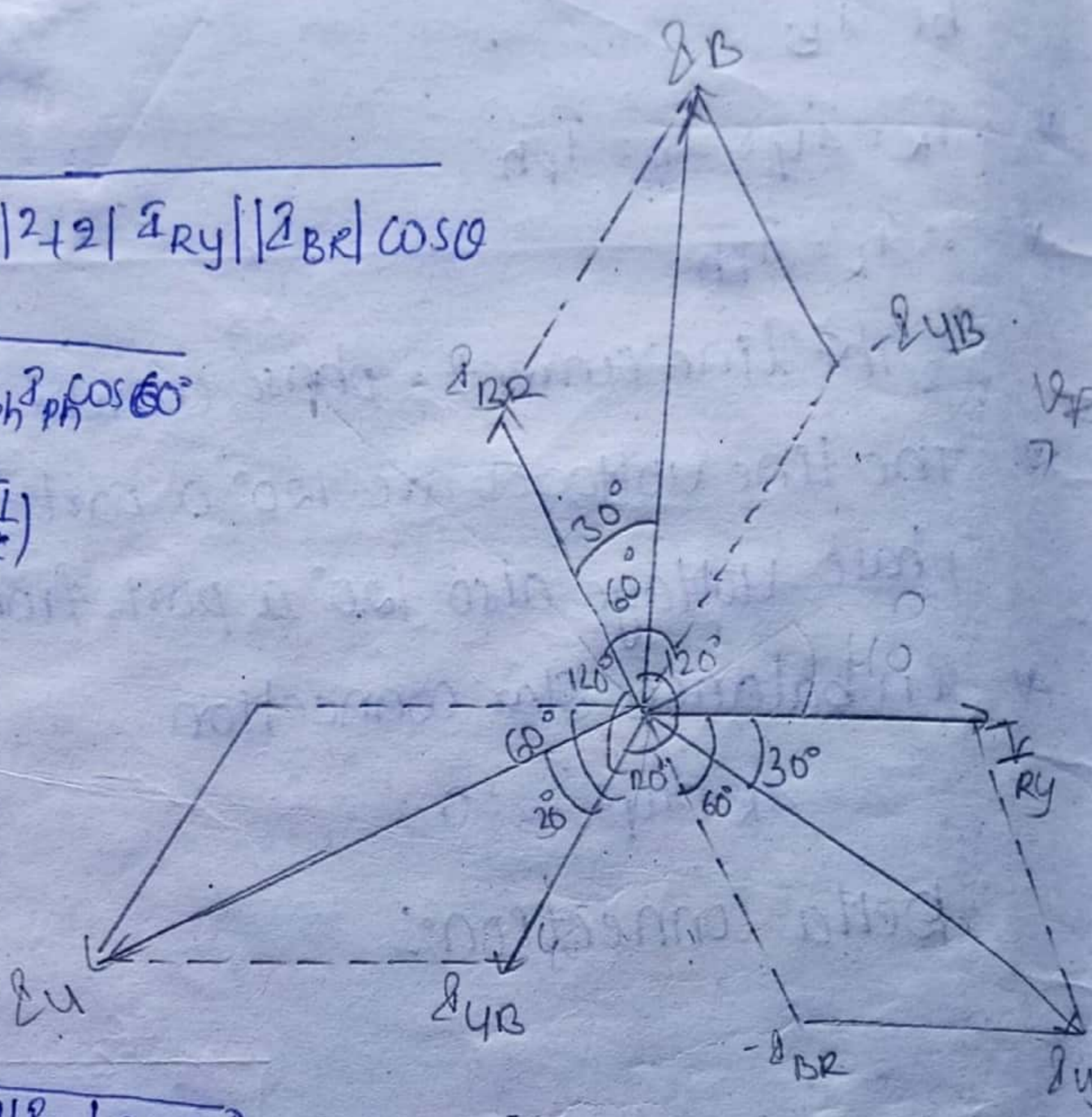

$$I_L = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph}I_{ph}\cos 60}$$

$$I_L = \sqrt{2I_{ph}^2 + 2I_{ph}^2\left(\frac{1}{2}\right)}$$

$$I_L = \sqrt{3I_{ph}^2}$$

$$I_L = \sqrt{3}I_{ph}$$

In delta connection $I_R = I_Y = I_B = I_L$

$$\therefore I_L = I_R = I_Y = I_B = \sqrt{3}I_{ph}$$

$$I_L = \sqrt{3}I_{ph}$$

→ In delta connection there is no neutral point. So, phase voltage is same as that of line voltage.

$$V_{RY} = V_{YB} = V_{BR} = V_{ph}$$

$$V_L = V_{ph}$$

→ In delta connection the line currents are 120° apart from each other & phase currents also 120° apart from each other.

Power in star connection

The total active power or True power in 3-phase load is the sum of power in the 3 phases for a balanced load. The power in each load is the same.

Hence total power = 3 power in each phase.

$$P = V_L I_L \cos \phi \quad \phi \text{ is the angle b/w voltage \& current}$$

$$P_{1\phi} = I_{ph} V_{ph} \cos \phi$$

$$P_{3\phi} = 3 V_{ph} I_{ph} \cos \phi$$

In star connection

$$V_L = \sqrt{3} V_{ph} \quad I_L = I_{ph}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}}$$

$$P_{3\phi} = 3 \frac{V_L}{\sqrt{3}} I_L \cos \phi$$

$$P_{3\phi} = \sqrt{3} V_L I_L \cos \phi$$

it is the active power

$$P_{3\phi} = \sqrt{3} V_L I_L \cos \phi \text{ k.w k}$$

Reactive power

$$Q = VI \sin \phi$$

$$Q_{3\phi} = 3 V_{ph} I_{ph} \sin \phi$$

$$Q_{3\phi} = \frac{V_L}{\sqrt{3}} 3 I_L \sin \phi$$

$$Q_{3\phi} = \sqrt{3} V_L I_L \sin \phi \text{ KUAR.}$$

Apparent power

$$S = VI$$

$$S_{3\phi} = 3 V_{ph} I_{ph}$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L$$

$$= \sqrt{3} V_L I_L = \sqrt{3} V_L I_L \text{ KVA}$$

power in delta connection

$$P = VI \cos \phi$$

In delta connection

$$I_L = \sqrt{3} I_{ph} \quad I_{ph} = \frac{I_L}{\sqrt{3}}$$

$$V_L = V_{ph}$$

$$P_{3\phi} = 3 V_{ph} I_{ph} \cos \phi$$

$$= 3 V_L \frac{I_L}{\sqrt{3}} \cos \phi$$

$$= \sqrt{3} V_L I_L \cos \phi$$

True power

$$P_{3\phi} = \sqrt{3} V_L I_L \cos \phi \text{ k.w}$$

$$P_L = \frac{V_L I_L}{\sqrt{3}} \cos \phi$$

$$I_L = \sqrt{3} I_{ph}$$

$$I_{ph} = \frac{I_L}{\sqrt{3}}$$

$$V_L = V_{ph}$$

$$P_{3\phi} = 3 V_{ph} I_{ph} \cos \phi$$

Reactive power

$$Q = UI \sin \phi$$

$$Q_{3\phi} = 3U_{ph} I_{ph} \sin \phi$$

$$Q_{3\phi} = 3U_L \frac{I_L}{\sqrt{3}} \sin \phi$$

$$Q_{3\phi} = \sqrt{3} U_L I_L \sin \phi \text{ (KVAR)}$$

In delta connection the total power in the delta circuit is the sum of the power in the 3 ϕ 's the load is balance. The power consumed in each phase is same

the total power = 3 x power in each phase


Apparent power


$$S_{3\phi} = 3V_{ph} I_{ph}$$

$$S_{3\phi} = 3U_L \frac{I_L}{\sqrt{3}}$$

$$= \sqrt{3} U_L I_L \text{ KVA}$$

3-phase balanced delta connection

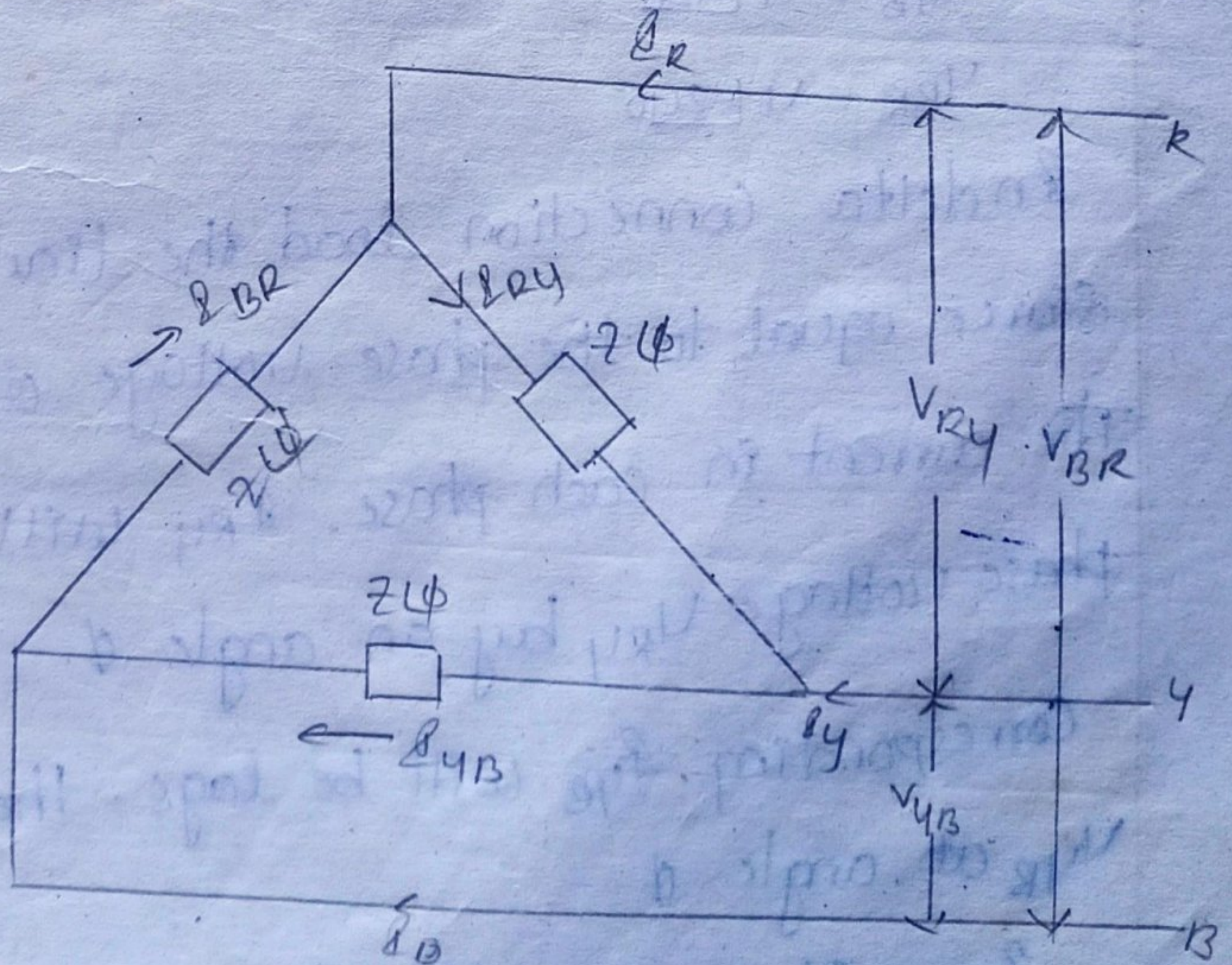

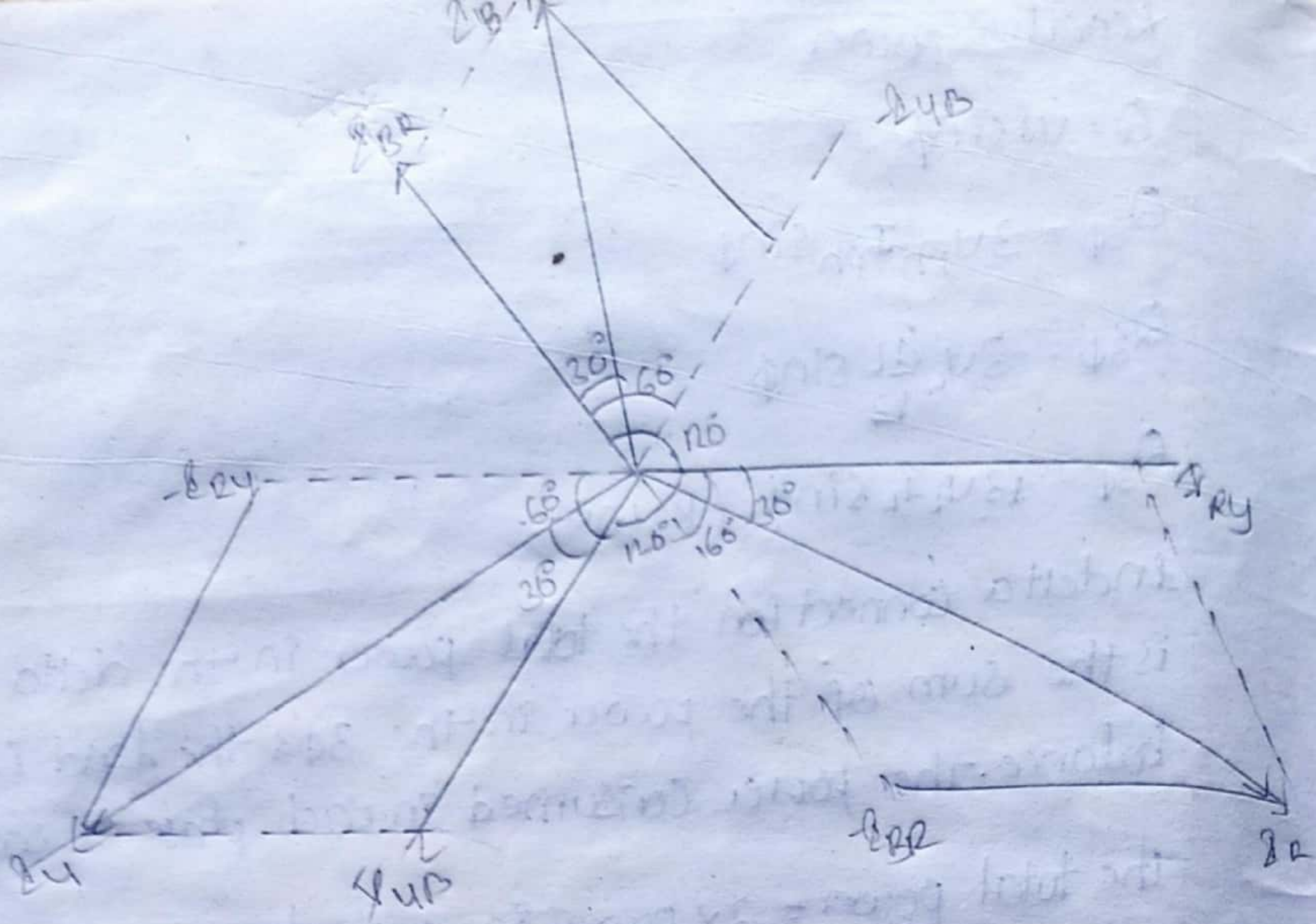

A 3 ϕ 3w/1 ϕ balance system supplying power to a balanced 3 ϕ delta load the phase sequence is R,Y,B let us assume the line voltages $V_{RY} = V_L \angle 0^\circ$ as the reference phasor then the three source voltages are given by

$$V_{RY} = V_L \angle 0^\circ$$

$$V_{YB} = V_L \angle 120^\circ$$

$$V_{BR} = V_L \angle 240^\circ$$

In delta connection load the line voltage of the source equal to the phase voltage of the load. The current in each phase, I_{RY} will be lags the phase voltage V_{RY} by an angle ϕ

Corresponding I_{YB} will be lags the phase voltage V_{YB} at angle ϕ

I_{BR} will be lags the phase voltage V_{BR} at an angle ϕ . If the load impedance is Z at angle ϕ

The current flowing in the 3 load impedence are

$$I_{RY} = \frac{V_{RY} \angle 0^\circ}{Z \angle \phi} = \frac{V \angle 0^\circ}{Z \angle \phi} = \left| \frac{V}{Z} \right| \angle -\phi$$

$\angle 0^\circ$

$$I_{YB} = \frac{V_{YB} \angle -120^\circ}{Z \angle \phi} = \frac{V \angle -120^\circ}{Z \angle \phi} = \left| \frac{V}{Z} \right| \angle -120^\circ - \phi$$

$$I_{BR} = \frac{V_{BR} \angle -240^\circ}{Z \angle \phi} = \frac{V \angle -240^\circ}{Z \angle \phi} = \left| \frac{V}{Z} \right| \angle -240^\circ - \phi$$

The line currents are $\sqrt{3}$ ph from phasor diagram 30° behind. they respective phase currents in the line R is given by

$$I_R = \sqrt{3} I_{RY} \\ = \sqrt{3} \left| \frac{V}{Z} \right| \angle -\phi - 30^\circ$$

$$I_Y = \sqrt{3} I_{YB} \\ = \sqrt{3} \left| \frac{V}{Z} \right| \angle -120^\circ - \phi$$



$$I_B = \sqrt{3} I_{BR} \\ = \sqrt{3} \left| \frac{V}{Z} \right| \angle -240^\circ - \phi$$

(1+)

Blank

Blank

Balanced 3-phase star connected load:-

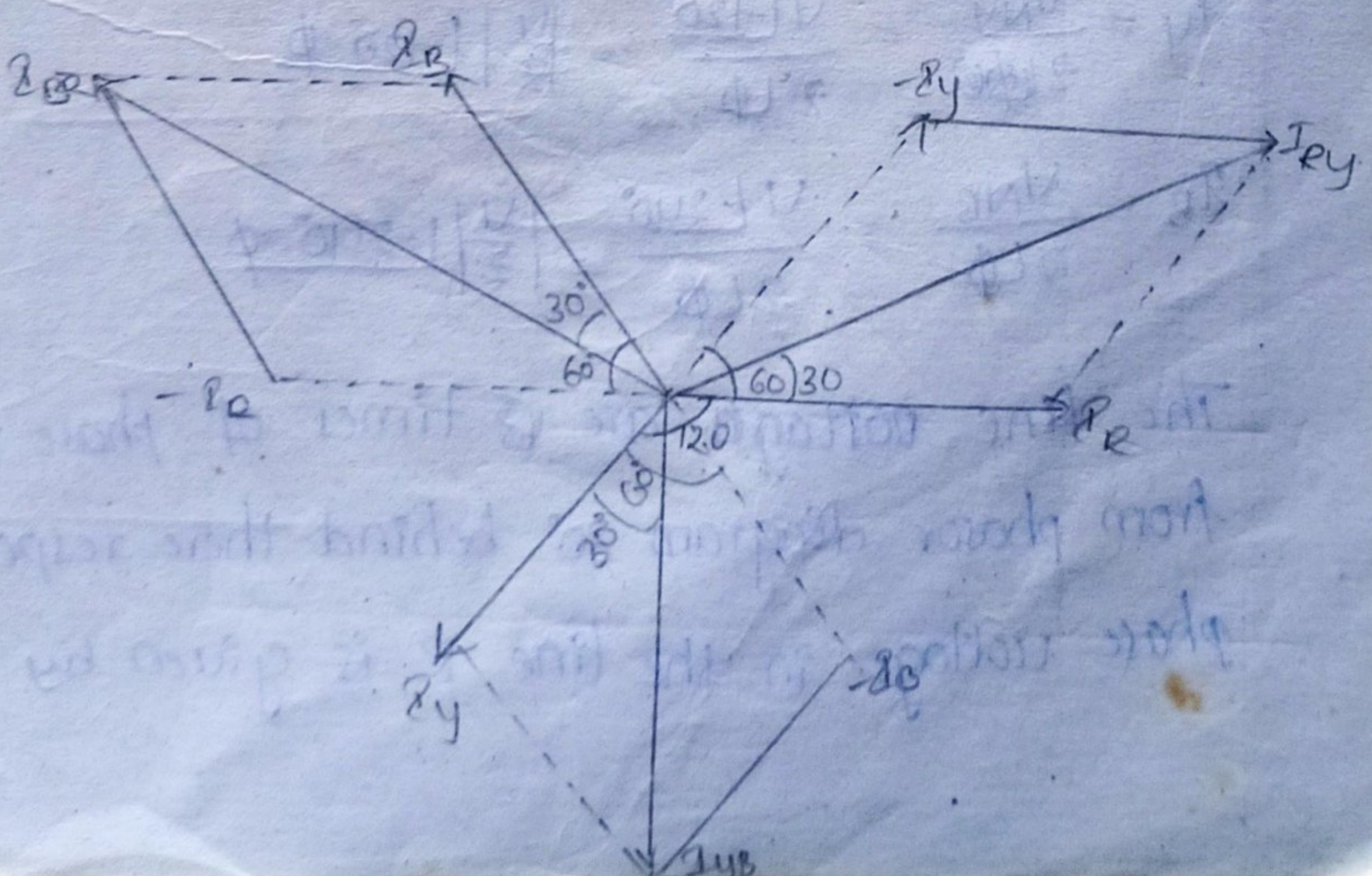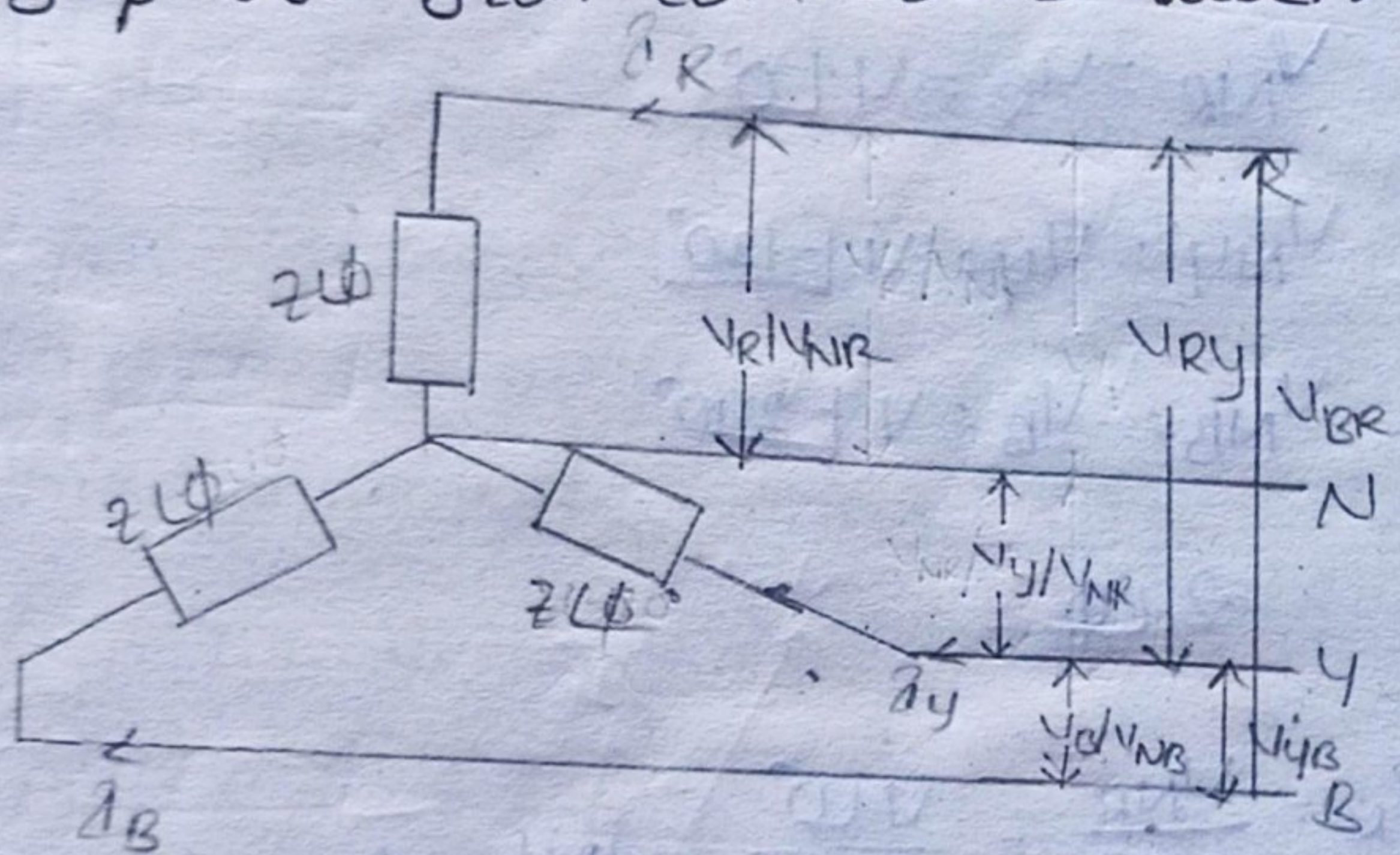

Consider a 3-phase 3 wire system supplying a power to a balance 3-phase star connected load the phase sequence is R, Y, B

In star connection phase current equal to line current

$$\text{i.e. } I_{ph} = I_L$$

The three-line or phase currents I_R, I_Y, I_B

The phase voltages V_R, V_Y, V_B (or) V_{NR}, V_{NY}, V_{NB} in between any line & neutral

Let us assume $V_{NR} = V \angle 0^\circ$ as reference phasor

Z_L is the load impedance.

$$V_{NR} = V_R = V \angle 0^\circ$$

$$V_{NY} = V_Y = V \angle -120^\circ$$

$$V_{NB} = V_B = V \angle 240^\circ$$

Z_L


$$I_R = \frac{V_{NR}}{Z_L} = \frac{V \angle 0^\circ}{Z_L} = \left| \frac{V}{Z} \right| \angle -\phi$$

$$I_Y = \frac{V_{NY}}{Z_L} = \frac{V \angle -120^\circ}{Z_L} = \left| \frac{V}{Z} \right| \angle -120^\circ - \phi$$


$$I_B = \frac{V_{NB}}{Z_L} = \frac{V \angle 240^\circ}{Z_L} = \left| \frac{V}{Z} \right| \angle 240^\circ - \phi$$

The line voltages are $\sqrt{3}$ times of phase voltages from phasor diagram 30° behind their respective phase voltage in the line R is given by

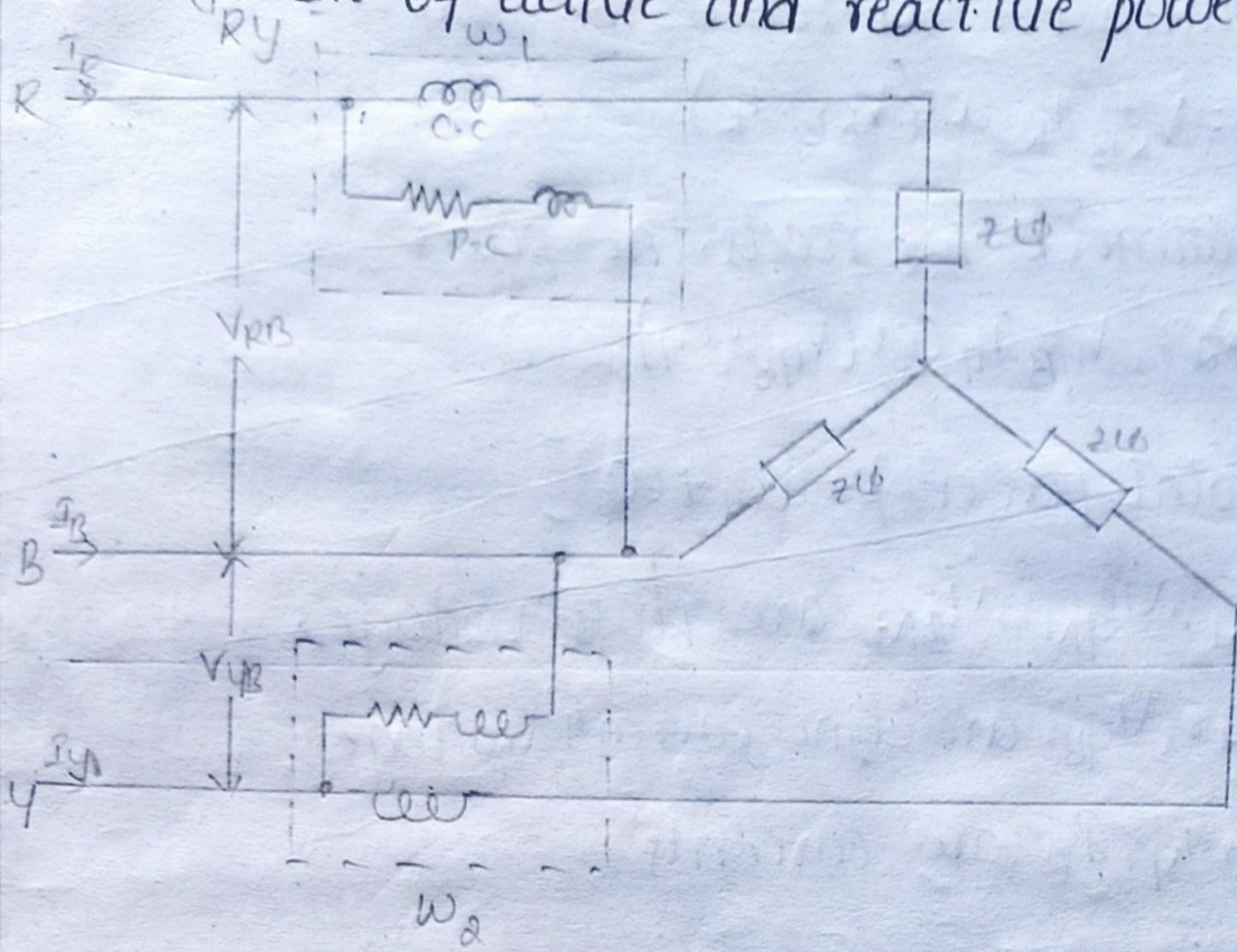Measurement of active and reactive powers:



- * Two wattmeters are connected and are shown in figure for ^{Star} connected load.
- * Two current coils are connected to a any pair of lines and potential coil is connected to a third line
- * The algebraic sum of the 2 wattmeter will gives the total power three phase load whether load is balanced
- * The line voltages are V_{RB} & V_{YB} .
- * The line currents are I_R & I_Y & I_B
- * The phase voltages are V_R, V_Y, V_B or V_{NR}, V_{NY}, V_{NB}
- * Assume the load is lagging load. the currents I_R, I_Y, I_B lags ~~sur~~ an angle ϕ by V_{RN}, V_{NY}, V_{NB} respectively

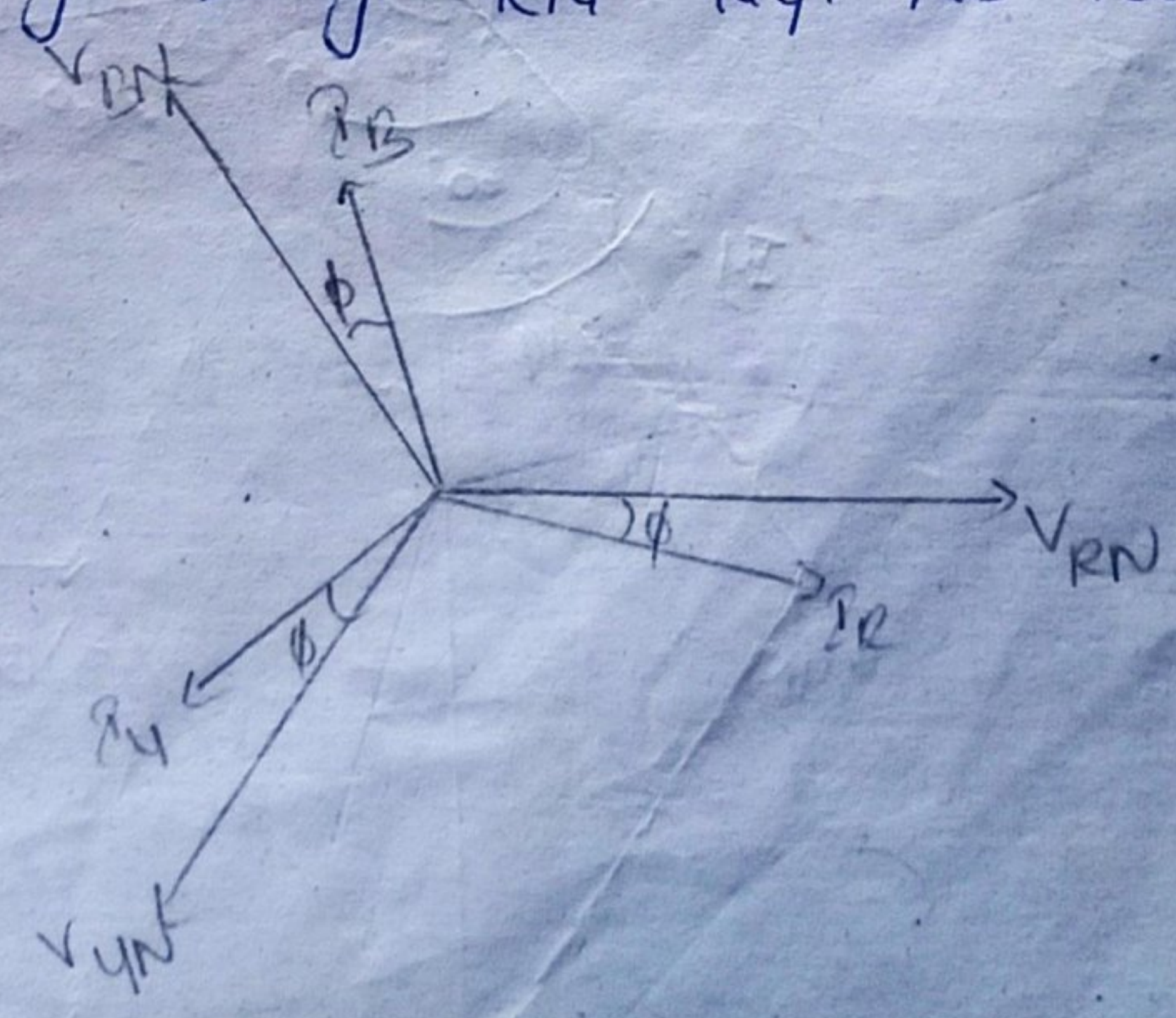

* The wattmeter w_1 reads the power

$$W_1 = V_{RB} \hat{I}_R \cos(\angle V_{RB} \hat{I}_R)$$

* The wattmeter w_2 reads the power

$$W_2 = V_{YB} \hat{I}_Y \cos(\angle V_{YB} \hat{I}_Y)$$

* The total power $p = W_1 + W_2$

V_{RN}, V_{YN}, V_{BN} are phase voltages

V_{RB}, V_{YB} are line ~~current~~ voltages

$\hat{I}_R, \hat{I}_Y, \hat{I}_B$ are currents


i.e. $\hat{I}_R = \hat{I}_Y = \hat{I}_B = \hat{I}_L = \hat{I}_{ph}$

$$V_{RB} = V_{RN} - V_{BN}$$

$$= V_{RN} + (-V_{BN})$$

$$V_{YB} = V_{YN} - V_{BN}$$

$$= V_{YN} + (-V_{BN})$$

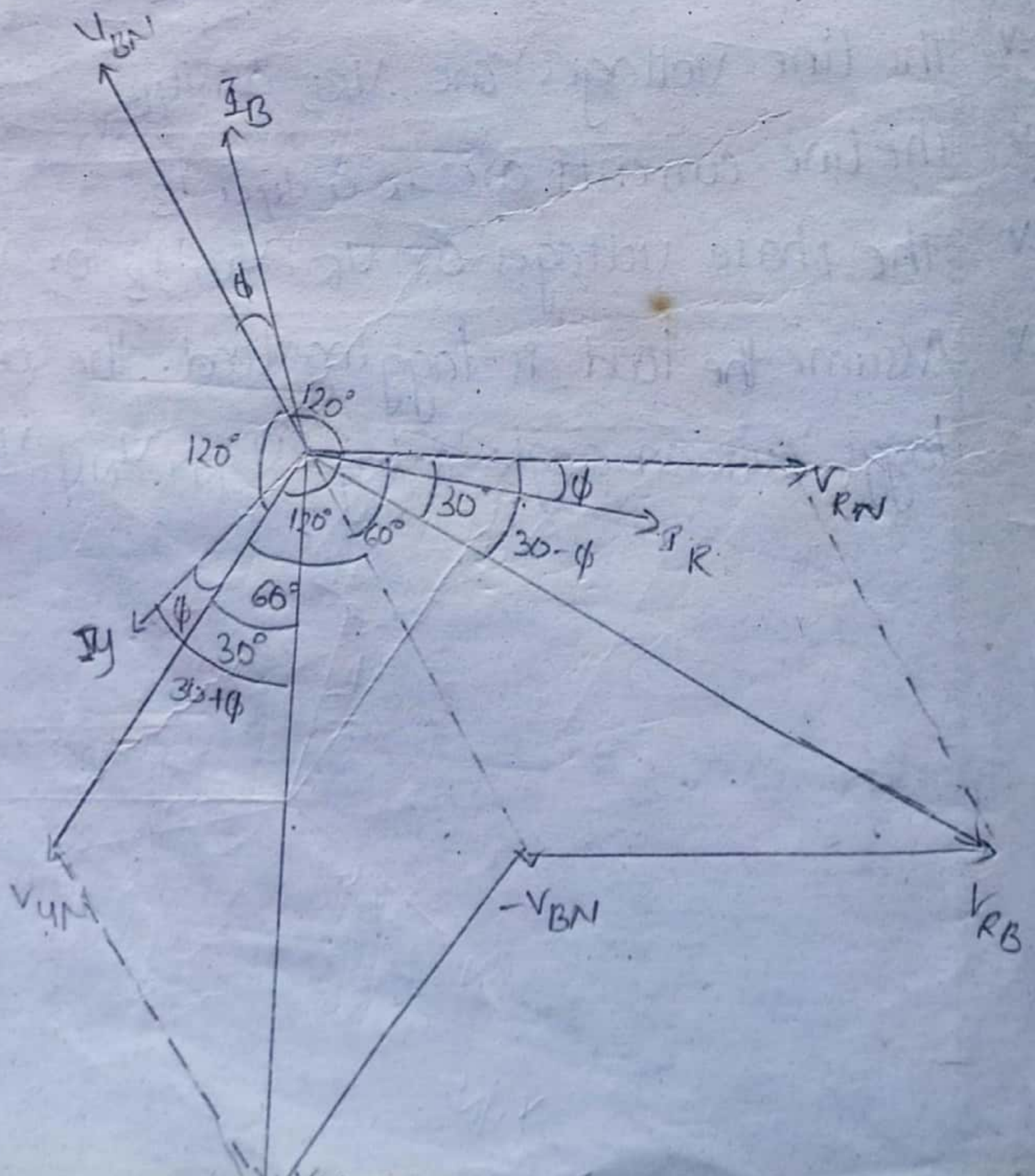

The angle between V_{RN} & I_R is ϕ ,

V_{YN} & I_Y is ϕ

$$V_{RN} = V_{YN} = V_{BN} = V_{ph}$$

$$V_{RB} = V_{YB} = V_L$$

$$I_R = I_Y = I_B = I_L = I_{ph}$$

From phasor diagram the angle between V_{RB} & I_R is $30-\phi$

The angle between V_{YB} & I_Y is $30+\phi$

The wattmeter w_1 reads the power

$$w_1 = V_{RB} I_R \cos(\angle V_{RB} \hat{I}_R) \\ = V_{RB} I_R \cos(30-\phi)$$

The wattmeter w_2 reads the power

$$w_2 = V_{YB} I_Y \cos(\angle V_{YB} \hat{I}_Y) \\ = V_{YB} I_Y \cos(30+\phi)$$

$$w_1 = P_1 = V_{RB} I_R \cos(\angle V_{RB} \hat{I}_R)$$

$$w_1 = P_1 = V_L I_L \cos(30-\phi)$$

$$w_2 = P_2 = V_{YB} I_Y \cos(\angle V_{YB} \hat{I}_Y)$$

$$w_2 = P_2 = V_L I_L \cos(30+\phi)$$

Total power $w = w_1 + w_2$

$$= V_L I_L \cos(30-\phi) + V_L I_L \cos(30+\phi)$$

$$= V_L I_L [\cos(30-\phi) + \cos(30+\phi)]$$

Active power $P = V_L I_L [\cos 30 \cdot \cos \phi + \sin 30 \cdot \sin \phi + \cos 30 \cdot \cos \phi - \sin 30 \cdot \sin \phi]$

$$P = V_L I_L 2 \cos 30 \cdot \cos \phi$$

$$P = V_L I_L 2 \cos \phi \frac{\sqrt{3}}{2}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$\therefore \cos(C-D) = \cos C \cos D + \sin C \sin D$$

$$\cos(C+D) = \cos C \cos D - \sin C \sin D$$

Reactive power $Q = \omega_1 - \omega_2$

$$Q = V_L I_L \cos(30^\circ - \phi) - V_L I_L \cos(30^\circ + \phi)$$

$$Q = V_L I_L [\cos(30^\circ - \phi) - \cos(30^\circ + \phi)]$$

$$Q = V_L I_L [\cos 30^\circ \cdot \cos \phi + \sin 30^\circ \sin \phi - \cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi]$$

$$Q = V_L I_L 2 \sin 30^\circ \sin \phi$$

$$Q = V_L I_L \sin \phi$$

$$Q = V_L I_L \sin \phi$$

But we know

$$Q = \sqrt{3} V_L I_L \sin \phi$$

$$Q = \sqrt{3} [\omega_1 - \omega_2]$$

Power factor:-

To find out the power factor by using two wattmeter

W.K.T

$$P = \omega_1 + \omega_2 = \sqrt{3} V_L I_L \cos \phi \rightarrow (1)$$

$$Q = \omega_1 - \omega_2 = V_L I_L \sin \phi \rightarrow (2)$$

$$\frac{(2)}{(1)} \Rightarrow \frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} = \frac{V_L I_L \sin \phi}{\sqrt{3} V_L I_L \cos \phi}$$

$$\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} = \frac{1}{\sqrt{3}} \tan \phi$$

$$\tan \phi = \sqrt{3} \left[\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right]$$

$$\phi = \tan^{-1} \left[\sqrt{3} \left[\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right] \right]$$

pb: 1 Two wattmeter are used to measure power in a 3- ϕ 3 wire load. Determine the total power, power factor and reactive power. If two wattmeters are read \bar{i} , 1000 watts each both positive \bar{ii} , 1000 watts each but opposite sign.

Given

\bar{i} , $\omega_1 = 1000\text{w}$, $\omega_2 = 1000\text{w}$

both are positive

\bar{ii} Total power $p = \omega_1 + \omega_2 = 2000\text{w}$

\bar{iii} Reactive power $Q = \sqrt{3}(\omega_1 - \omega_2) = \sqrt{3}(1000 - 1000) = 0$

\bar{iv} power factor $\cos\phi = ?$

$$\text{phase angle } \phi = \tan^{-1} \left[\frac{\sqrt{3}(\omega_1 - \omega_2)}{\omega_1 + \omega_2} \right] = \tan^{-1} \left(\frac{\sqrt{3}(0)}{2000} \right) = 0$$

$$\phi = 0$$

\bar{ii} , Opposite sign.

\bar{i} , $\omega_1 = 1000\text{w}$; $\omega_2 = -1000\text{w}$

$$\begin{aligned} \text{Total power } p &= \omega_1 - \omega_2 \\ &= 1000 - (-1000) \\ &= 2000 \end{aligned}$$

$$\begin{aligned} \text{Reactive power } Q &= \sqrt{3}(\omega_1 - \omega_2) \\ &= \sqrt{3}(1000 - (-1000)) \\ &= \sqrt{3}(2000) = 3464.1 \end{aligned}$$

power factor $\cos\phi = ?$

$$\text{phase angle } \phi = \tan^{-1} \left[\frac{\sqrt{3}(\omega_1 - \omega_2)}{\omega_1 + \omega_2} \right]$$

$$\phi = \tan^{-1} \left(\frac{\sqrt{3}(1000 - (-1000))}{1000 - 1000} \right)$$

$$\omega_1 \& \omega_2 = 1000$$

$$\omega_1 + \omega_2 = 1000 + 1000 = 2000$$

$$\omega_1 - \omega_2 = 1000 - 1000 = 0$$

$$\omega_1 = +1000$$

$$\omega_2 = -1000$$

$$Q = \sqrt{3}(\omega_1 - \omega_2)$$

$$= \sqrt{3}(\omega_1 - (-\omega_2))$$

$$= \sqrt{3}(1000 - (-1000))$$

$$\phi = \tan^{-1} \left(\frac{\sqrt{3}(2000)}{0} \right)$$

$$\phi = \tan^{-1} \infty$$

$$\phi = \tan^{-1} \tan 90$$

$$\phi = 90^\circ$$

$$\cos \phi = \cos 90^\circ = 0$$

Q.2 The power delivered to a balanced delta connected load a ~~400 volt~~ ^{volt} 3- ϕ supply is measured by a two wattmeter methods. if the reads of the two wattmeters are 2000 Watts 1500 watts respectively. calculate magnitude of the impedance in each arm of the delta connected load & its resistive component.

Given.

Delta connected load

$$V_L = 400 \text{ V } \text{ } 3\text{-}\phi$$

$$f = 50 \text{ Hz}$$

$$P_1 = W_1 = 2000 \text{ W}$$

$$P_2 = W_2 = 1500 \text{ W}$$

$$Z = 2$$

$$R = 2$$

$$\text{The phase angle } \phi = \tan^{-1} \left(\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right)$$

$$= \tan^{-1} \left(\frac{\sqrt{3}(2000 - 1500)}{2000 + 1500} \right)$$

$$= \tan^{-1} \left(\frac{\sqrt{3}(500)}{3500} \right)$$

$$= 13.49^\circ$$

$$\cos \phi = 0.97$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$P = 101 + 102 = 3500 \text{ W}$$

$$I_L = \frac{P}{\sqrt{3} V_L \cos \phi} = \frac{3500}{\sqrt{3} \times 400 \times (0.97)}$$

$$I_L = 5.2080 \text{ Amp.}$$

In delta connection

$$\sqrt{3} V_L = I_L Z$$

$$Z = \frac{\sqrt{3} V_L}{I_L}$$

$$Z = 133.08 \Omega$$

The relation b/w Z & R is from $\cos \phi = \frac{R}{Z}$.

$$R = Z \cos \phi$$

$$R = 129.08 \Omega$$

Q.3 A balance 3- ϕ star

connected load of 150 kW. takes a leading current of 100 amp. with a line voltage of 1100 volts, 50 Hz find the circuit constants of the load for phase

Given

$$f = 50 \text{ Hz}$$

$$V_L = 1100 \text{ V}$$

$$P = 150 \text{ kW}$$

$$\text{load current } I_L = 100 \text{ A}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$\cos \phi = \frac{P}{\sqrt{3} V_L I_L}$$

$$\phi = \cos^{-1} \left(\frac{150 \times 10^3}{\sqrt{3} (1100) (100)} \right)$$




$$\phi = 38.06$$

$$\cos \phi = 0.7872$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$I_L = \frac{P}{\sqrt{3} V_L \cos \phi}$$

$$\sqrt{3} V_L = I_L Z$$

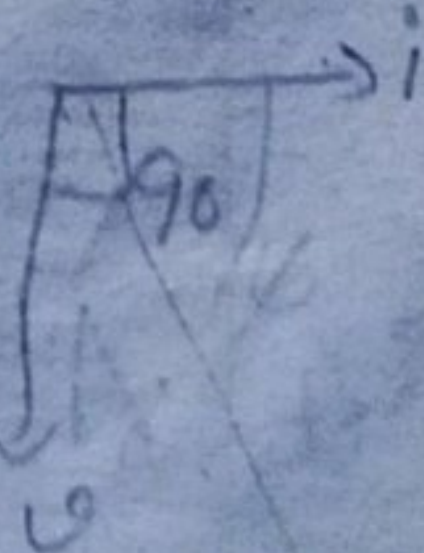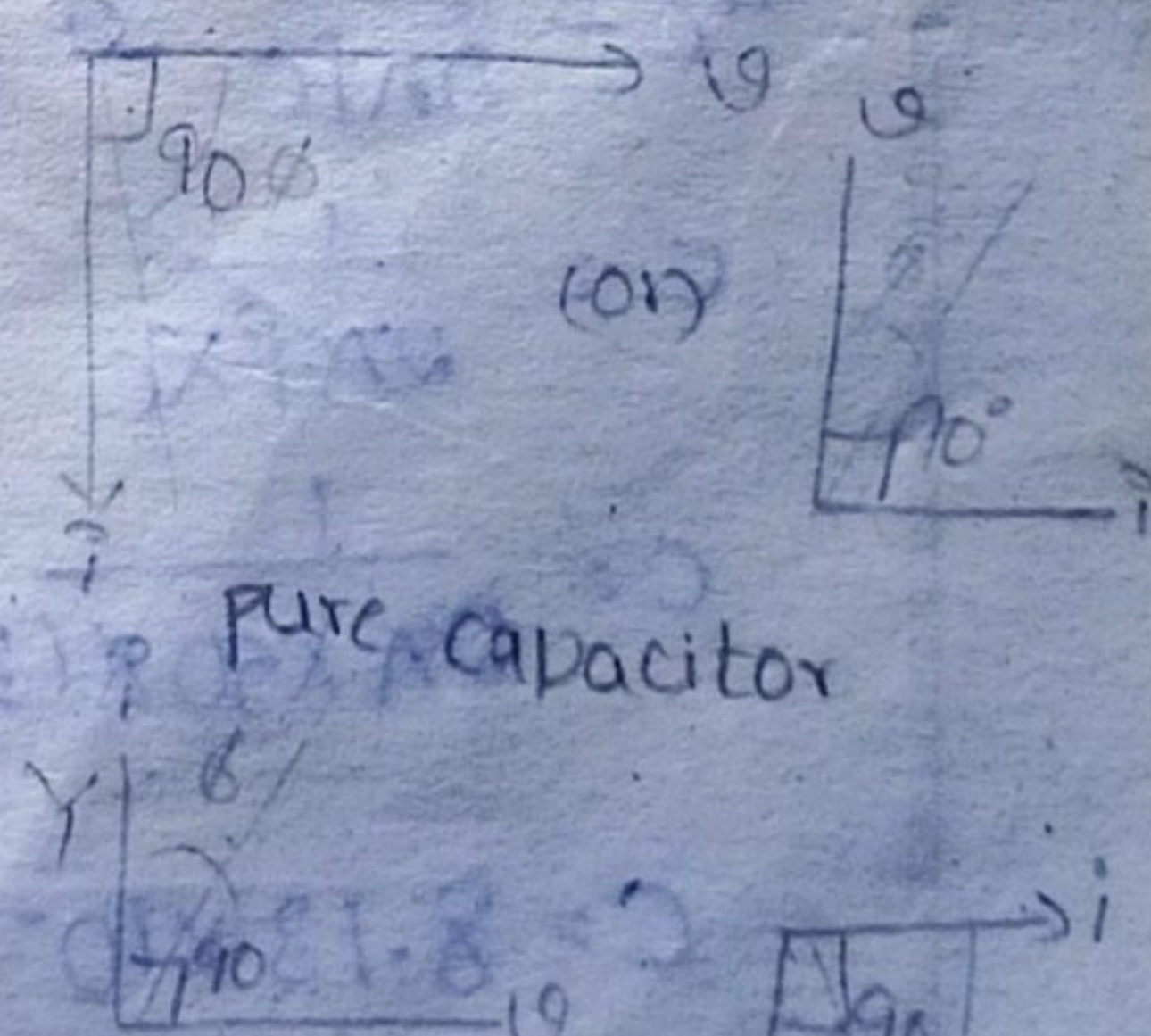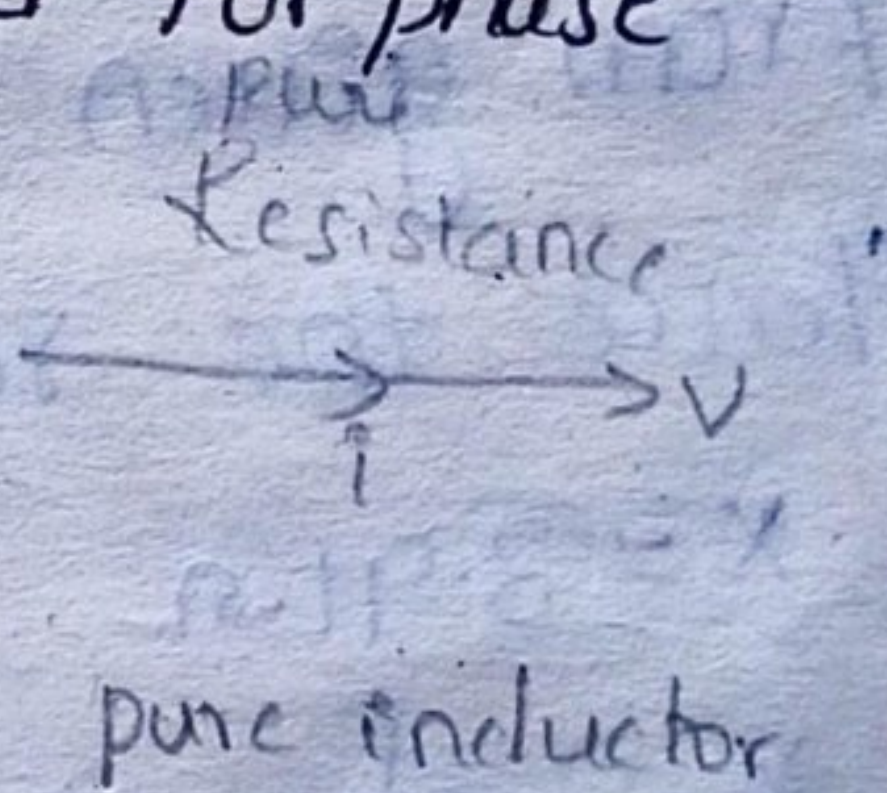

$$\cos \phi = \frac{R}{Z}$$

$$R = Z \cos \phi$$

$$Z = \frac{\sqrt{3} V_L}{\sqrt{3} I_L}$$

$$Z = \frac{1100}{\sqrt{3} 100}$$

$$Z = 1100 \cos \phi = 6.35 \Omega$$

$$R = Z \cos \phi$$

$$R = 6.35 (0.7872)$$

$$R = 4.99 \Omega$$

$$\sin \phi = \frac{X}{Z}$$

$$X = Z \sin \phi = (6.35)(0.616)$$

$$X = 3.91 \Omega$$

$$X = 3.91 \Omega$$

From given problem current is leading component
hence the reactance is taken capacitive reactance

$$X = 3.91 \Omega \quad X \text{ is taken as } X_c$$


$$X_c = \frac{1}{2\pi f C} \Omega \quad X = X_c$$

$$C = \frac{1}{2\pi f X_c}$$

$$C = \frac{1}{2\pi \times 50 \times (3.91)}$$

$$C = 8.13 \times 10^{-4} \text{ Faraday}$$

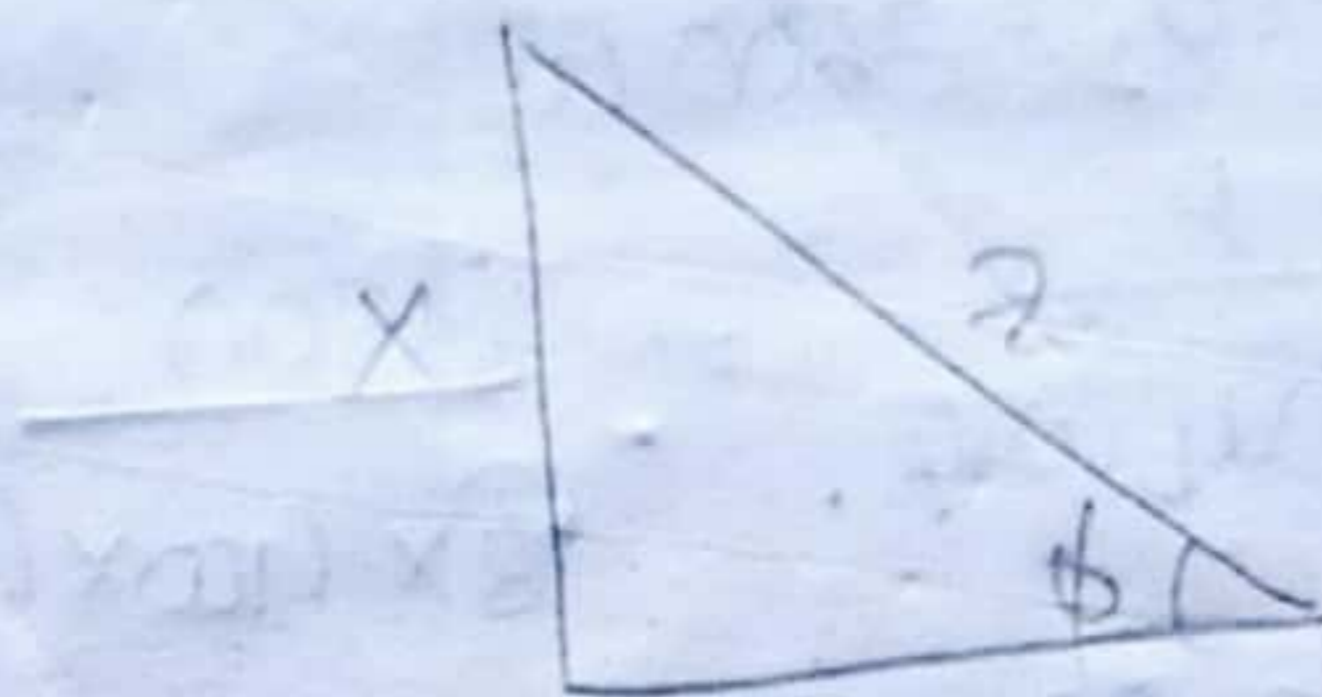4 A balanced delta connected load is supplied from a symmetrical 3 ϕ 400V, 50Hz supply system. The current in each phase is 20A & lags behind it



In delta connection

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

In star

$$I_L = I_{ph}$$

$$V_L = \sqrt{3} V_{ph}$$

phase voltage by an angle 40°

i. Line current ii. Total power iii. also draw the phasor diagram showing the voltages & currents in the lines & phases iv. The wattmeter reading in two wattmeter are used.

Sol Given data

delta connected load

$$V_L = V_{ph} = 400V$$

$$\phi = 40^\circ$$

$$f = 50 \text{ Hz}$$

$$I_{ph} = 20 \text{ A}$$

i. line current $I_L = \sqrt{3} I_{ph}$

$$I_L = \sqrt{3}(20)$$

$$I_L = 34.64 \text{ amp}$$

ii. Total power

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$Q = \sqrt{3} V_L I_L \sin \phi$$

$\cos \phi$

$$P = \sqrt{3} \times 400 \times 34.64 \times \cos 40^\circ$$

$$P = 23999.2 \times \cos 40^\circ$$

$$P = 23999.2 \times (0.766)$$

$$P = 18384.4 \text{ watts}$$

$$Q = \sqrt{3} V_L I_L \sin \phi$$


$$= 23999.2 \times (0.643)$$

$$= 15426.3 \text{ watts}$$

$$S = \sqrt{3} V_L I_L$$

$$S = 23999.2 \text{ watt}$$


$$S = 1809.9$$

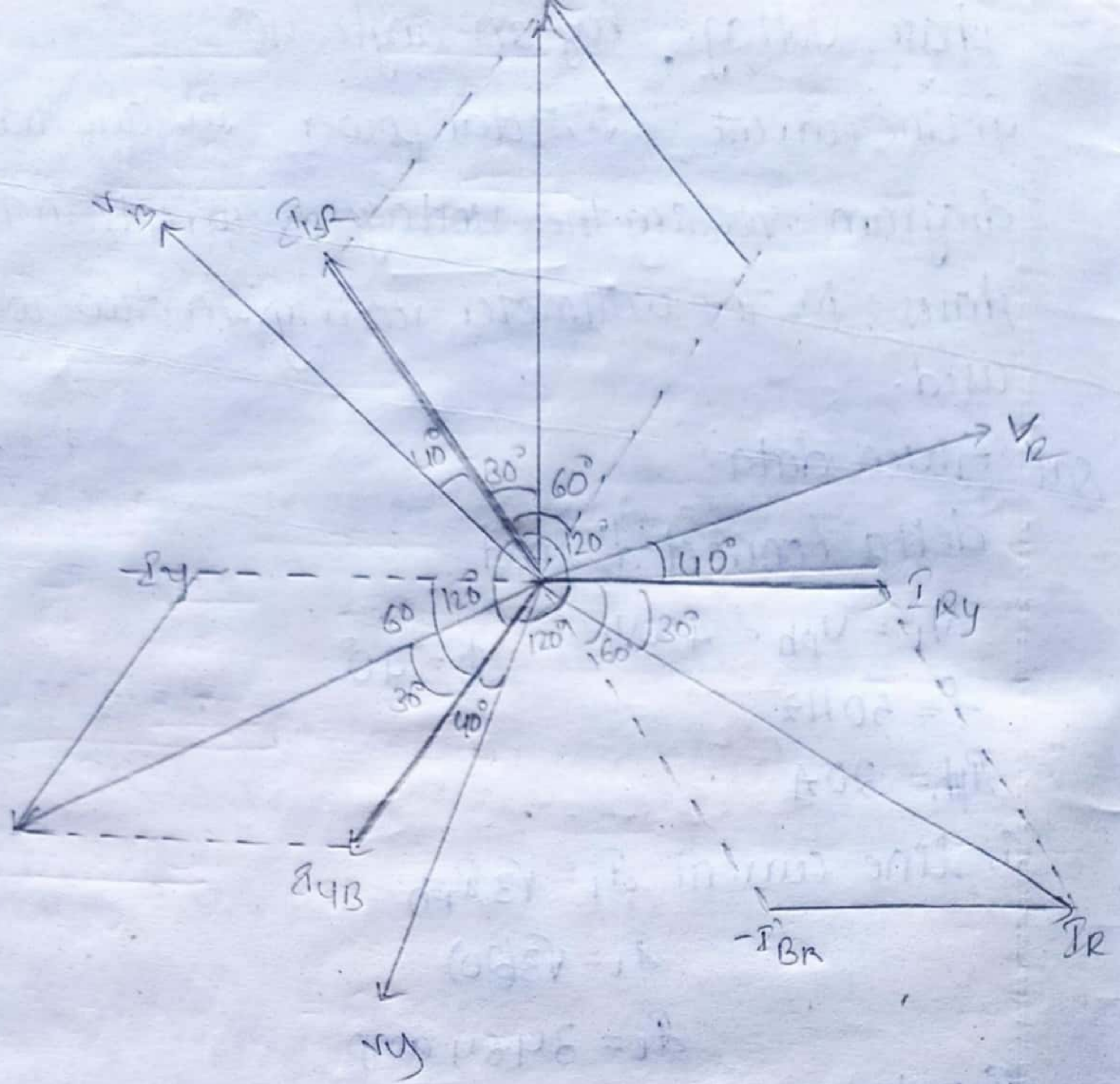

24-07-22

unbalanced 3-phase circuits

Star connection:-

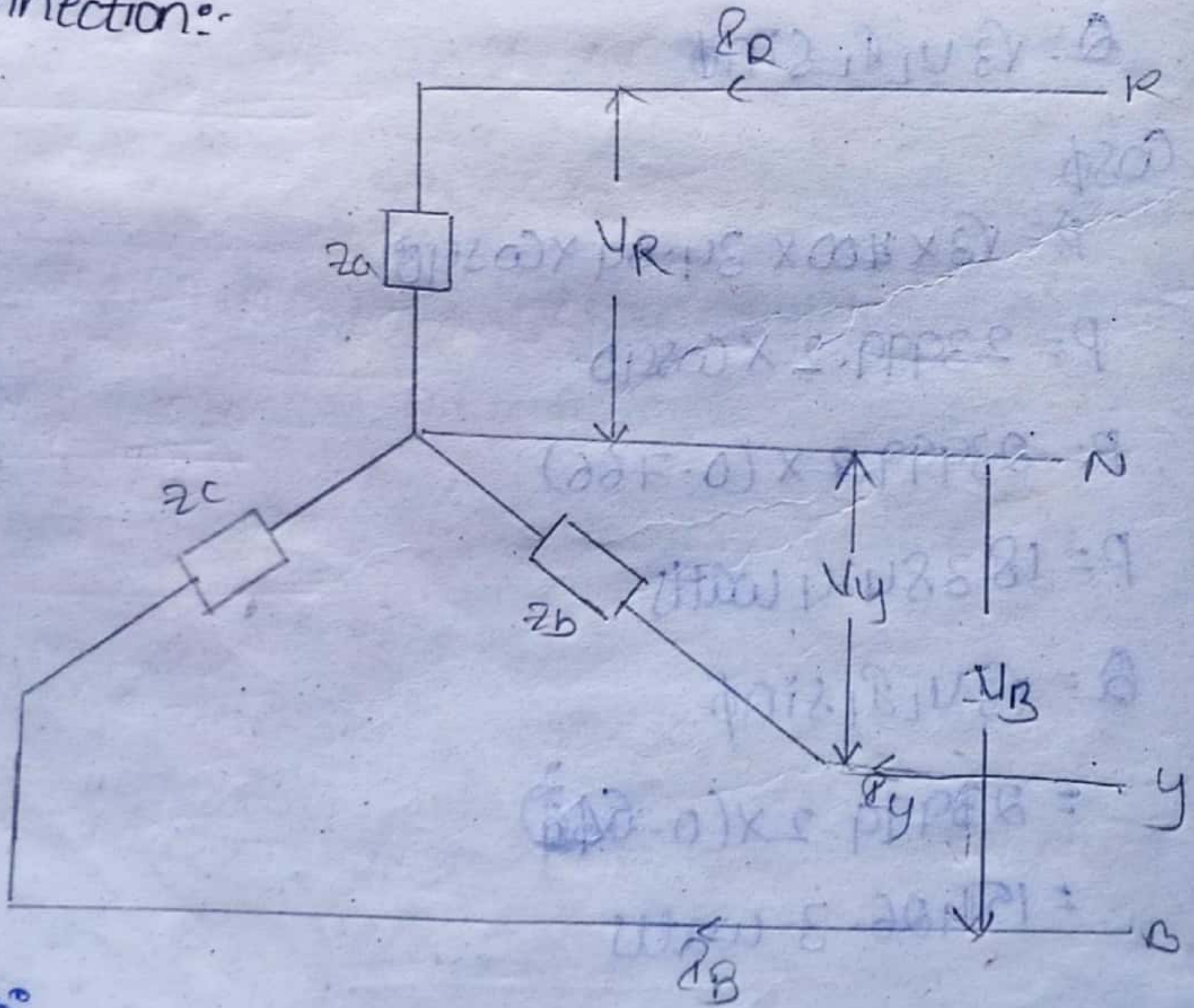

$$V_R = V_{ph} \angle 0^\circ$$

$$V_Y = V_{ph} \angle -120^\circ$$

$$V_B = V_{ph} \angle -240^\circ$$


$$\bar{I}_R = \frac{V_R}{Z_a} = \frac{V_{ph} \angle 0^\circ}{Z_a}$$

$$\bar{I}_Y = \frac{V_Y}{Z_b} = \frac{V_{ph} \angle -120^\circ}{Z_b}$$

$$\bar{I}_B = \frac{V_B}{Z_c} = \frac{V_{ph} \angle -240^\circ}{Z_c}$$

$$\bar{I}_N = -[\bar{I}_R + \bar{I}_Y + \bar{I}_B]$$

Delta connection:-

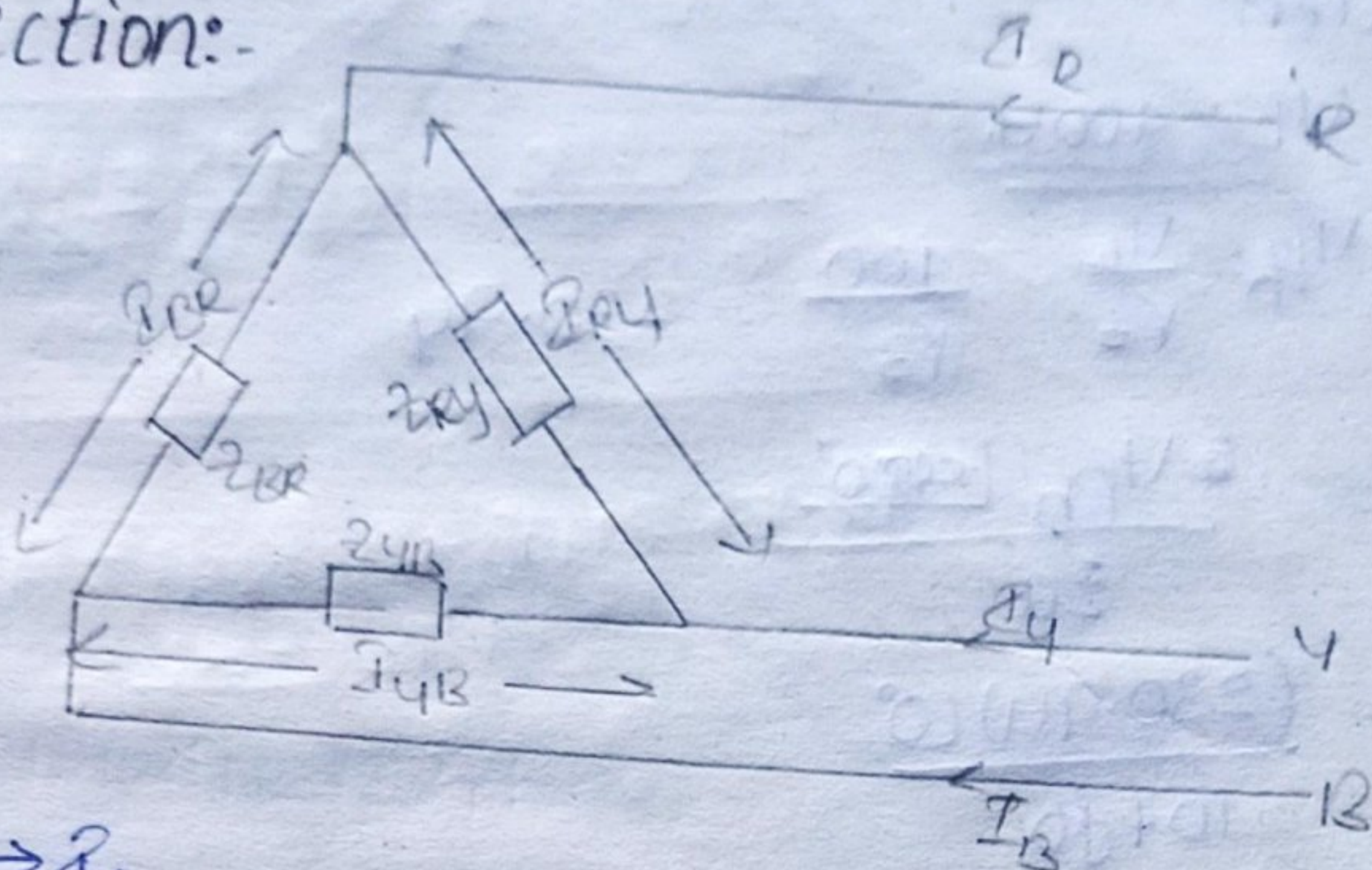

$$\bar{I}_R, \bar{I}_Y, \bar{I}_B \rightarrow \bar{I}_L$$

$$\bar{I}_{RY}, \bar{I}_{YB}, \bar{I}_{BR} \rightarrow \bar{I}_{ph}$$

$$V_{RY} = V_{ph} \angle 0^\circ$$

$$V_{YB} = V_{ph} \angle -120^\circ$$

$$V_{BR} = V_{ph} \angle -240^\circ$$

$$\bar{I}_{RY} = \frac{V_{RY}}{Z_a} = \frac{V_{ph} \angle 0^\circ}{Z_a}$$

$$\bar{I}_{YB} = \frac{V_{YB}}{Z_b} = \frac{V_{ph} \angle -120^\circ}{Z_b}$$

$$\bar{I}_{BR} = \frac{V_{BR}}{Z_c} = \frac{V_{ph} \angle -240^\circ}{Z_c}$$

Prob: A 3-phase 400 volts 4-wire system has a star connected load with $Z_a = (100 + j0) \Omega$, $Z_b = (15 + j10) \Omega$, $Z_c = (0 + j5) \Omega$. Find the line currents and current through Neutral point. draw the phasor diagram

$\bar{I}_R, \bar{I}_Y, \bar{I}_B$ are phase currents

In star connection

$$\text{phase current } \bar{I}_R = \frac{V_R \angle 0^\circ}{Z_a}$$

$$\vec{I}_y = \frac{U_y \angle -120^\circ}{z_b} = \frac{U_{ph} \angle -120^\circ}{z_b}$$

$$\vec{I}_B = \frac{U_B \angle -240^\circ}{z_c} = \frac{U_{ph} \angle -240^\circ}{z_c}$$

In star connection

$$\vec{I}_p = \vec{I}_L$$

Given

$$U_L = 400V$$

$$U_{ph} = \frac{U_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94$$

$$\vec{I}_R = \frac{U_{ph} \angle 0^\circ}{z_a}$$

$$= \frac{(230.94) \angle 0^\circ}{10 + j0}$$

$$= 23.09 + 0j$$

$$= 23.09 \angle 0^\circ$$

$$\vec{I}_y = \frac{U_{ph} \angle -120^\circ}{z_b}$$

$$= \frac{(230.94) \angle -120^\circ}{(15 + j10)}$$

$$= 23.09 + 10j \quad 12.535 + 1.06j = 12.75 \angle -153.69^\circ$$

$$\vec{I}_B = \frac{U_{ph} \angle -240^\circ}{z_c}$$

$$= \frac{(230.94) \angle -240^\circ}{(5 + j5)}$$


$$= 43.66 - 15.04j = 46 \angle 30^\circ$$

In star connection phase currents = line currents

$$\therefore \vec{I}_R = \vec{I}_L = \vec{I}_{ph} = 23.09 \angle 0^\circ$$

$$\vec{I}_y = \vec{I}_L = \vec{I}_{ph} = 12.75 \angle -153.69^\circ$$
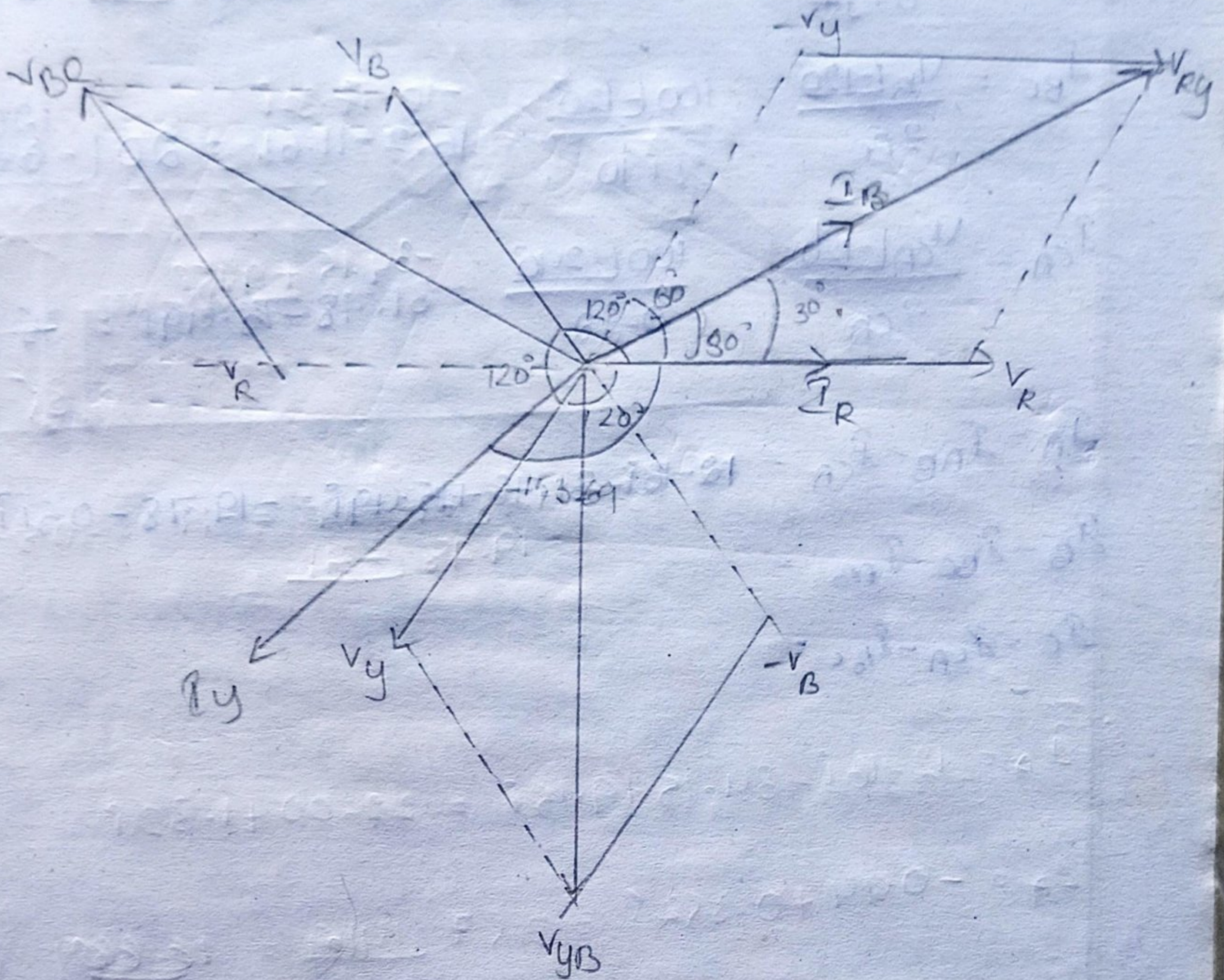
$$\vec{I}_B = \vec{I}_L = \vec{I}_{ph} = 46 \angle 30^\circ$$



pb For the network shown in figure. calculate the line currents and power consum. if the phase sequence is a b c

$$V_L = 100V$$

$$Z_{AB} = 3 + j4$$

$$Z_{BC} = 5 + j0$$

$$Z_{CA} = 2 - j2$$

In delta $V_L = V_{ph}$


$$I_L = \sqrt{3} I_{ph}$$

$$I_L = ?$$

$$I_A = I_{AB} - I_{CA}$$

$$I_B = I_{BC} - I_{AB}$$

$$I_C = I_{CA} - I_{BC}$$

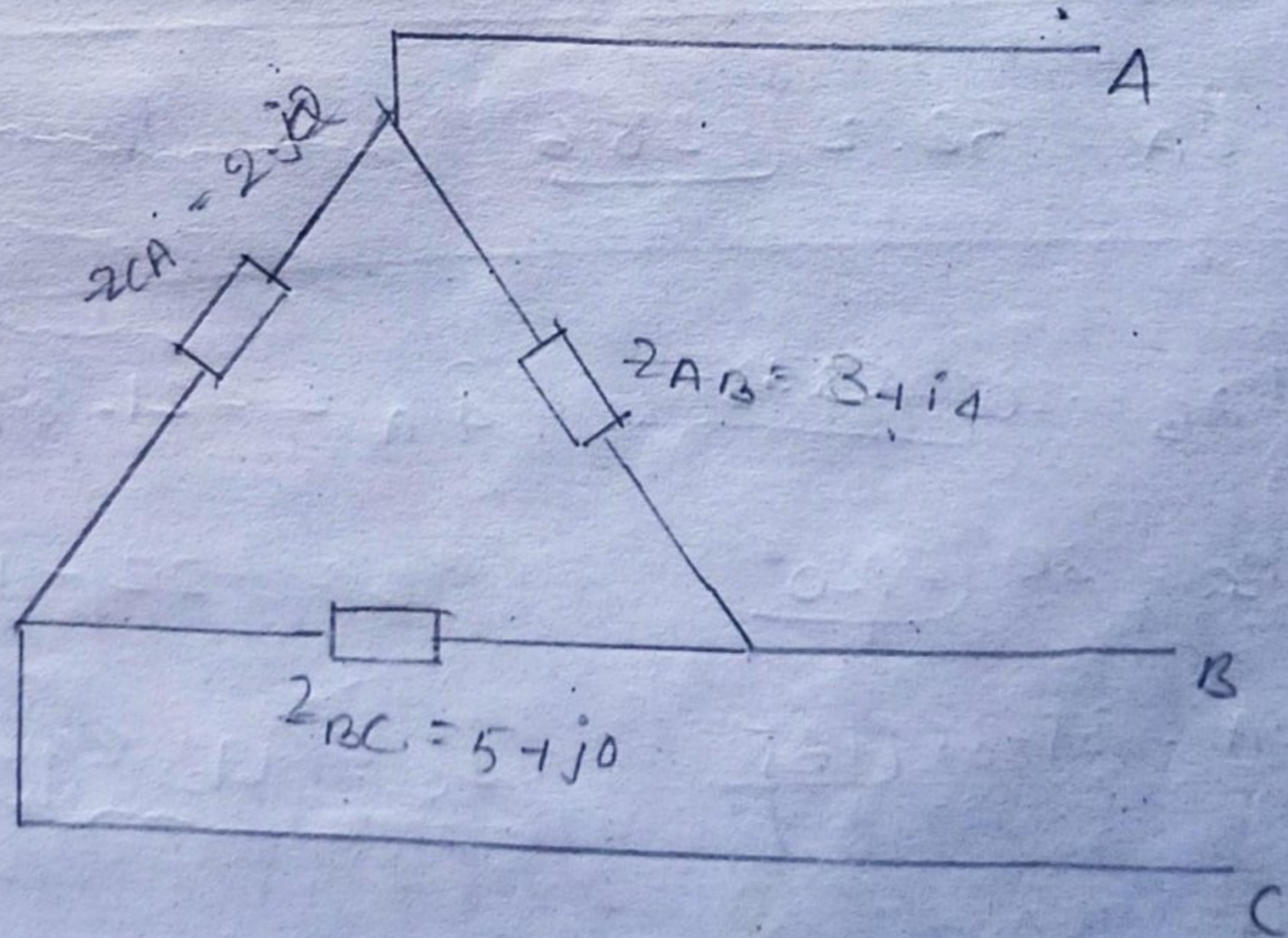

$$I_{AB} = \frac{V_{AB} \angle 0^\circ}{Z_{AB}}$$

$$= \frac{100 \angle 0^\circ}{3+j4}$$

$$= \frac{12-16j}{33-33+4j} = 33-33+4j = 33-33+4j = 20 \angle -53.1^\circ$$

$$I_{BC} = \frac{V_{BC} \angle -120^\circ}{Z_{BC}}$$

$$= \frac{100 \angle -120^\circ}{5+j0}$$

$$= \frac{-10-17.32j}{16.2-11.61j}$$

$$= 16.2-11.61j = 20 \angle -41.7^\circ$$

$$I_{CA} = \frac{V_{CA} \angle -240^\circ}{Z_{CA}}$$

$$= \frac{100 \angle -240^\circ}{2-j2}$$

$$= \frac{-34.15+9.15j}{31.78-15.49j}$$

$$= 31.78-15.49j = 35 \angle -28.6^\circ$$

$$35 \angle -28.6^\circ$$

$$I_A = I_{AB} - I_{CA} = 12-16j - 31.78+15.49j = 19.78-0.51j = 19.78 \angle -1.5^\circ$$

$$I_B = I_{BC} - I_{AB} =$$

$$= 16.2-11.61j - 12+16j = 4.2+4.39j = 4.78 \angle 46.1^\circ$$

$$I_C = I_{CA} - I_{BC} =$$

$$I_A = 12-16j - 34.15+9.15j = 22.00+1.32j$$

$$I_A = -0.44 + 0.3525j = 0.57 \angle 141.9^\circ = 0.57 \angle -28.6^\circ$$

$$I_B = 0.39 - 0.919j = 1 \angle -66.9^\circ$$

$$I_C = 0.45 - 1.69j = 1.75 \angle -75^\circ$$

$$I_A = 52.2 \angle -28.6^\circ$$


$$I_{AB} = 20 \angle -53.13^\circ = I_A = -21.89 - j26.64$$

$$I_{BC} = 20 \angle -120^\circ = I_B = -22 - j13.2$$

$$I_{CA} = 35 \angle -165^\circ = I_C = 43.89 + j27.36$$

$$S = -2364.19 + j2565.38$$


Star to delta transformation:-

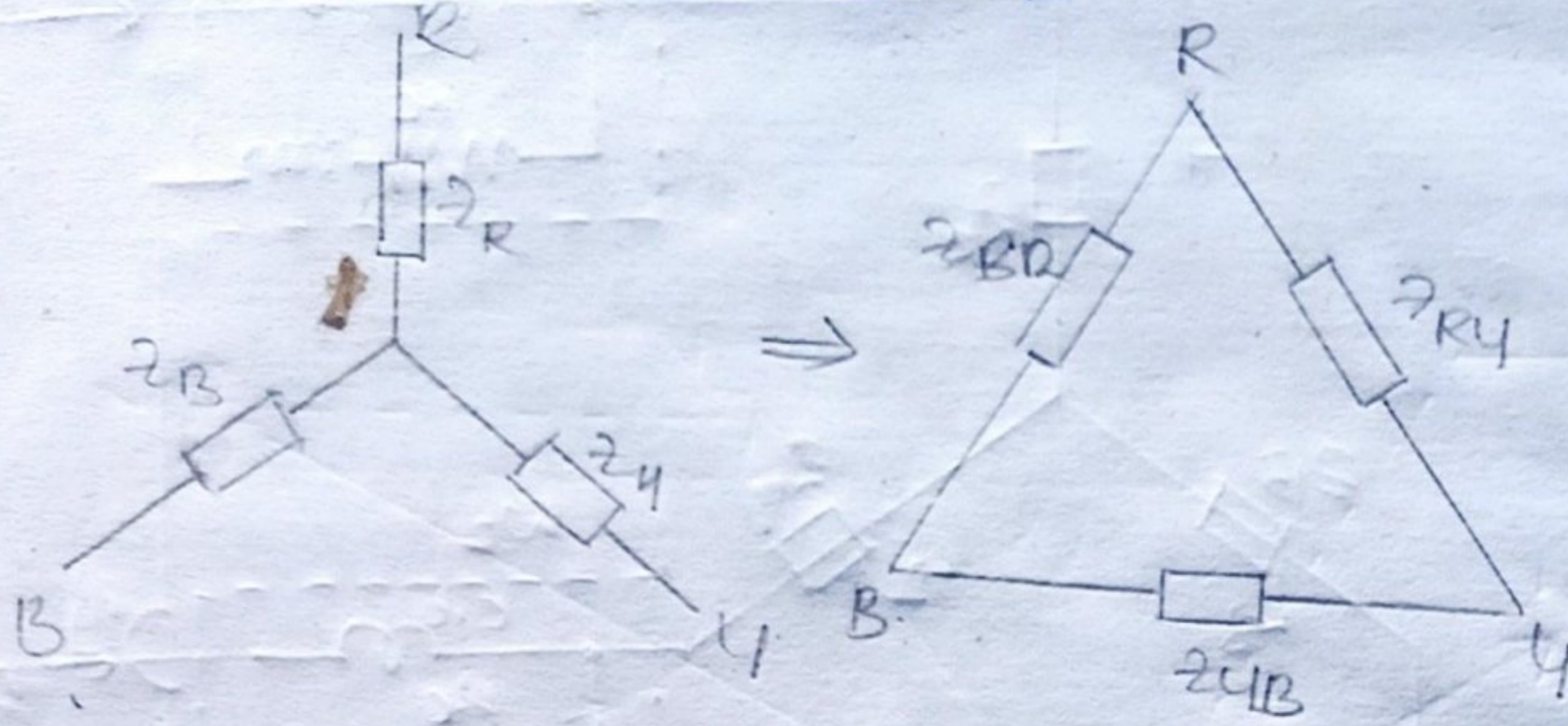


$$z_{RY} = z_R + z_Y + \frac{z_R z_Y}{z_B}$$

$$z_{YB} = z_Y + z_B + \frac{z_Y z_B}{z_R}$$
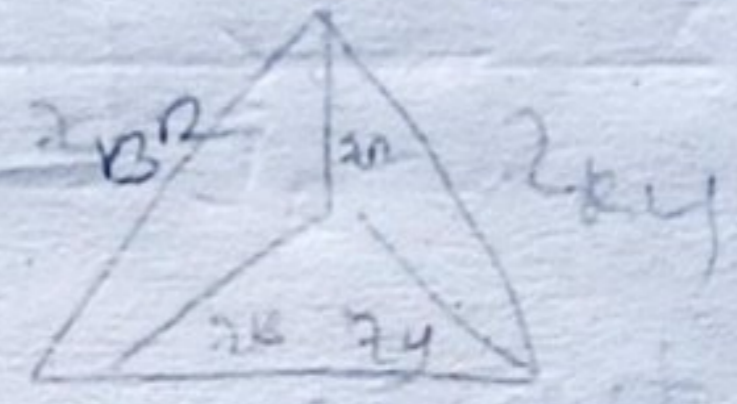
$$z_{BR} = z_B + z_R + \frac{z_B z_R}{z_Y}$$



Delta to star transformation

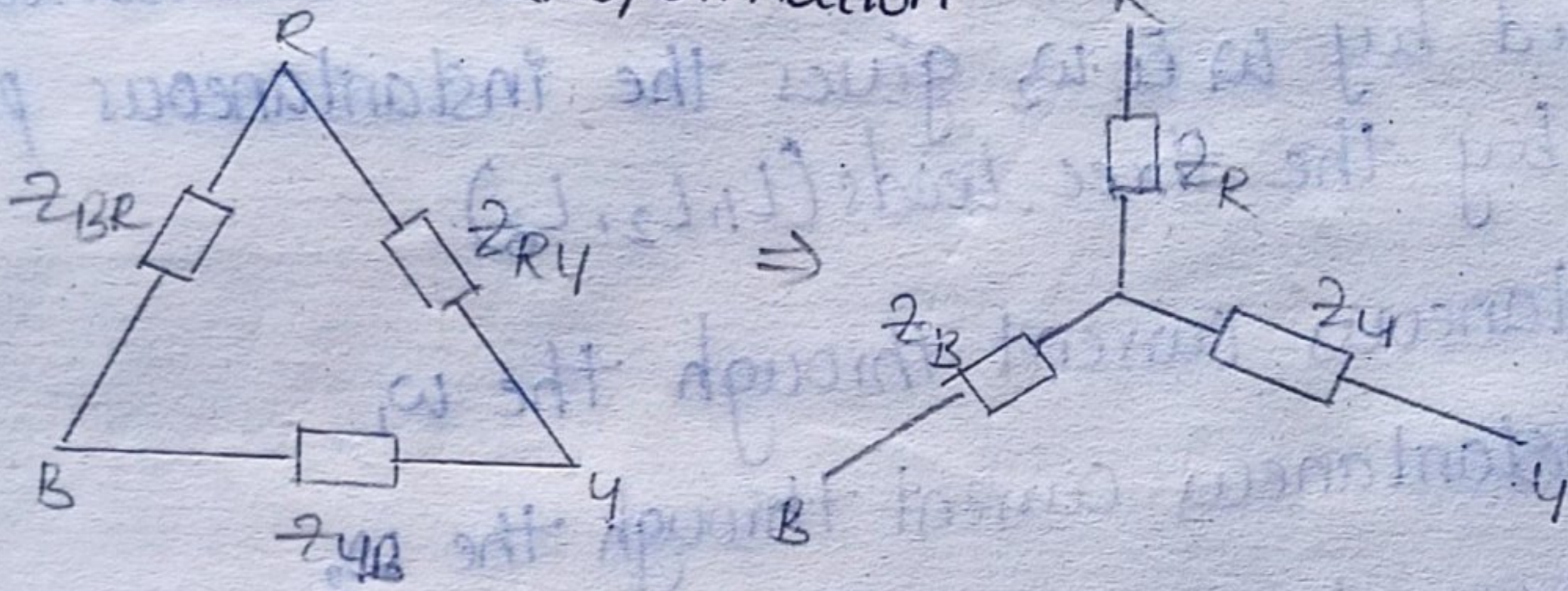


$$z_R = \frac{z_{RY} z_{BR}}{z_{RY} + z_{BR} + z_{YB}}$$

$$z_Y = \frac{z_{RY} z_{YB}}{z_{RY} + z_{YB} + z_{BR}}$$

$$z_B = \frac{z_{YB} z_{BR}}{z_{YB} + z_{BR} + z_{RY}}$$

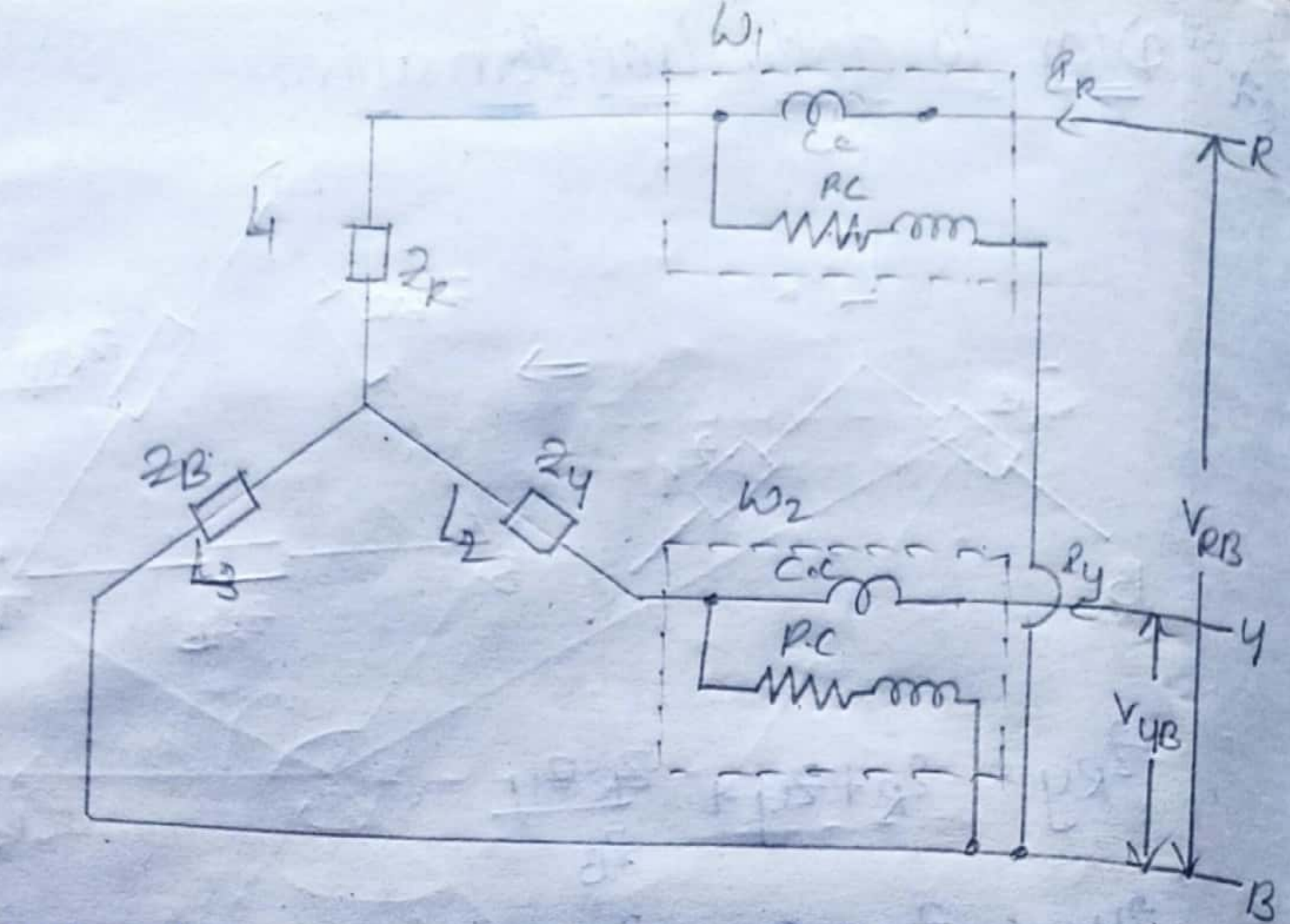2 Wattmeter method for measurement of 3-φ power unbalanced load:-



The two wattmeters are inserted any two lines and pressure coil of each meter is join to the third line in which the current coil will not included

It can prove that the sum of the instantaneous power indicated by w_1 & w_2 gives the instantaneous power absorb by the three loads (L_1, L_2, L_3)

i_R = Instantaneous current through the w_1

i_Y = Instantaneous current through the w_2

V_{RB} = Instantaneous potential difference across w_1

V_{YB} = Instantaneous potential difference across w_2

Instantaneous power measured by $w_1 = V_{RB} i_R$

$$w_1 = (V_R - V_B) i_R$$

Instantaneous power measured by $w_2 = V_{YB} i_Y$

$$w_2 = (V_Y - V_B) i_Y$$

Total power measured by two wattmeters

$$= w_1 + w_2$$

$$= V_R i_R - V_B i_R + V_Y i_Y - V_B i_Y$$

$$= V_R i_R + V_Y i_Y - (V_B (i_R + i_Y))$$

$$(\because i_R + i_Y + i_B = 0)$$

$$= V_R i_R + V_Y i_Y - V_B (-i_B)$$

$$= U_R \hat{r}_R + U_Y \hat{r}_Y + U_B \hat{r}_B$$


DC TRANSIENTSTransients:

In any transmission line the voltage is fluctuating or imbalanced due to short circuiting or if any fault or any imbalances. is called Transients Voltage

Transients is calculated for circuit elements
 i, R-L circuit ii, R-C circuit iii, R-L-C circuit

DC response of an R-L circuit:

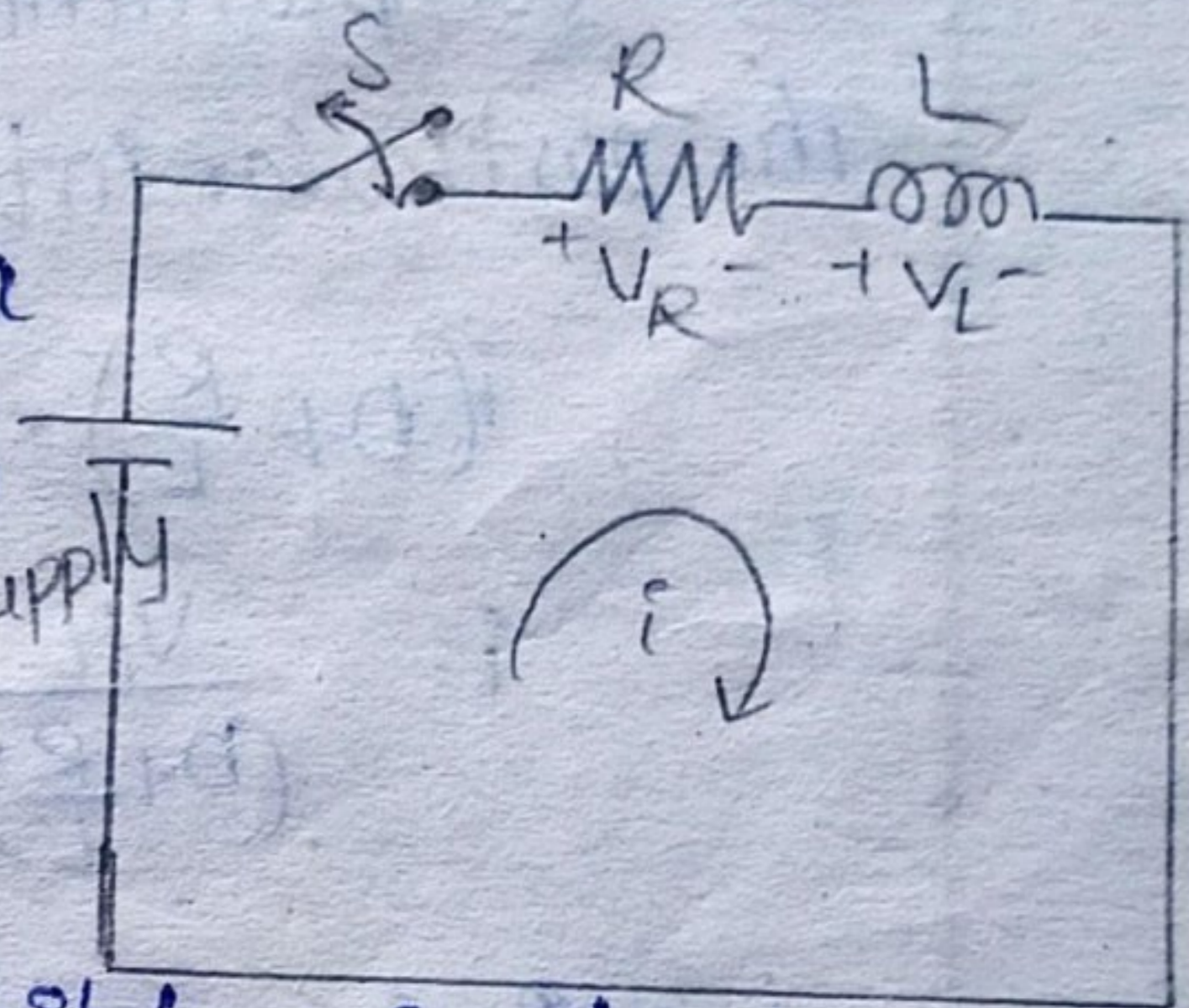Consider a circuit consisting of a resistance & inductance is shown in figure.



Initially the inductor in the circuit is uncharged. When the switch S is closed we can find the complete solution for the current.

apply KVL in above circuit

$$V = V_R + V_L$$

$$V = iR + L \frac{di}{dt}$$

- * The above eqn i is the current flowing through the circuit & V is the applied constant voltage.
- * The applied voltage V is applied to the circuit when the switch S is closed.
- * The above eqn is linear differential of a first order.

$$V = iR + L \frac{di}{dt}$$

$$\frac{V}{L} = \frac{iR}{L} + \frac{di}{dt}$$

$$\frac{di}{dt} + i \frac{R}{L} = \frac{V}{L}$$

The complementary function is

$$\frac{di}{dt} = 0 \text{ as operator}$$

$$Di + i \frac{R}{L} = \frac{V}{L}$$

$$i(D + \frac{R}{L}) = \frac{V}{L}$$

Solution

the complementary function C.F = ke^{Dt}

$$\text{the C.F } i(D + \frac{R}{L}) = 0$$

$$D + \frac{R}{L} = 0$$

$$D = -\frac{R}{L}$$

The complementary function C.F = $ke^{-\frac{R}{L}t}$

The particular integral

$$i(D + \frac{R}{L}) = \frac{V}{L}$$

$$i = \frac{V/L}{(D + \frac{R}{L})}$$

$$P.I = \frac{V}{L} \cdot \frac{1}{(D + \frac{R}{L})}$$

$$i = \frac{V}{L} \cdot \frac{1}{\frac{R}{L}(1 + \frac{D}{R/L})}$$

$$i = \frac{V}{R} (1 + \frac{D}{R/L})^{-1}$$

$$i = \frac{V}{R} (1)$$

$$i = \frac{V}{R}$$

The complete solution

$$i = C.F + P.I = ke^{-\frac{R}{L}t} + \frac{V}{R}$$

Because of the presence of the inductance doesn't allow the sudden change in current i.e

$$t=0; \text{ when } i=0.$$

$$0 = ke^{-\frac{R}{L}t} + \frac{V}{R}$$

$$0 = ke^0 + \frac{V}{R}$$

$$0 = k + \frac{V}{R}$$

$$k = -\frac{V}{R}$$

The complete solution / final solution is

$$i = -\frac{V}{R}e^{-\frac{R}{L}t} + \frac{V}{R} = \frac{V}{R} - \frac{V}{R}e^{-\frac{R}{L}t}$$

$$i = \frac{V}{R}(1 - e^{-\frac{R}{L}t})$$

The above equation consisting of two parts.

i. The steady part is $\frac{V}{R}$

ii. The transient part is $\frac{V}{R}e^{-\frac{R}{L}t}$.

voltage across the resistor $V_R = iR$

$$V_R = \frac{V}{R}(1 - e^{-\frac{R}{L}t})R$$

$$V_R = V(1 - e^{-\frac{R}{L}t})$$

voltage across the inductor $V_L = L \frac{di}{dt}$

$$V_L = L \frac{d}{dt} \left(\frac{V}{R}(1 - e^{-\frac{R}{L}t}) \right)$$

$$V_L = L \frac{V}{R} \frac{d}{dt} (1 - e^{-\frac{R}{L}t})$$

$$= \frac{LV}{R} (-e^{-\frac{R}{L}t}) \left(-\frac{R}{L} \right)$$

$$= Ve^{-\frac{R}{L}t}$$

power flowing through resistor

$$P_R = V_R i$$

$$= V(1 - e^{-\frac{R}{L}t}) \left[\frac{V}{R}(1 - e^{-\frac{R}{L}t}) \right]$$

$$= \frac{V^2}{R} (1 - e^{-\frac{R}{L}t})^2$$

power flowing through inductor

$$P_L = V_L i$$

$$= V e^{(-\frac{R}{L})t} \left[\frac{V}{R} (1 - e^{(-\frac{R}{L})t}) \right]$$

$$= \frac{V^2}{R} \left[e^{(-\frac{R}{L})t} (1 - e^{(-\frac{R}{L})t}) \right]$$

9-09-22 that $\frac{L}{R}$ is called time constant and it is denoted by τ

$\tau = \frac{L}{R}$ is known time constant of the circuit and is defined as the interval after which current or voltage changes 63.2% of its total change

At $t=0$

$$i = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$= \frac{V}{R} (1 - 1)$$

$$= 0$$

$$V_R = V (1 - e^{-\frac{R}{L}t})$$

$$= V (1 - 1)$$

$$= 0$$

$$V_L = V (e^{-\frac{R}{L}t})$$

$$= V (1)$$

$$= V$$

L acts as open circuit

At $t=\infty$

$$i = \frac{V}{R} (1 - e^{-\frac{R}{L}\infty})$$

$$= \frac{V}{R}$$

$$V_R = V (1 - e^{-\frac{R}{L}\infty})$$

$$= V$$

$(\frac{R}{L})\infty$



$$V_L = V e^{-\infty}$$

$$= 0$$

it acts as short circuit

At $t = \tau = \frac{L}{R}$
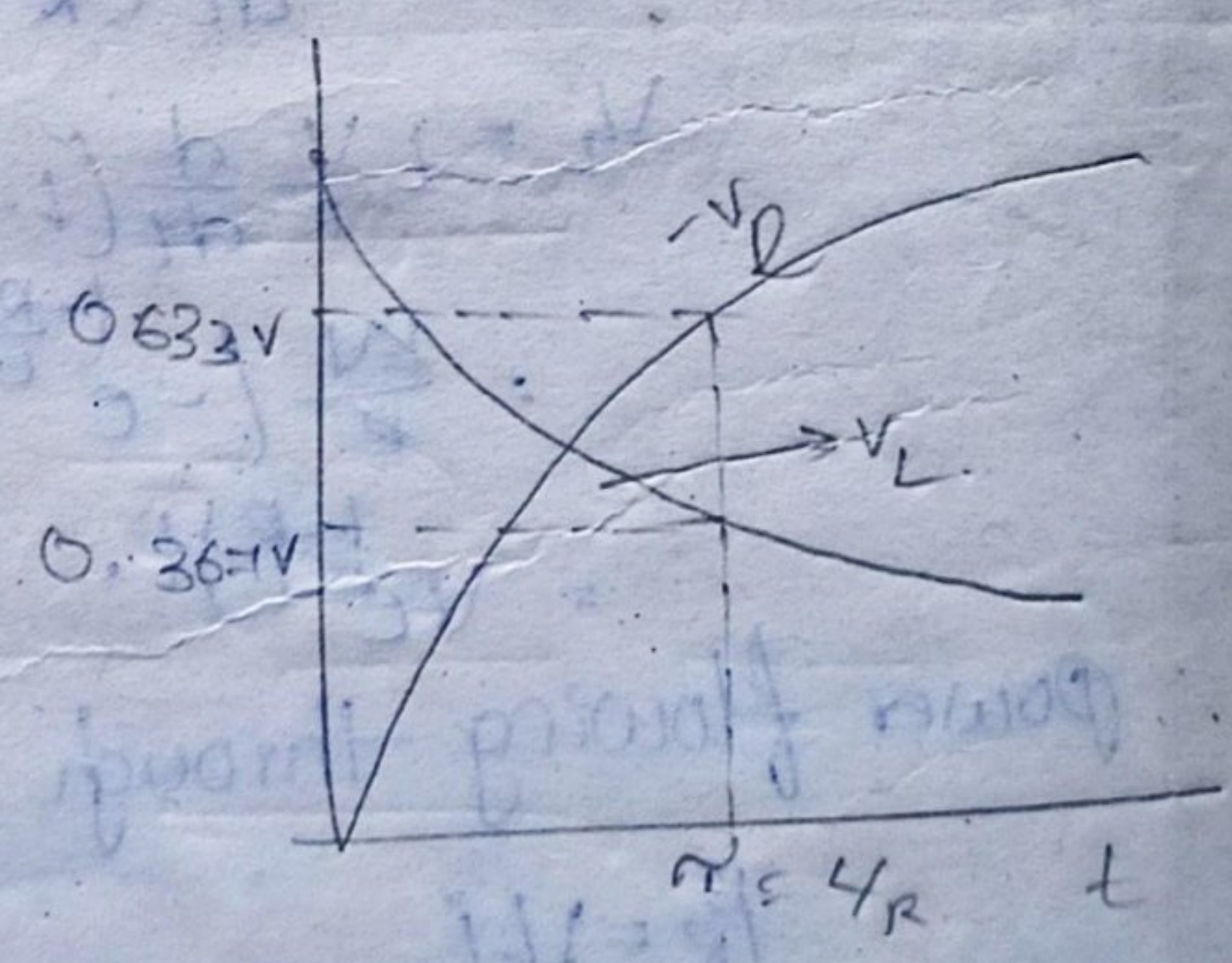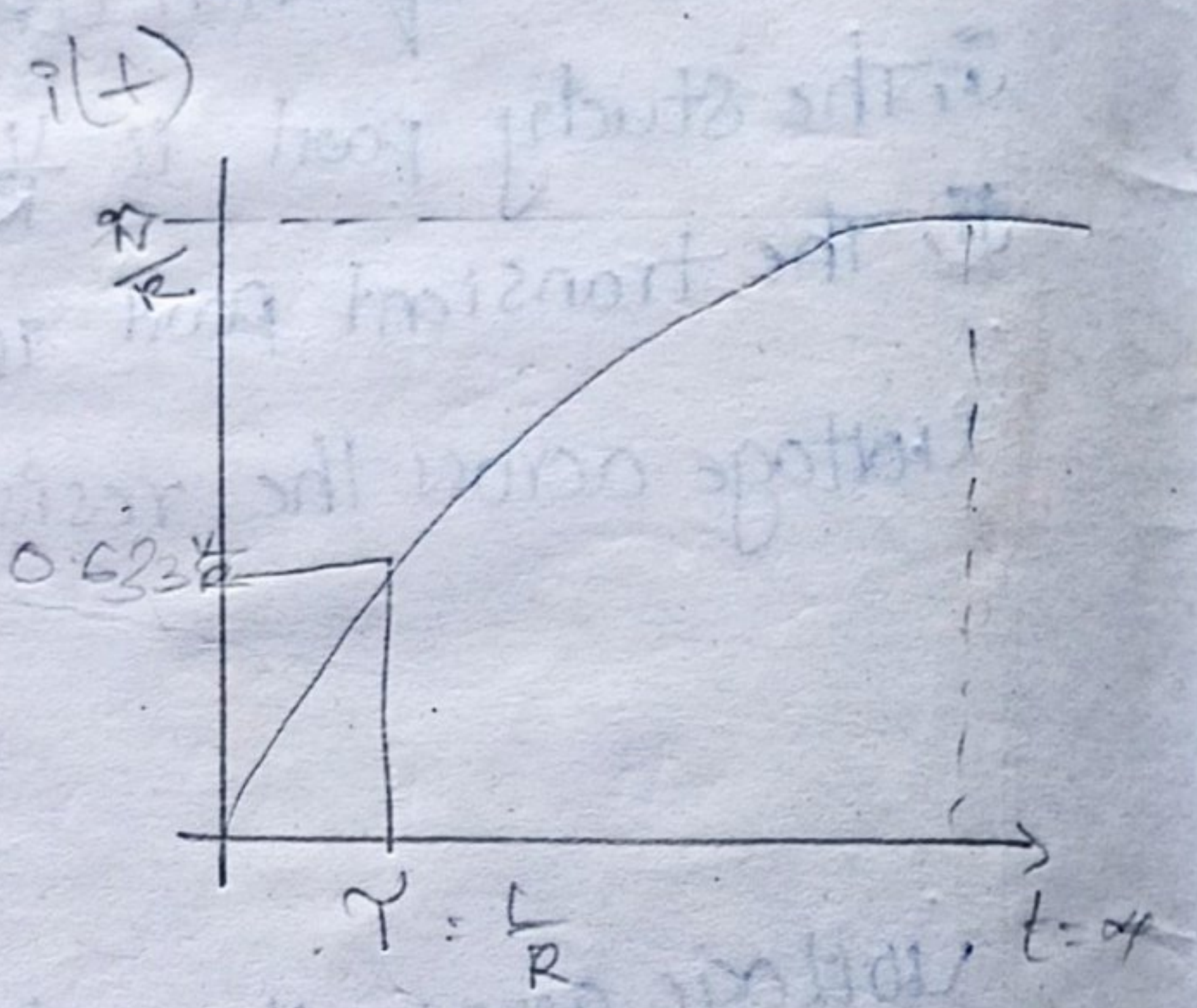
$$i = \frac{V}{R} (1 - e^{-\frac{R}{L} \frac{L}{R}})$$



$$i = \frac{V}{R} (1 - e^{-t}) = \frac{V}{R} (1 - \frac{1}{e})$$

$$i = \frac{V}{R} (1 - 0.367)$$

$$i = \frac{V}{R} (0.633)$$

$$V_R = V (1 - e^{-\frac{R}{L}t})$$


$$= V (1 - e^{-1})$$

$$V (0.633)$$

$$V_L = V (e^{-\frac{R}{L}t})$$

$$= V (e^{-1})$$


$$= V (0.367)$$

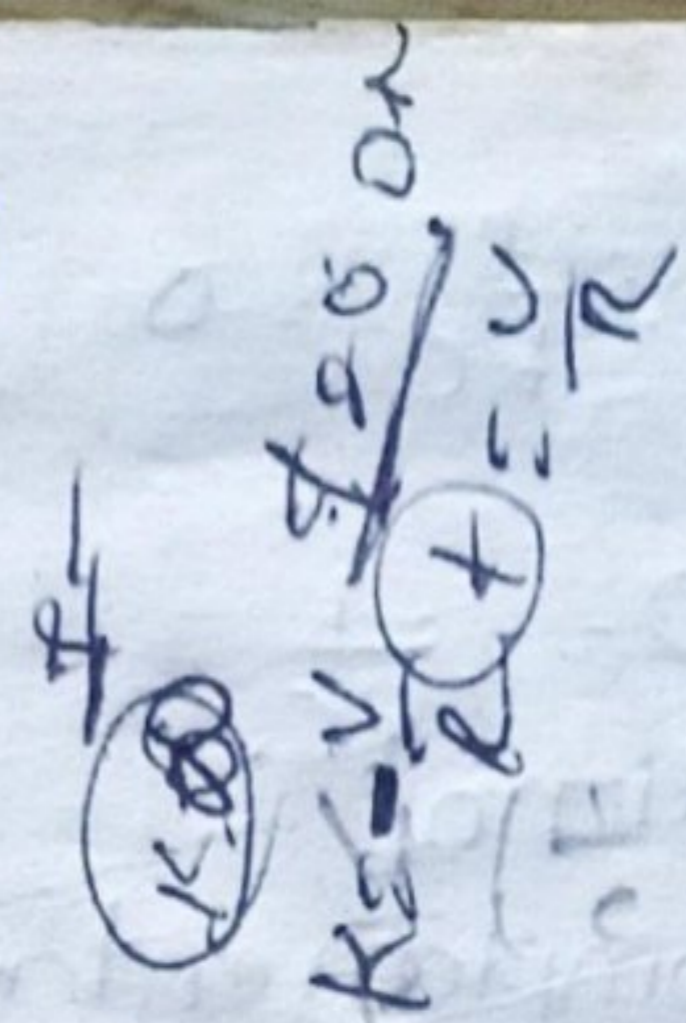

D.C. Response of a R-C Circuit:

Consider a circuit consisting of resistance ~~and~~ ^{in series} with capacitance as shown in figure

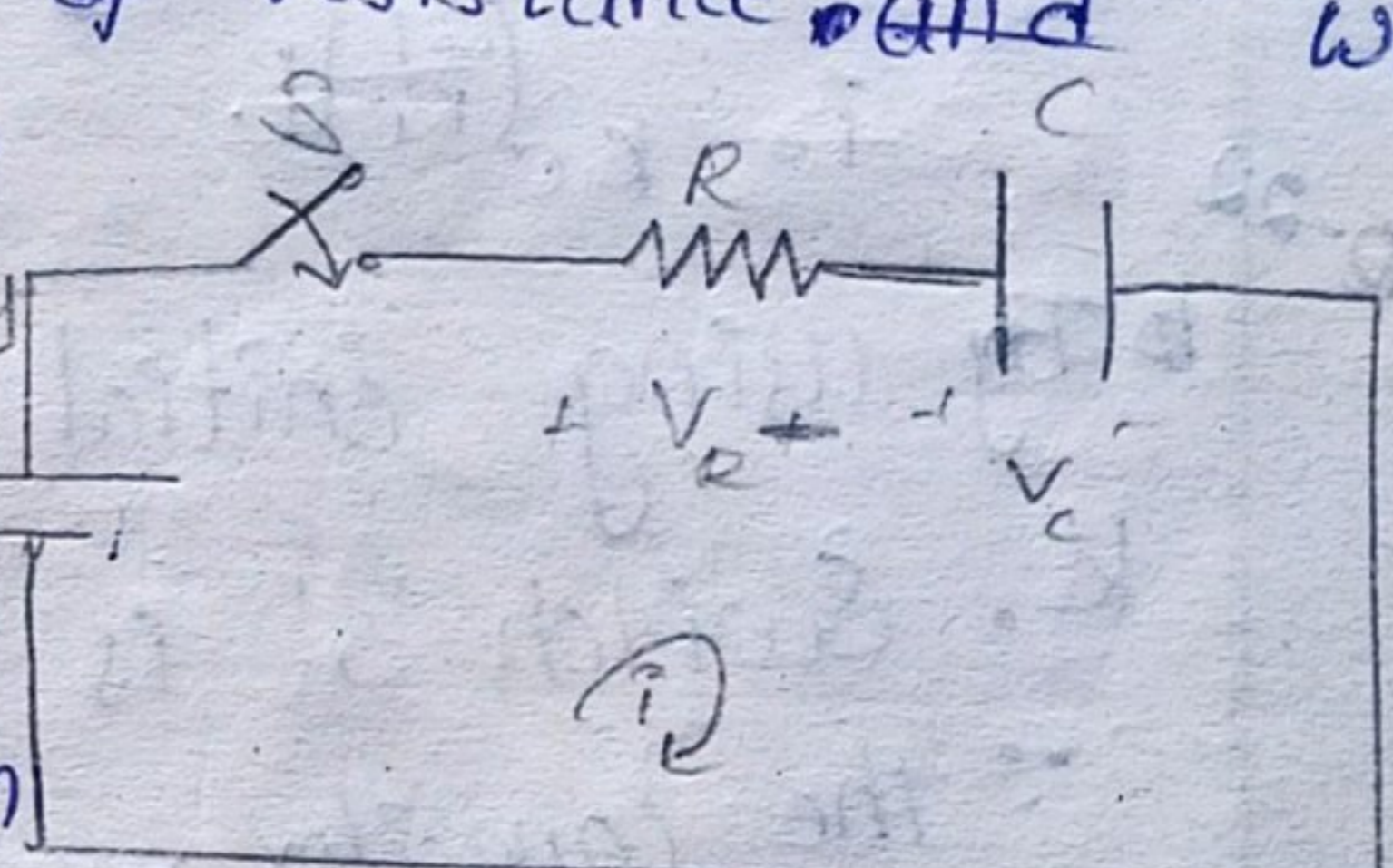When the switch S is closed at $t=0$, we can determine the complete solution for the current applying KVL



$$V = V_R + V_C$$

$$V = iR + \frac{1}{C} \int i dt$$

Differentiating above equation

$$0 = R \frac{di}{dt} + \frac{1}{C} i$$

$$0 = \frac{di}{dt} + \frac{1}{RC} i$$

The complementary function C.F. is

$$0 = Di + \frac{1}{RC} i$$

$$i(D + \frac{1}{RC}) = 0$$

The C.F. = $ke^{-t/RC}$

$$i(D + \frac{1}{RC}) = 0$$

$$D + \frac{1}{RC} = 0$$

$$D = -\frac{1}{RC}$$

Solution of

The complementary function = $k e^{-\frac{1}{RC}t}$

The particular integral p.i is

$$i(D + \frac{1}{RC}) = 0$$

$$i = \frac{0}{D + \frac{1}{RC}}$$

$$i = 0$$

The Complete Solution $i = C.F + p.i$

$$i = k e^{-\frac{1}{RC}t} + 0$$

$$i = k e^{-\left(\frac{1}{RC}\right)t}$$

10-10-22

By using initial condition we find the value of k . Switch 'S' is closed at $t=0$.

\therefore The capacitor ~~never~~ never allows the sudden changes in voltage. it will act as a short circuit at $t=0+$

At $t=0+$

$$i = \frac{V}{R}$$

$$i = k e^{-\left(\frac{1}{RC}\right)t}$$

$$\frac{V}{R} = k e^{-\left(\frac{1}{RC}\right)(0)}$$


$$\boxed{\frac{V}{R} = k}$$

The final solution is

$$i = \frac{V}{R} e^{-\left(\frac{1}{RC}\right)t}$$

Voltage across the resistance

$$V_R = iR$$

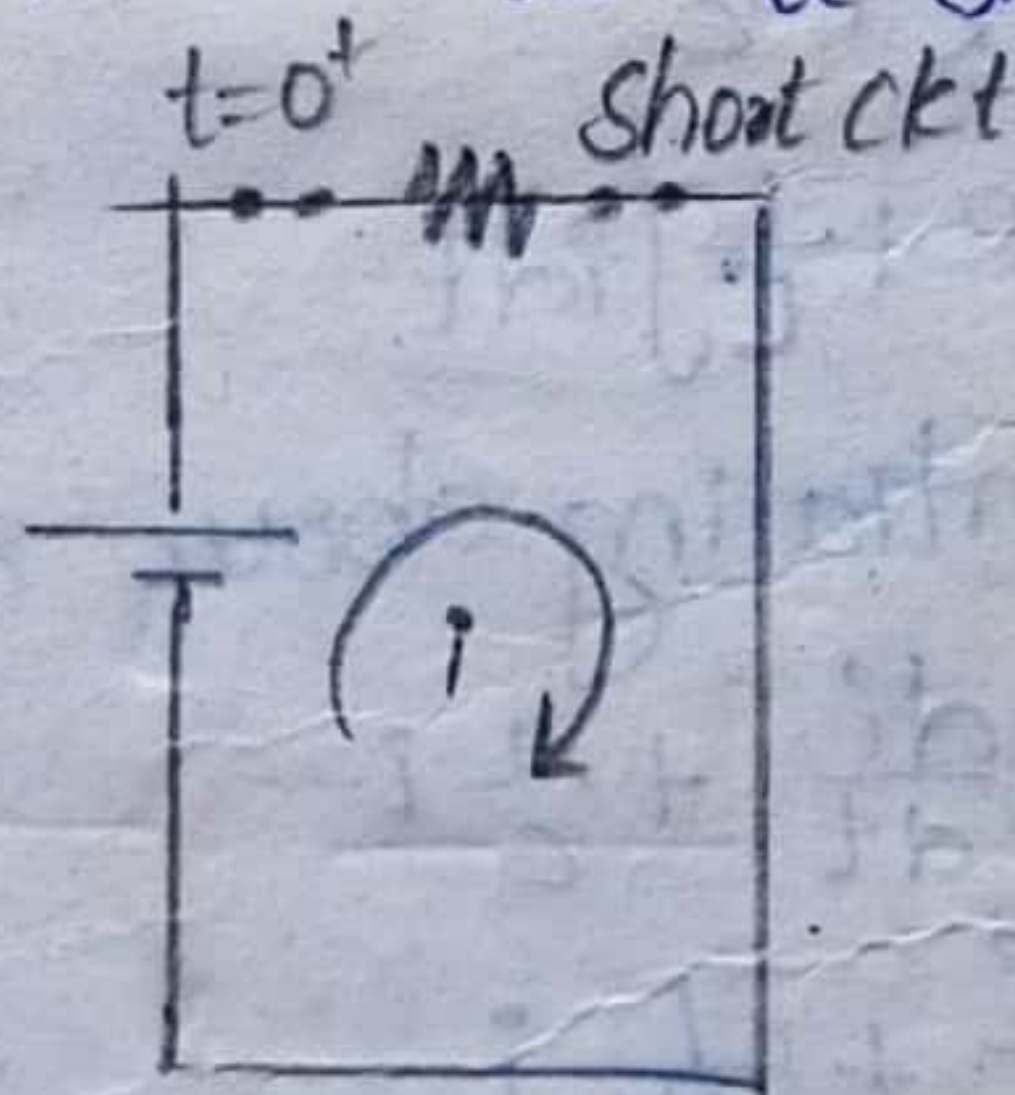

$$V_R = \frac{V}{R} e^{(-\frac{1}{RC})t} R \quad \text{at } t=0.$$

$$V_R = V e^{(-\frac{1}{RC})t}$$

$$V_R = V e^{(-\frac{1}{RC})0}$$

$$V_R = V$$

voltage across capacitor

$$V_C = \frac{1}{C} \int I dt$$

$$V_C = \frac{1}{C} \int \frac{V}{R} e^{(-\frac{1}{RC})t} dt$$

$$V_C = \frac{V}{CR} \int e^{(-\frac{1}{RC})t} dt$$

$$V_C = \frac{V}{CR} \frac{e^{(-\frac{1}{RC})t}}{-\frac{1}{RC}} + k$$

$$V_C = -V e^{(-\frac{1}{RC})t} + k$$

at $t=0$,

$$V_C = -V e^{(-\frac{1}{RC})0} + k$$

$$V_C = -V + k$$

at $V_C = 0$

$$0 = -V + k$$

$$\boxed{k = V}$$

At $t=0$ the voltage across the capacitor is 0
($\because V_C = 0$)

$$V_C = -V e^{(-\frac{1}{RC})t} + V$$

$$V_C = V(1 - e^{(-\frac{1}{RC})t})$$

The above equation is the final solution

power through resistor $P_R = V_R i$

$$P_R = V e^{(-\frac{1}{RC})t} \frac{V}{R} e^{(-\frac{1}{RC})t}$$

$$= \frac{V^2}{R} (e^{(-\frac{1}{RC})t})^2$$

power through capacitor:

$$P_c = V_c i$$

$$= V \left(1 - e^{-\frac{t}{RC}}\right) \frac{V}{R} e^{-\frac{t}{RC}}$$

$$= \frac{V^2}{R} \left[e^{-\frac{t}{RC}} - \left(e^{-\frac{t}{RC}}\right)^2 \right]$$

When Switch S is closed the response decays with time as shown in figure.


The quantity RC is the time constant and it denoted by τ

$\tau = RC \rightarrow$ Time constant in sec.


$$t=0 \rightarrow i = \frac{V}{R}$$

$$t=\infty \Rightarrow i=0$$
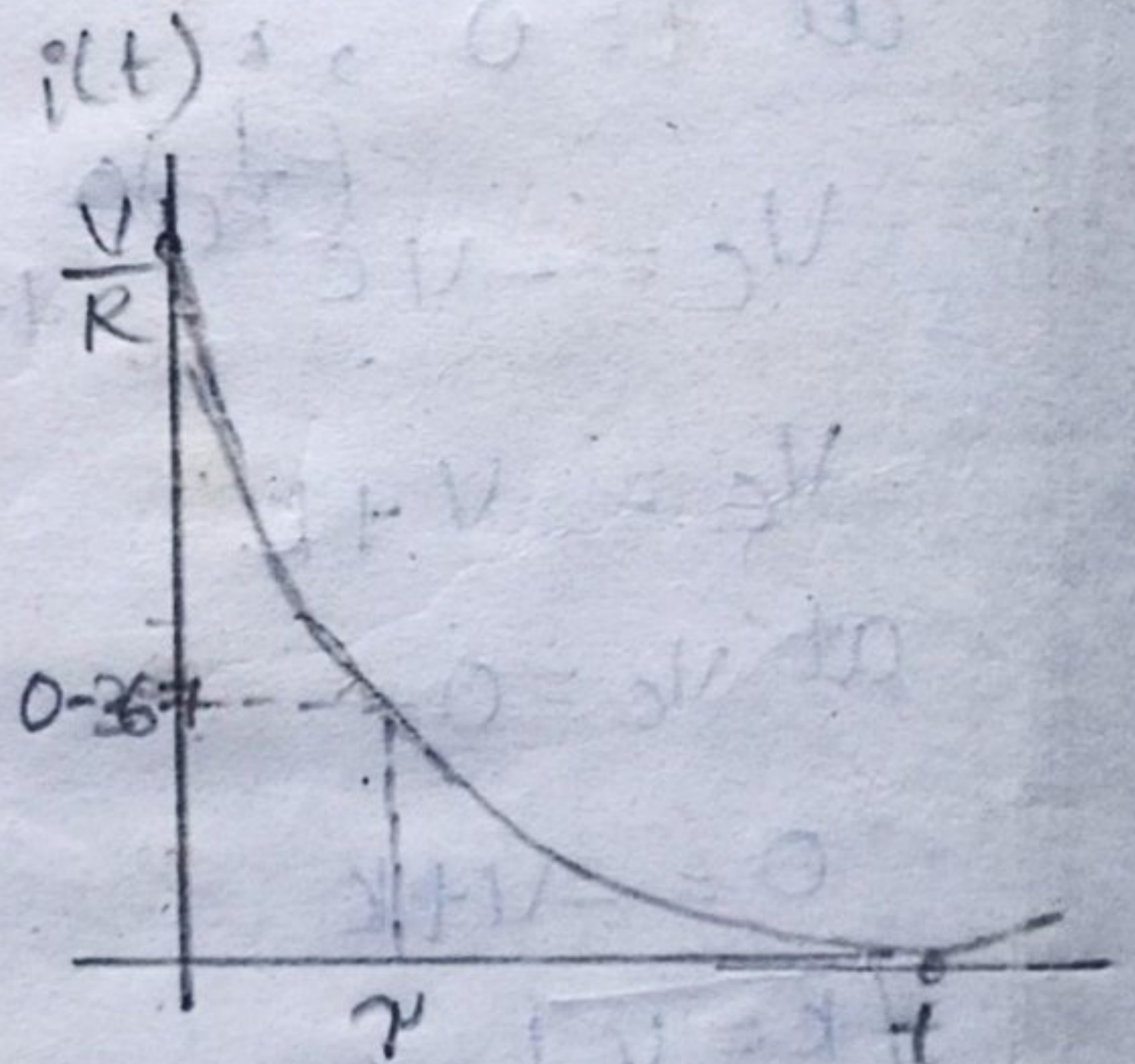
$$t = \tau \Rightarrow i = \frac{V}{R} (0.367)$$



DC Response of a R-L-C circuit:-

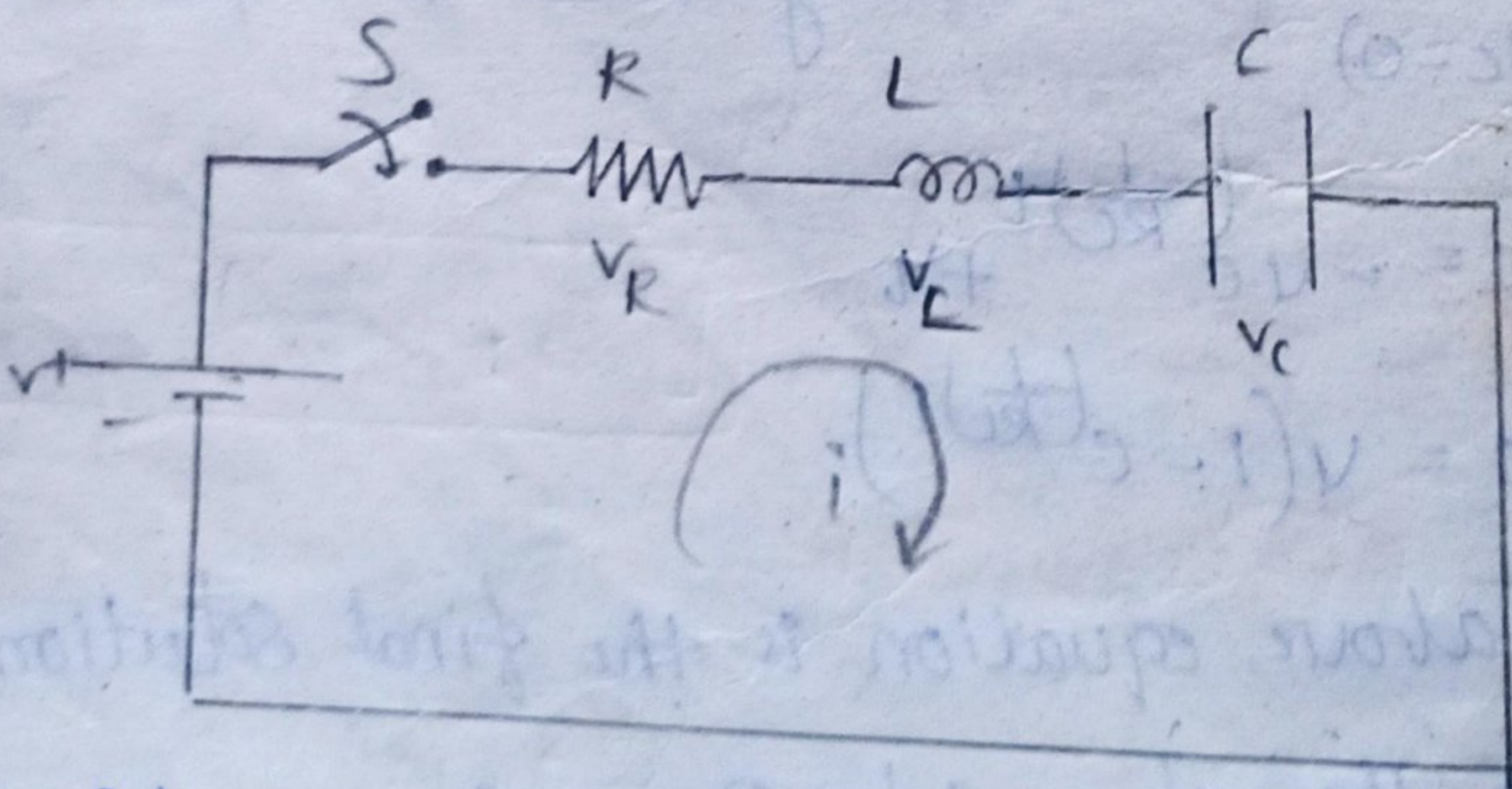

consider a circuit consisting of a resistance inductance, capacitance as shown in figure

initially the capacitor & inductor are ^{un}charge in series with resistor.

When switch S is closed at $t=0$. we can find the complete solution (of the) for the current: applying KVL in above circuit.

$$-iR - L \frac{di}{dt} - \frac{1}{C} \int i dt + V = 0$$

$$V = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

differentiating above equation for complete sol

$$0 = R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$\frac{d}{dt} \Rightarrow D$ as operator.

$$i \left[D^2 + \frac{R}{L} D + \frac{1}{LC} \right] = 0$$

The roots of the above eq is α, β

$$\alpha_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

D_1, D_2

$$\alpha_{1,2} = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - 4 \left(\frac{1}{LC}\right) \frac{1}{LC}}}{2 \left(\frac{1}{LC}\right)}$$

D_1, D_2

$$\alpha_{1,2} = \frac{\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2}$$

D_1, D_2

$$\frac{R^2}{L^2} \left(1 - \frac{4L}{RC} \right)$$

$$\alpha_{1,2} = \frac{\frac{R}{L} \pm \frac{R}{L} \sqrt{1 - \frac{4L}{RC}}}{2}$$

D_1, D_2

$$\alpha_{1,2} = \frac{R}{L} \left(\frac{-1 \pm \sqrt{1 - \frac{4L}{RC}}}{2} \right)$$

D_1, D_2

$$D_1, D_2 = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Now it is in the form $\alpha \pm \beta$

$$\alpha = \frac{-R}{2L} \quad \beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

The current response

$$i = k_1 e^{D_1 t} + k_2 e^{D_2 t}$$

Where k_1, k_2 are the constants

D_1, D_2 are the roots

Case i, when

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

At this time β is ^{positive} real and α (positive real quantity) quantity

Hence the roots are D_1, D_2 are real and unequal

$$D_1 = \alpha + \beta \quad D_2 = \alpha - \beta$$


The current solution is

$$i = k_1 e^{D_1 t} + k_2 e^{D_2 t}$$

$$i = k_1 e^{(\alpha + \beta)t} + k_2 e^{(\alpha - \beta)t}$$

$$i = k_1 e^{\alpha t} e^{\beta t} + k_2 e^{\alpha t} e^{-\beta t}$$
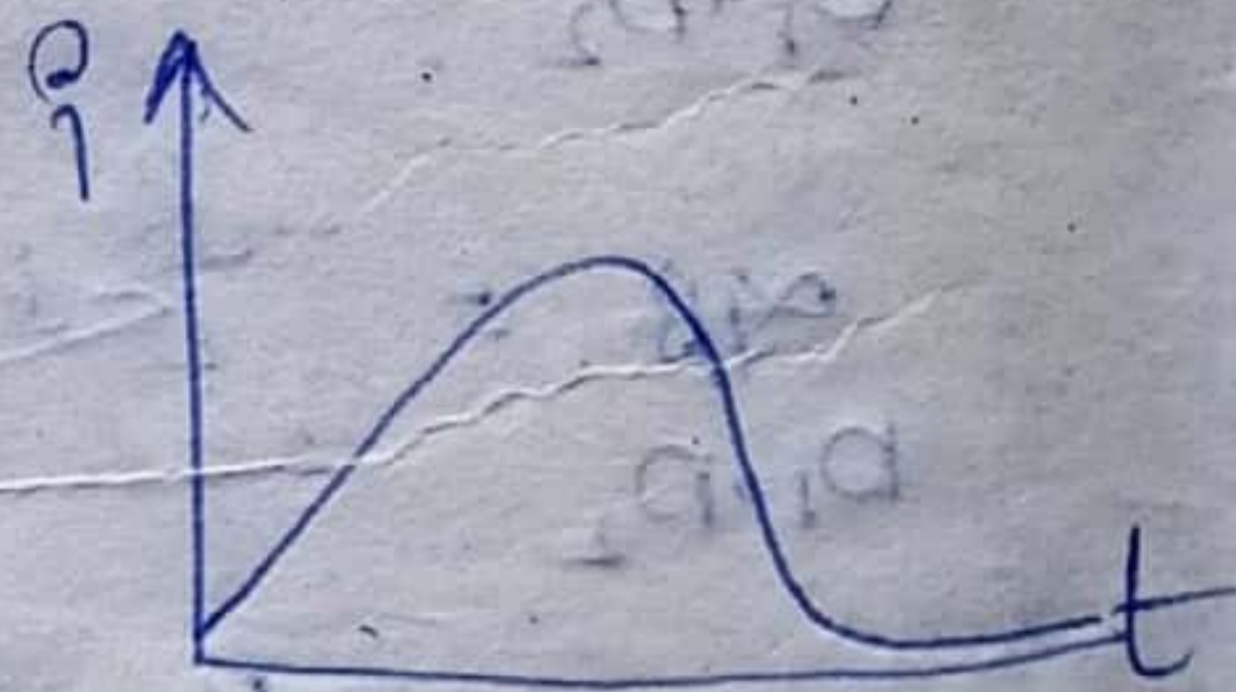
$$i = e^{\alpha t} \left[k_1 e^{\beta t} + k_2 e^{-\beta t} \right]$$



The above equation is the current solution

Case ii, when $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$

At this time β is imaginary quantity & the roots D_1, D_2 are complex conjugate


$$D_1 = \alpha + j\beta, \quad D_2 = \alpha - j\beta$$

$$i = k_1 e^{D_1 t} + k_2 e^{D_2 t}$$

$$i = k_1 e^{(\alpha + j\beta)t} + k_2 e^{(\alpha - j\beta)t}$$

$$i = k_1 e^{\alpha t} \cdot e^{j\beta t} + k_2 e^{\alpha t} \cdot e^{-j\beta t}$$
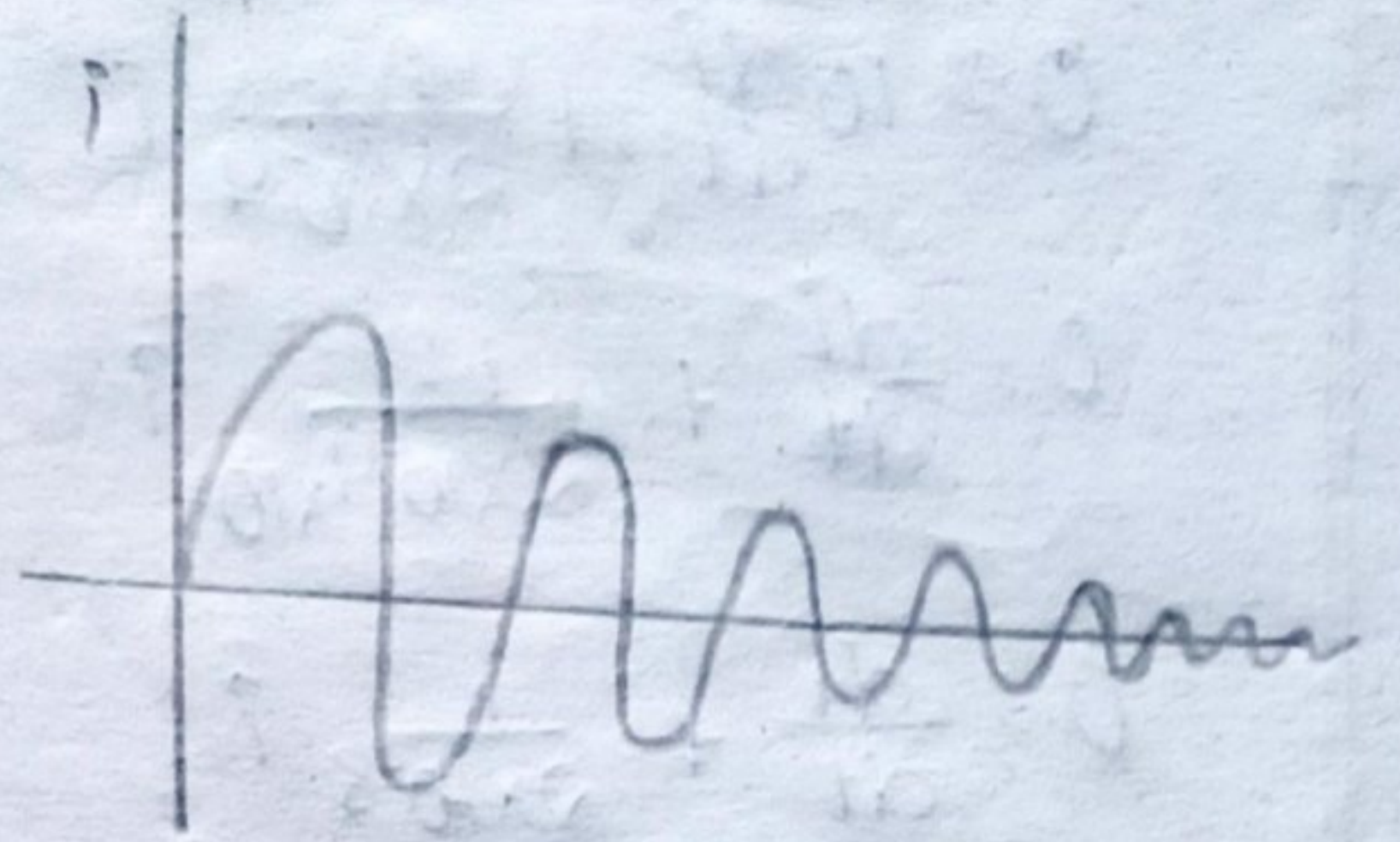
$$i = e^{\alpha t} [k_1 e^{j\beta t} + k_2 e^{-j\beta t}]$$



The current solution is oscillatory and underdamped

Case iii, $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$

Here $D_1 = \alpha + j\beta, \quad D_2 = \alpha - j\beta$

At this time β is zero hence D_1, D_2 are real & equal
 $\therefore D_1 = D_2 = \alpha$


$$D_1 = \alpha + 0 \quad D_2 = \alpha - 0$$

$$D_1 = \alpha \quad D_2 = \alpha$$

$$i = k_1 e^{\alpha t} + k_2 e^{\alpha t}$$

$$i = k_1 e^{\alpha t} + k_2 e^{\alpha t}$$

$$i = e^{\alpha t} [k_1 + k_2]$$

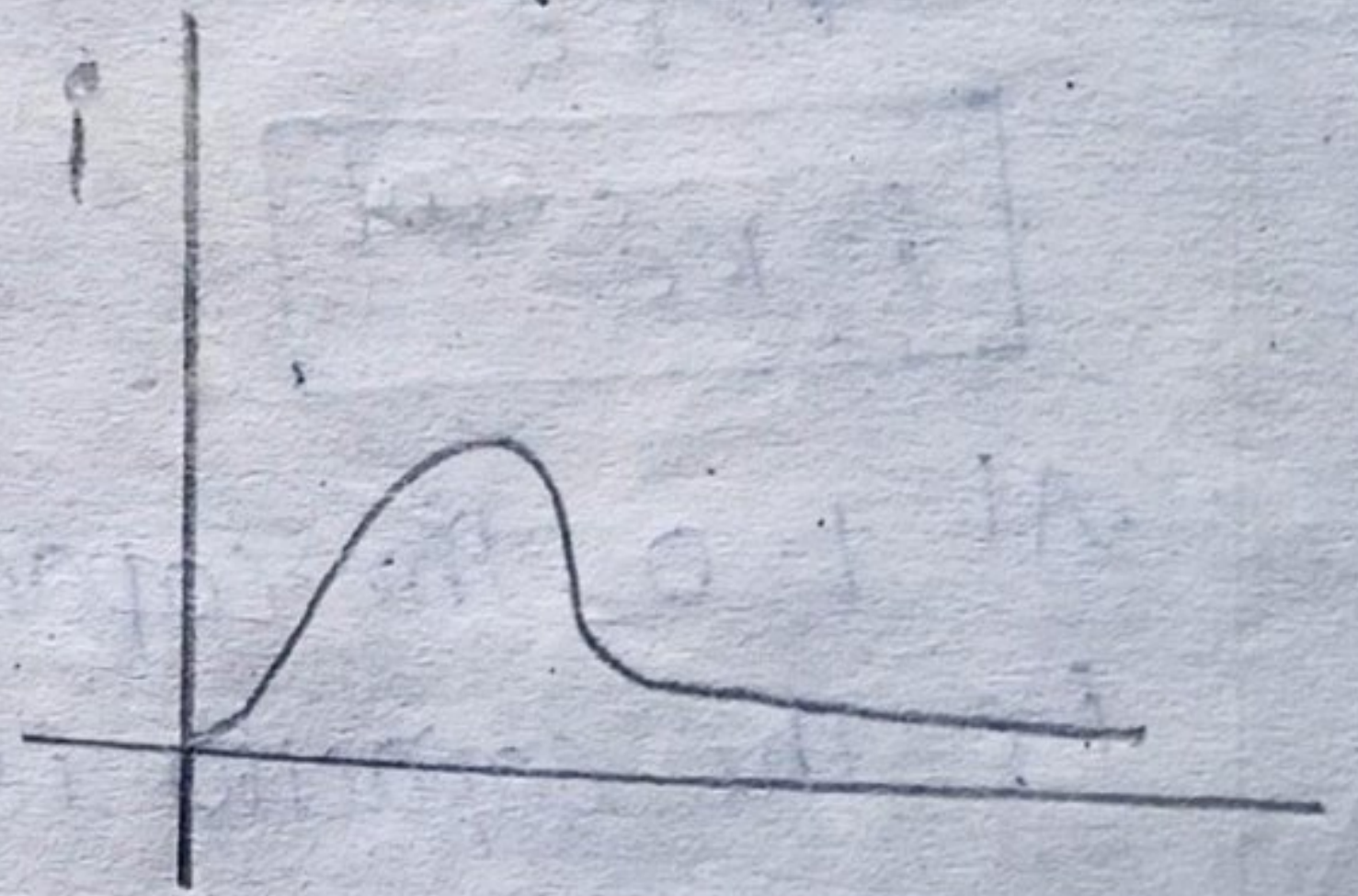

The current solution is critically damped


Prob: 1 For the circuit shown in figure determine the current at any time $t > 0$. The switch S is closed at $t = 0$ assume initial current & initial charge on the capacitor is zero

Applying the KVL

$$V = V_R + V_C$$

$$50 = i(10) + \frac{1}{2 \times 10^{-4}} \int i dt$$
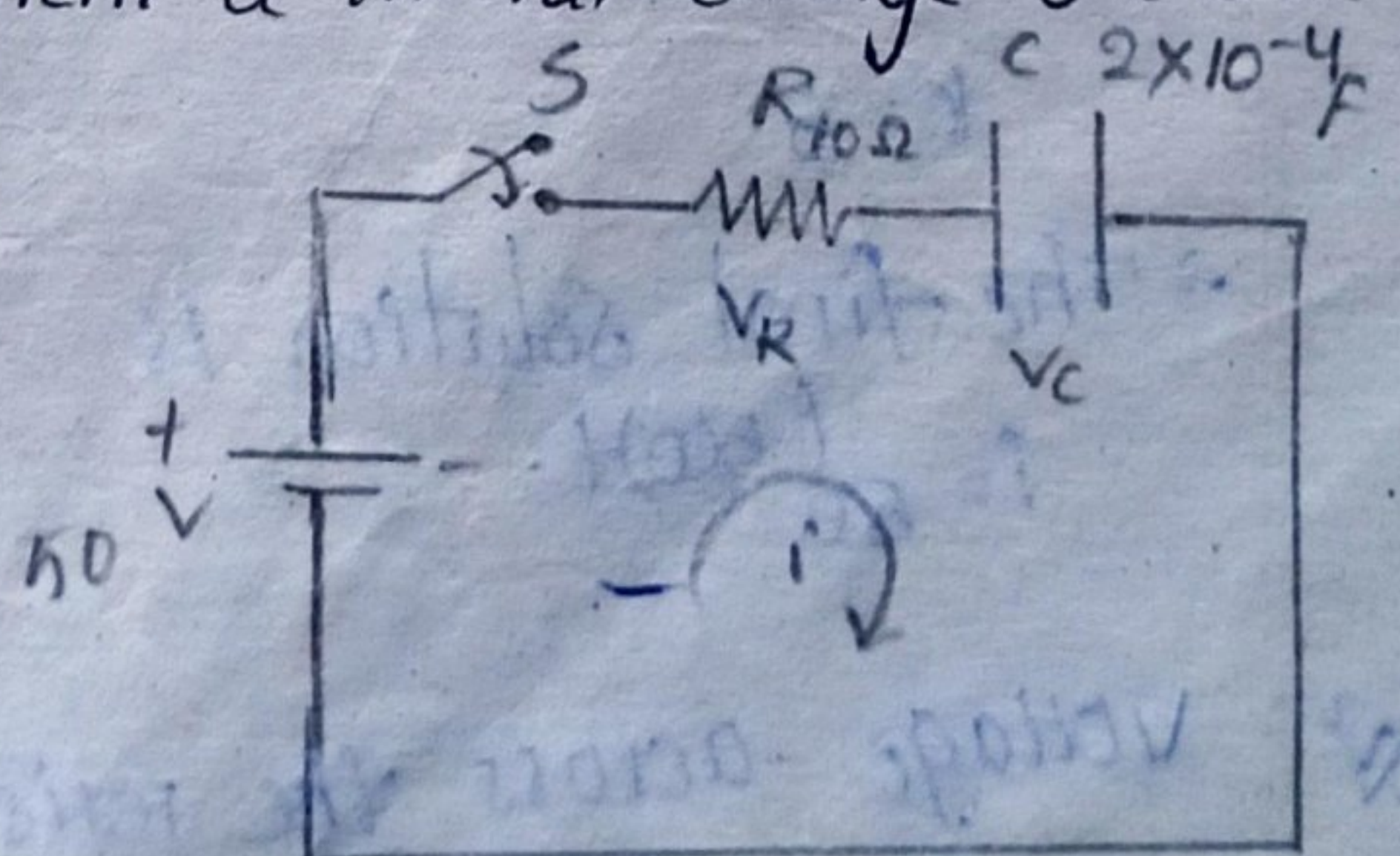
$$50 = 10i + \frac{1}{2 \times 10^{-4}} \int i dt$$



differentiating above equation

$$0 = 10 \frac{di}{dt} + \frac{1}{2 \times 10^{-4}} i$$

$$0 = \frac{di}{dt} + \frac{1}{2 \times 10^{-4} \times 10} i$$

$$0 = \frac{di}{dt} + \frac{1}{2 \times 10^{-3}} i$$

$$0 = Di + \frac{1}{2 \times 10^{-3}} i$$

$$0 = Di + (0.5) \times 10^3 i$$

$$0 = i(D + (0.5) \times 10^3)$$

$$0 = i(D + 500)$$

$$\Rightarrow D + 500 = 0 \quad D = -500$$

The current solution is

$$i = k e^{Dt}$$

$$i = k e^{-500t}$$

At $t=0$ the capacitor never allows sudden changes
i.e. the capacitor is a short ckt.

$$\therefore V_C = 0$$

$$i = \frac{V}{R} = \frac{50}{10}$$

$$i = 5 \text{ A}$$

$$\text{From } i = k e^{-500t}$$

$$5 = k e^{(-500)0}$$

$$k = 5$$

\therefore The final solution is

$$i = 5 e^{(-500)t}$$

voltage across the resistor $V_R = iR$

$$V_R = 5 e^{-500t} \times 10$$

$$V_R = 50$$

voltage across the capacitor $V_C = \frac{1}{C} \int i dt$

$$V_C = \frac{1}{2 \times 10^{-4}} \int 5 e^{-500t} dt$$

$$= \frac{5}{2 \times 10^{-4}} \int e^{-500t} dt$$

$$= \frac{5}{2 \times 10^{-4}} \frac{e^{-500t}}{-500}$$

$$= \frac{-1}{2 \times 10^{-2}} e^{-500t}$$

$$= -(0.5) \times 10^2 e^{-500t}$$

$$= -50 e^{-500t}$$

$$= -50 e^{-500t}$$

pb: 2 A Series R-L circuit has $R = 25 \Omega$ & $L = 5 H$. A dc voltage of 100 volts is applied at $t = 0$.

i. Find the equation for charging current, voltage across R & L

ii. The current in the circuit 0.5 sec later

iii. The time at which the drops across R & L are same

i. charging current $i = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$

$$i = \frac{100}{25} (1 - e^{-\frac{25}{5}t})$$

$$= 4(1 - e^{-5t})$$

$$x = 4(1 - e^{-5t})$$

$$x = 4(1 - 0)$$

$$x = 4$$

voltage across resistance $V_R = iR$

$$V_R = 4(1 - e^{-5t})(25)$$

$$V_R = 100(1 - e^{-5t})$$

Voltage across an inductance $V_L = \frac{1}{6} L \frac{di}{dt}$

$$V_L = 5 \frac{d}{dt} (4(1 - e^{-5t}))$$

$$= 20 \frac{d}{dt} (1 - e^{-5t})$$

$$= 20(-e^{-5t}(-5))$$

$$= 100 e^{-5t}$$

At $t = 0.5$ sec

$$i = 4(1 - e^{-5t})$$

$$i = 4(1 - e^{-5(0.5)})$$

$$i = 4(1 - e^{-2.5})$$

$$i = 4(1 - 0.08)$$

$$i = 4(0.92)$$

$$i = 3.68 \text{ amp.}$$

$$i = 3.68 \text{ amp}$$

(iii) To satisfying the condition $V_R = V_L$

At which time

$V_R = V_L$ at supply voltage $e = 100V$

$$V_R = V_L = 50$$

$$iR = L \frac{di}{dt}$$

$$50 = 100e^{-5t}$$

$$e^{-5t} = \frac{1}{2}$$

$$-5t = \log\left(\frac{1}{2}\right)$$

$$t = \frac{+1}{5} \log\left(\frac{1}{2}\right)$$

$$t = 0.060$$

Laplace transforms:

$$L(f(t)) = f(s)$$

$$L(1) = \frac{1}{s}$$

$$L(k) = \frac{k}{s}$$

$$L(t) = \frac{1}{s^2}$$

$$L[e^{-at}] = \frac{1}{s+a}$$

$$L[f'(t)] = sf(s) - f(0)$$

$$L[f''(t)] = s^2f(s) - sf(0) - f'(0)$$

Laplace of integration


$$L\left[\int_0^t f(t)\right] = \frac{F(s)}{s}$$

$$L[\cos \omega t] = \frac{s}{s^2 + \omega^2}$$

$$L[\sin \omega t] = \frac{\omega}{s^2 + \omega^2}$$

Transient response of R-L circuit. by using Laplace transform:-

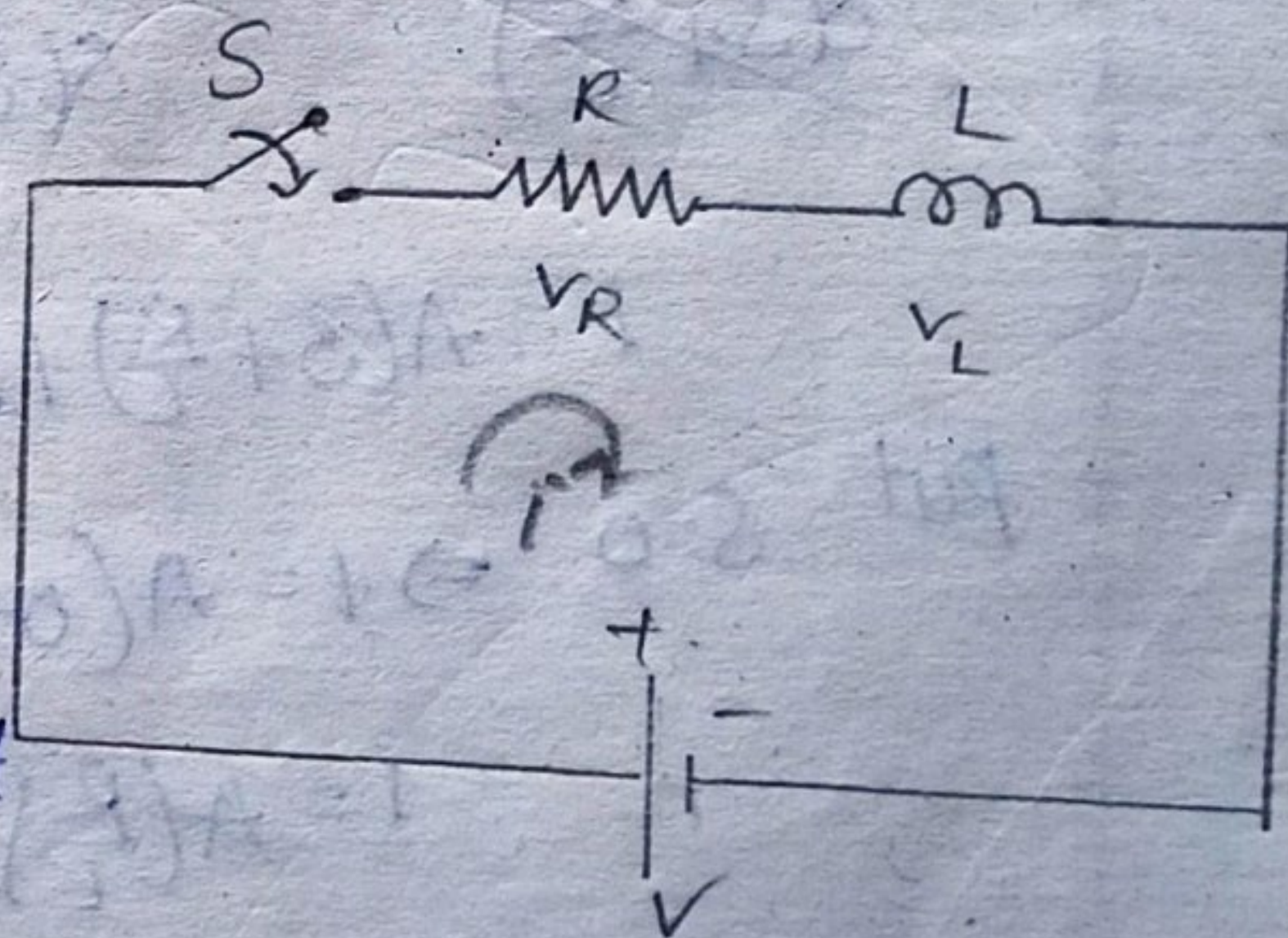A circuit consisting of a resistance in series with inductance as shown in fig



Apply the KVL in above ckt

$$V = iR + L \frac{di}{dt}$$

Apply Laplace transform

$$V = i(t)R + L \frac{di(t)}{dt}$$

$$\frac{V}{s} = R I(s) + L [s I(s) - I(0)]$$

before closing the switch $I(0) = 0$

$$\frac{V}{s} = R I(s) + L s I(s)$$

$$\frac{V}{s} = I(s)[R+LS]$$

$$I(s) = \frac{V/s}{R+LS}$$

$$= \frac{V}{s(R+LS)}$$

$$= \frac{V}{LS(s+\frac{R}{L})}$$

$$I(s) = \frac{V/L}{s(s+\frac{R}{L})}$$

$$I(s) = \frac{V}{L} \left(\frac{1}{s(s+\frac{R}{L})} \right)$$

Apply partial differentiation

$$I(s) = \frac{V}{L} \left(\frac{A}{s} + \frac{B}{s+\frac{R}{L}} \right) \rightarrow \text{①}$$

$$\frac{1}{s(s+\frac{R}{L})} = \frac{A}{s} + \frac{B}{s+\frac{R}{L}}$$

$$\frac{1}{s(s+\frac{R}{L})} = \frac{A(s+\frac{R}{L}) + Bs}{s(s+\frac{R}{L})}$$

$$1 = A(s+\frac{R}{L}) + Bs$$

$$\text{put } s=0 \Rightarrow 1 = A(0+\frac{R}{L}) + B(0)$$

$$1 = A(\frac{R}{L})$$

$$A = \frac{L}{R}$$

$$\text{put } s = -\frac{R}{L} \Rightarrow 1 = A\left[-\frac{R}{L} + \frac{R}{L}\right] + B\left[-\frac{R}{L}\right]$$

$$1 = A(0) + B\left(-\frac{R}{L}\right)$$

$$1 = B\left(-\frac{R}{L}\right)$$

$$B = -\frac{L}{R}$$

A & B values sub in eq ①

$$\frac{A}{s} + \frac{B}{s + \frac{R}{L}} = \frac{\frac{L}{R}}{s} + \frac{\frac{-L}{R}}{s + \frac{R}{L}}$$

$$= \frac{\frac{L}{R}}{s} - \frac{\frac{L}{R}}{s + \frac{R}{L}}$$

$$P(s) = \frac{V}{L} \left(\frac{1}{s(s + \frac{R}{L})} \right)$$

$$= \frac{V}{s} \left(\frac{\frac{L}{R}}{s} - \frac{\frac{L}{R}}{s + \frac{R}{L}} \right)$$

$$= \frac{V}{R} \left(\frac{1}{s} - \frac{1}{s + \frac{R}{L}} \right)$$

$$P(s) = \frac{V}{R} \left[\frac{1}{s} - \frac{1}{s + \frac{R}{L}} \right] \rightarrow \text{Eq ②}$$

Eq ② Apply inverse Laplace transform

$$i(t) = \frac{V}{R} \left[1 - e^{\left(-\frac{R}{L}\right)t} \right]$$

15-10-22


Transient response of R-C circuit:

Consider a circuit consisting of resistance in series with capacitance as shown in figure

Apply KVL in given circuit

$$V = V_R + V_C$$


$$= iR + \frac{1}{C}$$

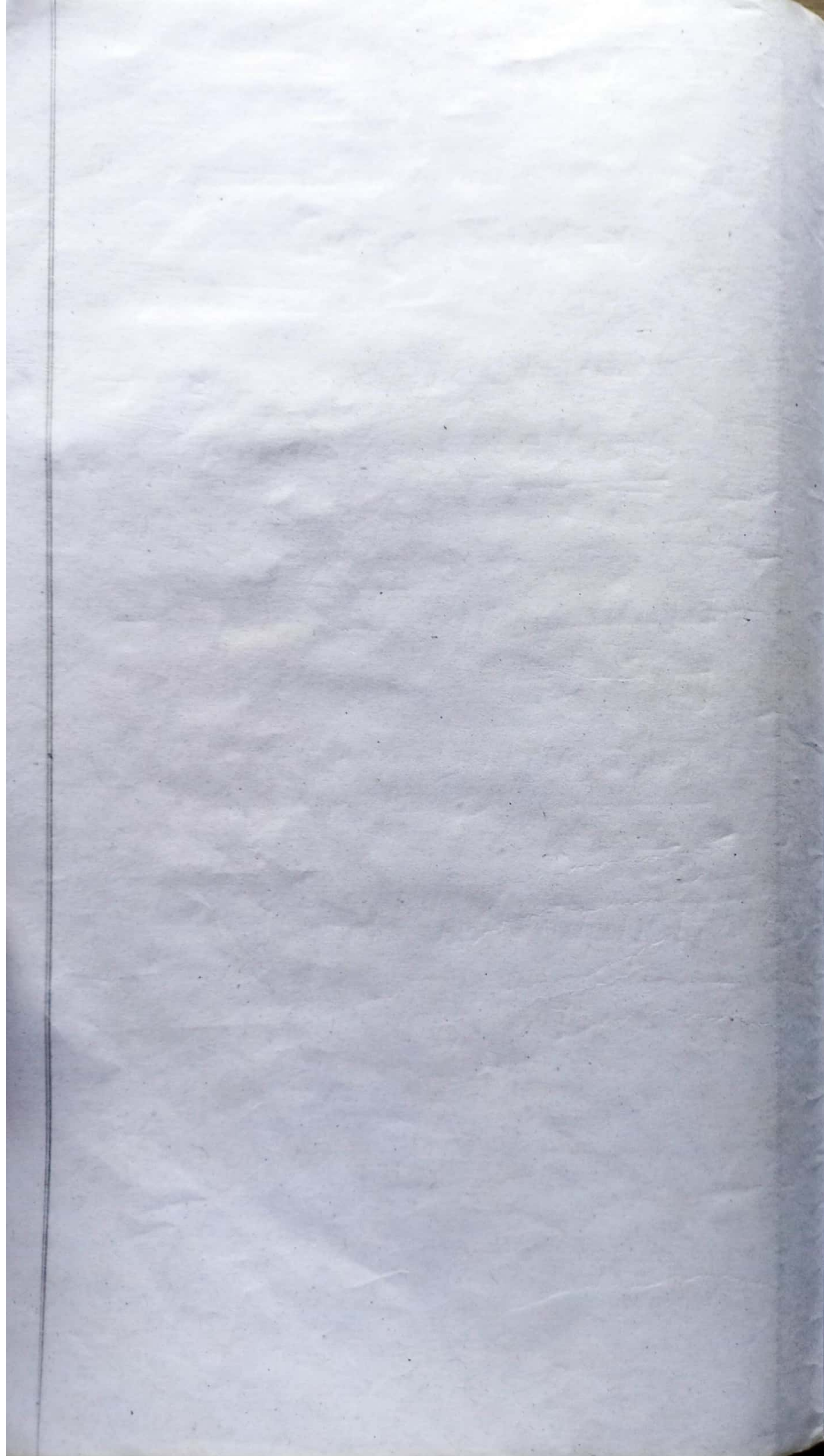

AC TRANSIENTS

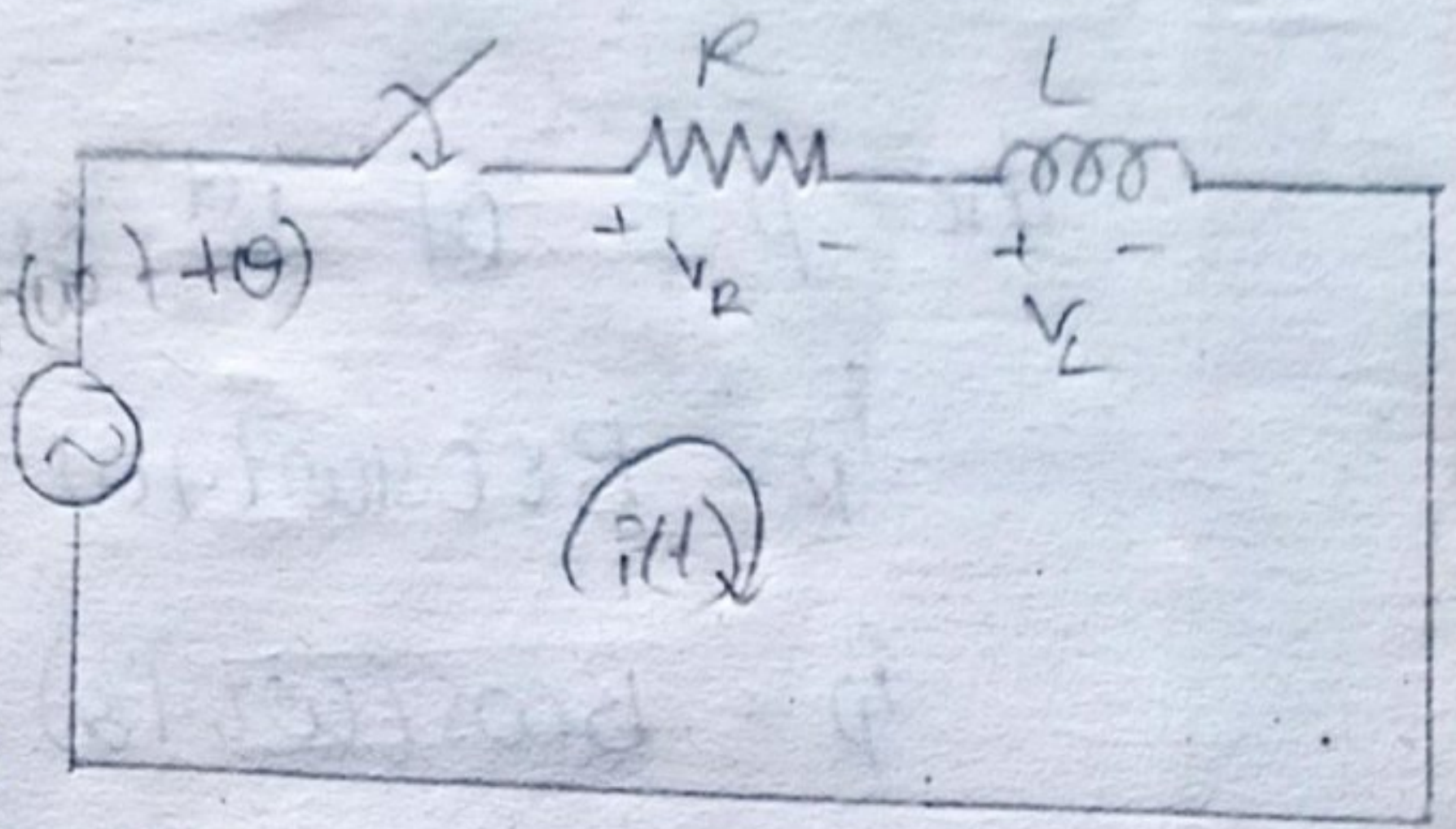1. Sinusoidal response of a RL circuit:

Consider a series circuit consisting of resistance and inductance as shown in figure. The switch 's' is



closed at $t=0$. A sinusoidal voltage $V_m \sin \omega t$ is applied to the series RL circuit

where V_m is the amplitude of the wave and θ is the phase angle

Apply KVL in above circuit

$$V_m \sin(\omega t + \theta) = V_R + V_L$$

$$V_m \sin(\omega t + \theta) = i(t)R + L \frac{di(t)}{dt}$$

$$L \left[\frac{di(t)}{dt} + \frac{R}{L} i(t) \right] = V_m \sin(\omega t + \theta)$$

$$\frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{V_m}{L} \sin(\omega t + \theta) \rightarrow (1)$$

The above equation is linear differential equation of a first order

$$\frac{d}{dt} = D \text{ as a operator}$$

$$D i(t) + \frac{R}{L} i(t) = \frac{V_m}{L} \sin(\omega t + \theta)$$

$$\frac{V_m}{L} \sin(\omega t + \theta) = i(t) \left[D + \frac{R}{L} \right]$$

$$\text{The C.P. is } \left[D + \frac{R}{L} \right] i(t) = 0$$

$$D = -\frac{R}{L}$$

The solution of C.F is $= Ae^{-\frac{R}{L}t}$.

$$C.F = i_c = Ae^{-\frac{R}{L}t}$$

The p.i of 1st order differential equation is

$$i_p = B \cos(\omega t + \theta) + C \sin(\omega t + \theta) \rightarrow (2)$$

$$i_p = B \cos(\omega t + \theta) + C \sin(\omega t + \theta)$$

$$\frac{di_p}{dt} = B(-\sin(\omega t + \theta)\omega) + C \cos(\omega t + \theta)\omega$$

$$= -B\omega \sin(\omega t + \theta) + C\omega \cos(\omega t + \theta) \rightarrow (3)$$

Sub (2) & (3) in eq (1)

$$\frac{V_m}{L} \sin(\omega t + \theta) = \frac{R}{L} [B \cos(\omega t + \theta) + C \sin(\omega t + \theta)] + [-B\omega \sin(\omega t + \theta) + C\omega \cos(\omega t + \theta)]$$

$$\frac{V_m}{L} \sin(\omega t + \theta) = \frac{R}{L} [B \cos(\omega t + \theta) + C \sin(\omega t + \theta)] + [-B\omega \sin(\omega t + \theta) + C\omega \cos(\omega t + \theta)]$$

$$\frac{V_m}{L} \sin(\omega t + \theta) = \sin(\omega t + \theta) \left[\frac{R}{L} C - B\omega \right] + \cos(\omega t + \theta) \left[\frac{R}{L} B + C\omega \right]$$

$$\frac{V_m}{L} \sin(\omega t + \theta) = \sin(\omega t + \theta) \left[\frac{R}{L} C - B\omega \right] + \cos(\omega t + \theta) \left[\frac{R}{L} B + C\omega \right]$$

Compare sin & cos terms

$$\frac{V_m}{L} = \frac{R}{L} C - B\omega \rightarrow (4)$$

$$0 = B \frac{R}{L} + C\omega$$

$$\frac{BR}{L} = -C\omega$$

$$B = -\frac{L}{R} C\omega \rightarrow (5)$$

B value in (4)

$$\frac{V_m}{L} = \frac{RC}{L} - B\omega$$

$$\frac{V_m}{L} = C \frac{R}{L} - \left(\frac{L}{R} C \omega \right) \omega$$

$$\frac{V_m}{L} = C \frac{R}{L} + \frac{L}{R} C \omega^2$$

$$\frac{V_m}{L} = C \left[\frac{R}{L} + \frac{L}{R} \omega^2 \right]$$

$$\frac{V_m}{L} = C \left[\frac{R^2 + L^2 \omega^2}{LR} \right]$$

$$V_m = C \left(\frac{R^2 + L^2 \omega^2}{R} \right)$$

$$C = \frac{V_m R}{R^2 + L^2 \omega^2}$$

from (5)

$$B = -\frac{L\omega}{R} \left(\frac{V_m R}{R^2 + L^2 \omega^2} \right)$$

$$B = -V_m \left(\frac{L\omega}{R^2 + L^2 \omega^2} \right)$$


Sub B & C in eq(2)

$$i_p = \frac{-V_m(L\omega)}{(R^2 + L^2 \omega^2)} \cos(\omega t + \theta) + \frac{V_m R}{(R^2 + L^2 \omega^2)} \sin(\omega t + \theta)$$

$$= \frac{V_m}{\sqrt{R^2 + L^2 \omega^2}} \left[\frac{L\omega}{\sqrt{R^2 + L^2 \omega^2}} \cos(\omega t + \theta) + \frac{R}{\sqrt{R^2 + L^2 \omega^2}} \sin(\omega t + \theta) \right]$$

$$i_p = \frac{V_m}{\sqrt{R^2 + L^2 \omega^2}} \left[\frac{-L\omega \cos(\omega t + \theta)}{\sqrt{R^2 + L^2 \omega^2}} + \frac{R \sin(\omega t + \theta)}{\sqrt{R^2 + L^2 \omega^2}} \right]$$
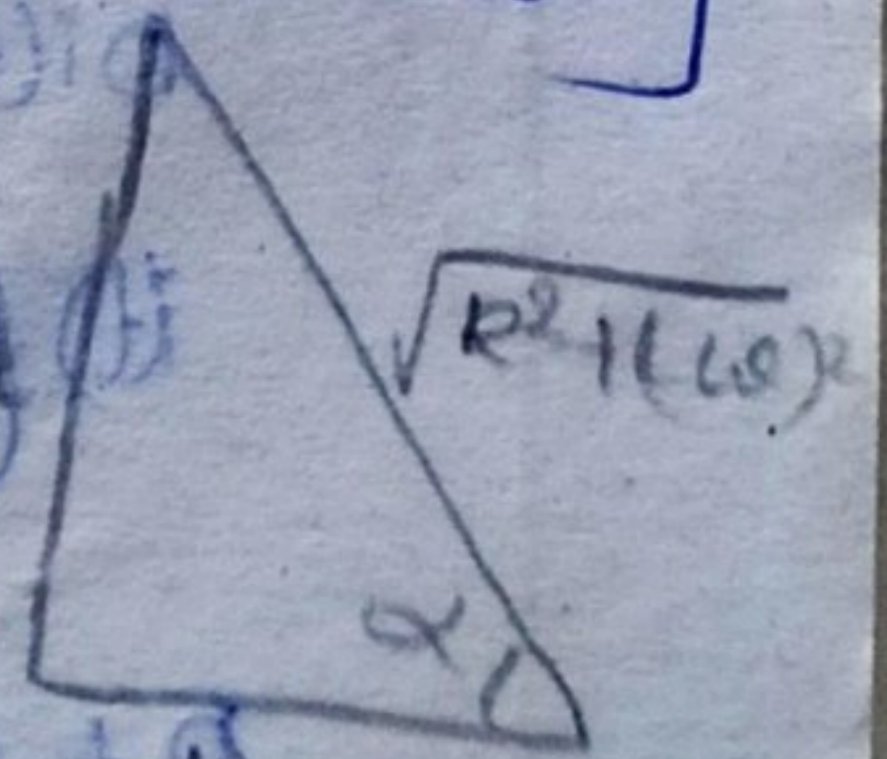
$$\sin \alpha = \frac{\omega L}{\sqrt{R^2 + L^2 \omega^2}} \quad \cos \alpha = \frac{R}{\sqrt{R^2 + L^2 \omega^2}}$$



$$\Rightarrow i_p = \frac{V_m}{\sqrt{R^2 + (L\omega)^2}} \left[-\sin\alpha \cos(\omega t + \theta) + \cos\alpha \sin(\omega t + \theta) \right]$$

$$= \frac{V_m}{\sqrt{R^2 + (L\omega)^2}} \sin(\omega t + \theta - \alpha)$$

$$= \frac{V_m}{\sqrt{R^2 + (L\omega)^2}} \sin(\omega t + \theta - \alpha)$$

* Sinusoidal response of R-C circuit:-

$$V_m \sin(\omega t + \theta) = V_R + V_C$$

$$V_m \sin(\omega t + \theta) = iR + \frac{1}{C} \int i dt$$

(integrating on both)

differentiating on both.

$$V_m \sin(\omega t + \theta) =$$

$$V_m \cos(\omega t + \theta) \omega = R \frac{di(t)}{dt} + \frac{1}{C} i(t)$$

$$V_m \omega \cos(\omega t + \theta) = R \frac{di(t)}{dt} + \frac{1}{C} i(t)$$

$$\frac{V_m \omega}{R} \cos(\omega t + \theta) = \frac{di(t)}{dt} + \frac{1}{RC} i(t) \rightarrow \text{--- (1)}$$

The above equation is in linear differential equation of a first order

$$\frac{d}{dt} = D \text{ as operator}$$

$$Di(t) + \frac{1}{RC} i(t) = \frac{V_m \omega}{R} \cos(\omega t + \theta)$$

$$i(t) \left[D + \frac{1}{RC} \right] = \frac{V_m \omega}{R} \cos(\omega t + \theta)$$

$$D + \frac{1}{RC} = 0$$

$$D = \frac{-1}{RC}$$

The solution of C.F is $= Ae^{-\frac{R}{L}t}$
 $= Ae^{-\frac{1}{RC}t}$

$$C.F = i_c = A e^{-\frac{1}{RC}t}$$

The p.s of first order differential equation is

$$i_p = B \cos(\omega t + \theta) + C \sin(\omega t + \theta) \rightarrow (2)$$

$$\frac{di_p}{dt} = B(-\sin(\omega t + \theta)\omega) + C \cos(\omega t + \theta)\omega$$

$$= -B\omega \sin(\omega t + \theta) + C\omega \cos(\omega t + \theta) \rightarrow (3)$$

Sub (2) & (3) in eq (1)

$$\frac{V_m \omega}{R} \cos(\omega t + \theta) = \frac{1}{RC} [B \cos(\omega t + \theta) + C \sin(\omega t + \theta)]$$

$$-B\omega \sin(\omega t + \theta) + C\omega \cos(\omega t + \theta)$$

$$\frac{V_m \omega}{R} \cos(\omega t + \theta) = \sin(\omega t + \theta) \left[\frac{1}{RC} C - B\omega \right] + \cos(\omega t + \theta) \left[\frac{1}{RC} B + C\omega \right]$$

$$\frac{V_m \omega}{R} \cos(\omega t + \theta) = \sin(\omega t + \theta) \left[\frac{1}{RC} C - B\omega \right] + \cos(\omega t + \theta) \left[\frac{1}{RC} B + C\omega \right]$$

Compare Sin & Cos

$$\frac{V_m \omega}{R} = \frac{B}{RC} + C\omega \rightarrow (4)$$

$$0 = \frac{1}{RC} C - B\omega \rightarrow (5)$$

$$B\omega = \frac{1}{RC} C \rightarrow \text{Constant} \rightarrow \text{Capacitance}$$

$$B = \frac{1}{RC \omega} \rightarrow (5)$$

B value in eq (1)

$$\frac{V_m \omega}{R} = \left(\frac{C}{RC \omega} \right) + C \omega$$

$$\frac{V_m \omega}{R} = \frac{C}{(RC)^2 \omega} + C \omega$$

$$\frac{V_m \omega}{R} = C \left(\omega + \frac{1}{(RC)^2 \omega} \right)$$

$$C = \frac{V_m \omega}{R \left(\omega + \frac{1}{(RC)^2 \omega} \right)} = \frac{V_m \omega}{R \left[1 + \frac{1}{(\omega \cdot RC)^2} \right]}$$

$$C = \frac{V_m \omega}{R \left(\omega + \frac{1}{(RC)^2 \omega} \right)} = \frac{V_m \omega}{\frac{R}{RC^2} \left[R^2 + \frac{1}{(\omega C)^2} \right]}$$

$$\therefore B = \frac{1}{RC \omega} (C)$$

$$B = \frac{1}{RC \omega} \frac{V_m \omega}{R \left(\omega + \frac{1}{(RC)^2 \omega} \right)}$$

$$B = \frac{V_m}{R^2 C \left(\omega + \frac{1}{(RC)^2 \omega} \right)}$$


$$C = \frac{V_m R}{R^2 + \left(\frac{1}{\omega C} \right)^2}$$

Sub B & C value in eq (2)

$$i_p = \frac{V_m}{R^2 C \left(\omega + \frac{1}{(RC)^2 \omega} \right)} \cos(\omega t + \theta) + \frac{V_m \omega}{R \left(\omega + \frac{1}{(RC)^2 \omega} \right)} \sin(\omega t + \theta)$$

$$i_p = \frac{V_m}{R \left(\omega + \frac{1}{(RC)^2 \omega} \right)} \left[\frac{\cos(\omega t + \theta)}{RC} + \omega \sin(\omega t + \theta) \right]$$
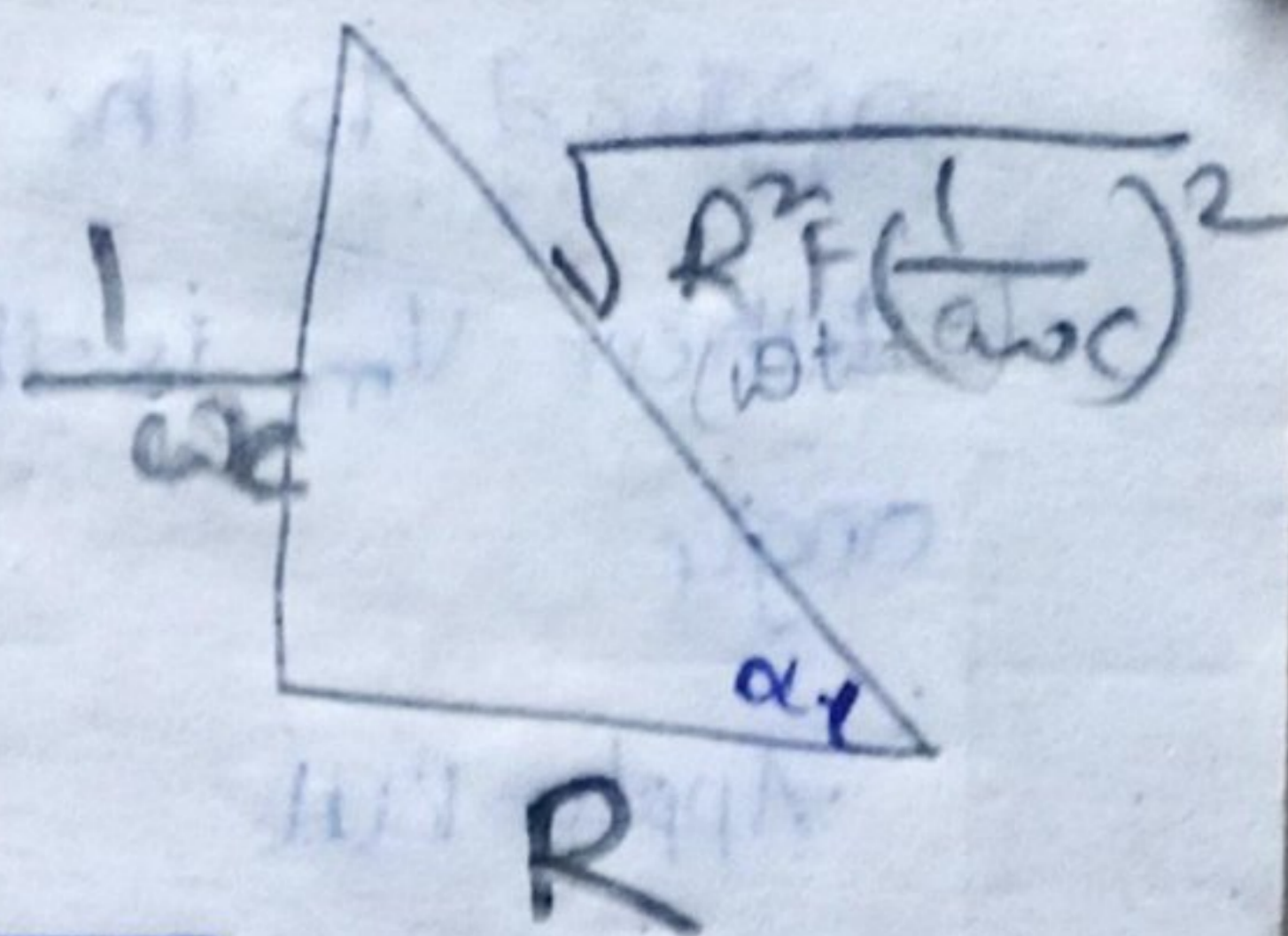
$$B = \frac{V_m R}{\omega R C (R^2 + (\frac{1}{\omega C})^2)}$$



$$B = \frac{V_m}{\omega C (R^2 + (\frac{1}{\omega C})^2)}$$

$$i_p = \frac{V_m}{\omega C (R^2 + (\frac{1}{\omega C})^2)} \cos(\omega t + \theta) + \frac{V_m R}{R^2 + (\frac{1}{\omega C})^2} \sin(\omega t + \theta)$$

$$i_p = \frac{V_m}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \left[\frac{1}{\omega C} \frac{\cos(\omega t + \theta)}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} + \frac{R \sin(\omega t + \theta)}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \right]$$

from the diagram:

$$\sin \alpha = \frac{1}{\omega C} \frac{1}{\sqrt{R^2 + (\frac{1}{\omega C})^2}}$$

$$\cos \alpha = \frac{R}{\sqrt{R^2 + (\frac{1}{\omega C})^2}}$$

$$i_p = \frac{V_m}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \left[\sin \alpha \cos(\omega t + \theta) + \cos \alpha \sin(\omega t + \theta) \right]$$

$$= \frac{V_m}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \left[\sin(\omega t + \theta + \alpha) \right]$$

Sinusoidal response of R-L-C circuit

Consider a series circuit consisting of resistance, inductance, capacitance

as shown in fig. The switch S is closed at t=0. A

sinusoidal voltage $V_m \sin \omega t$

applied to the R-L-C circuit

where V_m is the amplitude & θ is the phase angle

Apply KVL

$$V_m \sin(\omega t + \theta) = V_R + V_L + V_C$$

$$V_m \sin(\omega t + \theta) = iR + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$

differentiating on both sides

$$V_m \cos(\omega t + \theta) = R \frac{di(t)}{dt} + L \frac{d^2 i(t)}{dt^2} + \frac{1}{C} i(t)$$

$$\frac{V_m \cos(\omega t + \theta)}{L} = \frac{R}{L} \frac{di(t)}{dt} + \frac{d^2 i(t)}{dt^2} + \frac{1}{LC} i(t)$$

$\frac{d}{dt} = D$ as operator

$$D^2 i(t) + \frac{R}{L} D i(t) + \frac{1}{LC} i(t) = \frac{V_m}{L} \cos(\omega t + \theta) \rightarrow \textcircled{1}$$

$$i(t) \left[D^2 + \frac{R}{L} D + \frac{1}{LC} \right] = \frac{V_m}{L} \cos(\omega t + \theta)$$

$$D^2 + \frac{R}{L} D + \frac{1}{LC} = 0$$

$$D_{1,2} = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4 \times \frac{1}{LC}}}{2}$$

$$D_{1,2} = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2}$$

$$D_{1,2} = \frac{-\frac{R}{L} \pm \frac{R}{L} \sqrt{1 - \frac{4L}{R^2 C}}}{2}$$

$$\alpha = \frac{R}{2L}$$

$$= \frac{-R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

$$\beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$= \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Solution of C.F. is $i_c = k_1 e^{D_1 t} + k_2 e^{D_2 t}$

k_1 & k_2 are the constants

D_1, D_2 are the roots

Case i, When

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

At this time β is positive real quantity
hence the roots are D_1, D_2 are real & unequal

$$D_1 = \alpha + \beta \quad D_2 = \alpha - \beta$$

The current solution is

$$i = k_1 e^{D_1 t} + k_2 e^{D_2 t}$$

$$i = k_1 e^{(\alpha + \beta)t} + k_2 e^{(\alpha - \beta)t}$$

$$i = k_1 e^{\alpha t} e^{\beta t} + k_2 e^{\alpha t} e^{-\beta t}$$

$$i = e^{\alpha t} [k_1 e^{\beta t} + k_2 e^{-\beta t}]$$

The above equation is the current solution

ii, When $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$

at this time β is imaginary quantity & the roots
 D_1, D_2 are complex conjugate

$$D_1 = \alpha + j\beta \quad D_2 = \alpha - j\beta$$

$$i = k_1 e^{D_1 t} + k_2 e^{D_2 t}$$

$$i = k_1 e^{(\alpha + j\beta)t} + k_2 e^{(\alpha - j\beta)t}$$

$$i = k_1 e^{\alpha t} e^{j\beta t} + k_2 e^{\alpha t} e^{-j\beta t}$$

$$i = e^{\alpha t} [k_1 e^{j\beta t} + k_2 e^{-j\beta t}]$$

$$i = e^{\alpha t} [k_1 e^{j\beta t} + k_2 e^{-j\beta t}]$$

Current

The Solution is oscillatory & underdamped

Case iii,

$$\frac{R}{LQ} = \frac{1}{LC}$$

$$D_1 = \alpha + j\beta \quad D_2 = \alpha - j\beta$$

at this time β is zero Hence D_1, D_2 are the real & equal

$$D_1 = \alpha + 0 \quad D_2 = \alpha + 0$$

$$D_1 = \alpha \quad D_2 = \alpha$$

$$i = k_1 e^{\alpha t} + k_2 e^{\alpha t}$$

$$i = e^{\alpha t} [k_1 + k_2]$$

The Solution is critically damped

The p-2 solution is

$$i_p = B \cos(\omega t + \theta) + C \sin(\omega t + \theta) \rightarrow (1)$$

$$\frac{di_p}{dt} = B(-\sin(\omega t + \theta))\omega + C \cos(\omega t + \theta)\omega$$

$$\frac{di_p}{dt} = -B\omega \sin(\omega t + \theta) + C\omega \cos(\omega t + \theta) \rightarrow (2)$$

$$\frac{d^2 i_p}{dt^2} = -B\omega^2 \cos(\omega t + \theta) + C\omega[-\sin(\omega t + \theta)]\omega$$

$$\frac{d^2 i_p}{dt^2} = -B\omega^2 \cos(\omega t + \theta) - C\omega^2 \sin(\omega t + \theta)$$

from the eq (1)

$$-B\omega^2 \cos(\omega t + \theta) - C\omega^2 \sin(\omega t + \theta) + \frac{R}{L} [-B\sin(\omega t + \theta) + C\omega \cos(\omega t + \theta)] + \frac{1}{LC} [B\cos(\omega t + \theta) + C\sin(\omega t + \theta)] = \frac{V_m}{L} \cos(\omega t + \theta)$$

Compare cos terms & sin terms

$$\frac{V_m}{L} = -B\omega^2 + \frac{R\omega}{L}C + \frac{1}{LC}B \rightarrow (3)$$

$$\frac{V_m}{L} = B\left[\frac{1}{LC} - \omega^2\right] + C\frac{R\omega}{L} \rightarrow (4) \quad D = \frac{d}{dt}$$

$$B\left[\frac{1}{LC} - \omega^2\right] = \frac{V_m}{L} - \frac{CR\omega}{L} \quad D^2 i(t)$$

$$B = \frac{\left(\frac{V_m - CR\omega}{L}\right)}{\left(\frac{1}{LC} - \omega^2\right)} \quad \frac{d^2 i(t)}{dt^2}$$

$$B = \frac{\frac{1}{L}(V_m - CR\omega)}{\frac{1}{L}\left(\frac{1}{C} - L\omega^2\right)} \Rightarrow B = \frac{\omega\left[\frac{V_m}{\omega} - CR\right]}{\omega^2\left[\frac{1}{C\omega} - L\right]}$$

$$B = \frac{C(V_m - CR\omega)}{\omega\left[\frac{1}{C\omega} - L\right]} \Rightarrow B = \frac{\left[\frac{V_m}{\omega} - CR\right]}{\omega\left[\frac{1}{C\omega} - L\right]}$$

Compare sin terms

$$-C\omega^2 - \frac{R\omega}{L}B + \frac{1}{LC}C = 0 \rightarrow (5)$$

$$C\left[\frac{1}{LC} - \omega^2\right] = \frac{R\omega}{L}B$$

$$B = C\left[\frac{1}{LC} - \omega^2\right]\left[\frac{L}{R\omega}\right]$$

from eq (4)

$$-C\omega^2 - \frac{R\omega}{L}\left[\frac{L}{R\omega}\right]\left[C\left[\frac{1}{LC} - \omega^2\right]\right] + \frac{1}{LC}C = 0$$

$$C\left[-\omega - \frac{1}{LC} + \omega^2\right] + \frac{1}{LC}C = 0$$

$$-\frac{1}{LC}C + \frac{1}{LC}C = 0$$

from eq (3) Sub B

$$\frac{V_m}{L} = \left[\frac{1}{LC} - \omega^2 \right] \left[\frac{L}{R\omega} \right] \left[\frac{1}{LC} - \omega^2 \right] + C \frac{R\omega}{L}$$

$$\frac{V_m}{L} = C \left[\left(\frac{1}{LC} - \omega^2 \right)^2 \left(\frac{L}{R\omega} \right) \right] + C \frac{R\omega}{L}$$

$$\frac{V_m}{L} = C \left[\left(\frac{1}{LC} - \omega^2 \right)^2 \left(\frac{L}{R\omega} \right) + \frac{R\omega}{L} \right]$$

$$C = \frac{V_m}{L} \left[\frac{1}{\left(\frac{1}{LC} - \omega^2 \right)^2 \left(\frac{L}{R\omega} \right) + \left(\frac{R\omega}{L} \right)} \right]$$

$$B = \frac{V_m}{K} \left[\frac{1}{\left(\frac{1}{LC} - \omega^2 \right)^2 \left(\frac{L}{R\omega} \right) + \left(\frac{R\omega}{L} \right)} \right] \left[\frac{1}{LC} - \omega^2 \right] \left(\frac{L}{R\omega} \right)$$

$$B = \frac{V_m \left(\frac{1}{LC} - \omega^2 \right)}{\left[\left(\frac{1}{LC} - \omega^2 \right)^2 \left(\frac{L}{R\omega} \right) + \frac{R\omega}{L} \right]}$$

Badhaga untadi

Dopam kannu

$$i_p = \left[\frac{V_m \left(\frac{1}{LC} - \omega^2 \right)}{\left(\frac{1}{LC} - \omega^2 \right)^2 \frac{L}{R\omega} + \frac{R\omega}{L}} \right] \cos(\omega t + \theta) + \frac{V_m}{L} \left[\frac{1}{\left(\frac{1}{LC} - \omega^2 \right)^2 \frac{L}{R\omega} + \frac{R\omega}{L}} \right] \sin(\omega t + \theta)$$

$$i_p = \frac{V_m \left(\frac{1}{LC} - \omega^2 \right)}{\frac{L}{R\omega} \left[\left(\frac{1}{LC} - \omega^2 \right)^2 + \frac{R^2 \omega^2}{L^2} \right]} \cos(\omega t + \theta) + \frac{V_m}{L} \frac{1}{\left[\left(\frac{1}{LC} - \omega^2 \right)^2 + \left(\frac{R\omega}{L} \right)^2 \right] \frac{L}{R\omega}}$$

= V_m

Handwritten text in Telugu script, appearing as bleed-through from the reverse side of the page. The text is arranged in several lines and includes some numbers and symbols.

2-11-22

UNIT - IV Network Parameters

Two port network.

Generally any network may be represented by a rectangular box


A network may be represented either source or load or different purpose

port: A pair of terminals at which a signal may enter or leave a network is called a port.

Two port network:-

A Two port network or two terminals pair of network in which 4 terminals

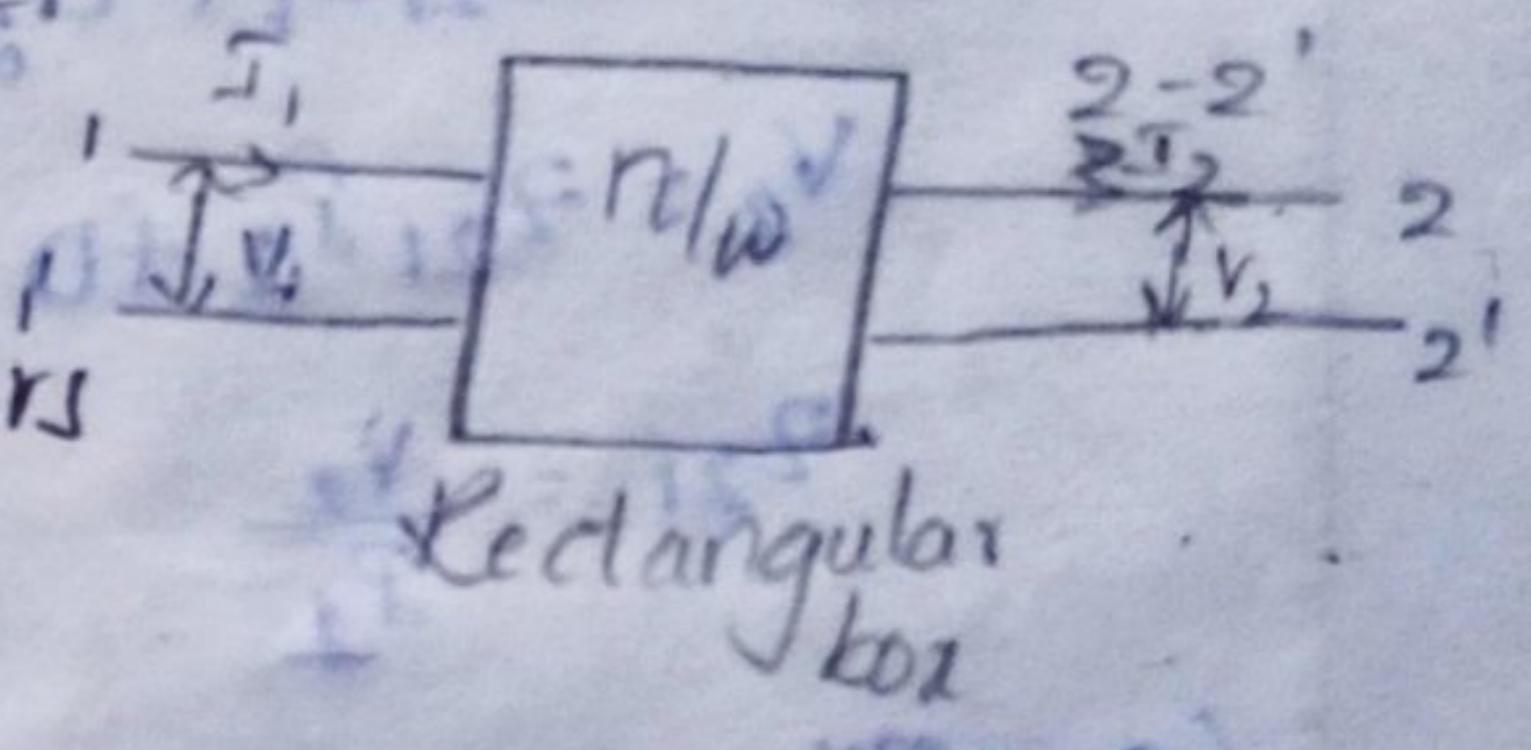The port 1-1' voltage and current at the input terminals V_1 & I_1 , the 2-2' is the another port is output terminals




→ Types of 2-port n/w parameters

1. Z-parameters
2. Y-parameter
3. ABCD-parameter
4. H-parameter
5. H⁻¹ - parameter (Inverse H)

H = Hybrid.

Z-parameters / open circuit parameters

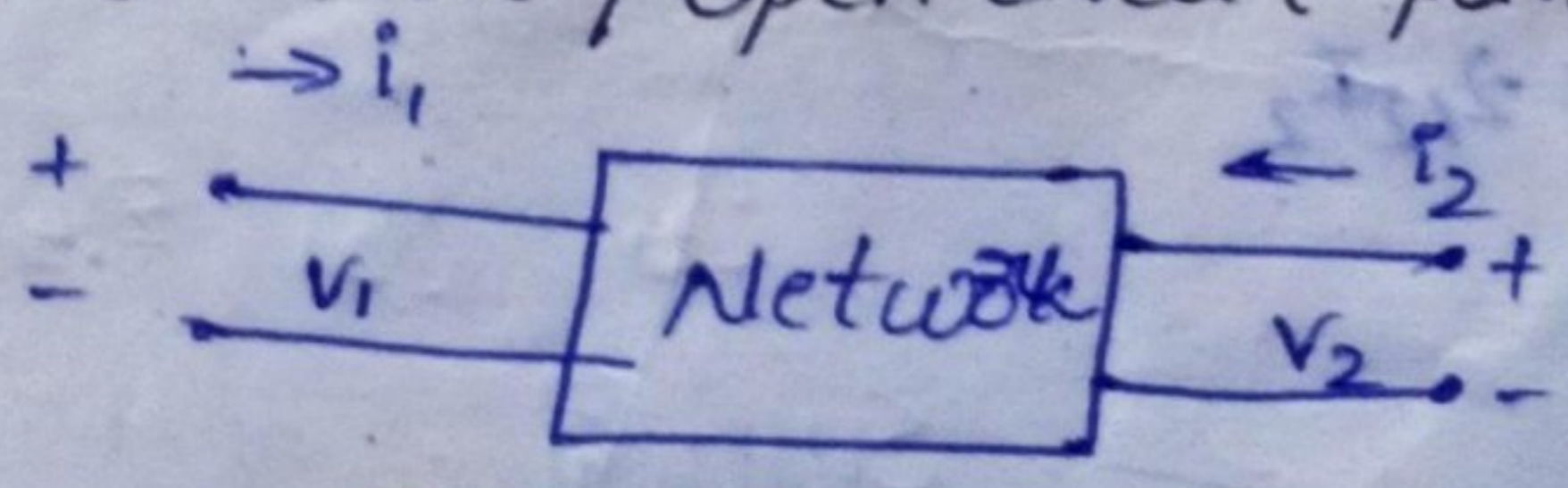

$$V = ZI$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

[u is dependent
I is independent]

$$V_1 = z_{11}I_1 + z_{12}I_2 \quad \text{--- } \textcircled{1}$$

$$V_2 = z_{21}I_1 + z_{22}I_2 \quad \text{--- } \textcircled{2}$$

Case (i) port 2 is open $I_2 = 0$

$$\textcircled{1} \Rightarrow V_1 = z_{11}I_1 + z_{12}(0)$$

$$V_1 = z_{11}I_1 + z_{12}(0)$$

$$V_1 = z_{11}I_1 + 0$$

$$V_1 = z_{11}I_1$$

$$z_{11} = \frac{V_1}{I_1}$$

drawing port 2 impedance at port 1

$$\textcircled{2} \Rightarrow V_2 = z_{21}I_1 + z_{22}I_2$$

$$V_2 = z_{21}I_1 + z_{22}(0)$$

$$V_2 = z_{21}I_1 + 0$$

$$z_{21} = \frac{V_2}{I_1}$$

Case (ii) first port is open $I_1 = 0$

$$\textcircled{1} \Rightarrow V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_1 = z_{11}(0) + z_{12}I_2$$

$$V_1 = z_{12}I_2$$

$$z_{12} = \frac{V_1}{I_2}$$

Reciprocity:-

$$y_{12} = y_{21} \quad z_{12} = z_{21}$$

Symmetry:-

$$y_{11} = y_{22} \quad z_{11} = z_{22}$$

$$\textcircled{2} \Rightarrow V_2 = z_{21}I_1 + z_{22}I_2$$

$$V_2 = z_{21}(0) + z_{22}I_2$$

$$V_2 = Z_{22} I_2$$

$$Z_{22} = \frac{V_2}{I_2}$$


$\therefore Z_{22}$ driving point impedance at port 2

$\therefore Z_{01}$ Open circuit forward transform impedance

2 Y parameters (or) short-circuit parameters

where V_1 is dependent

V_2 is independent

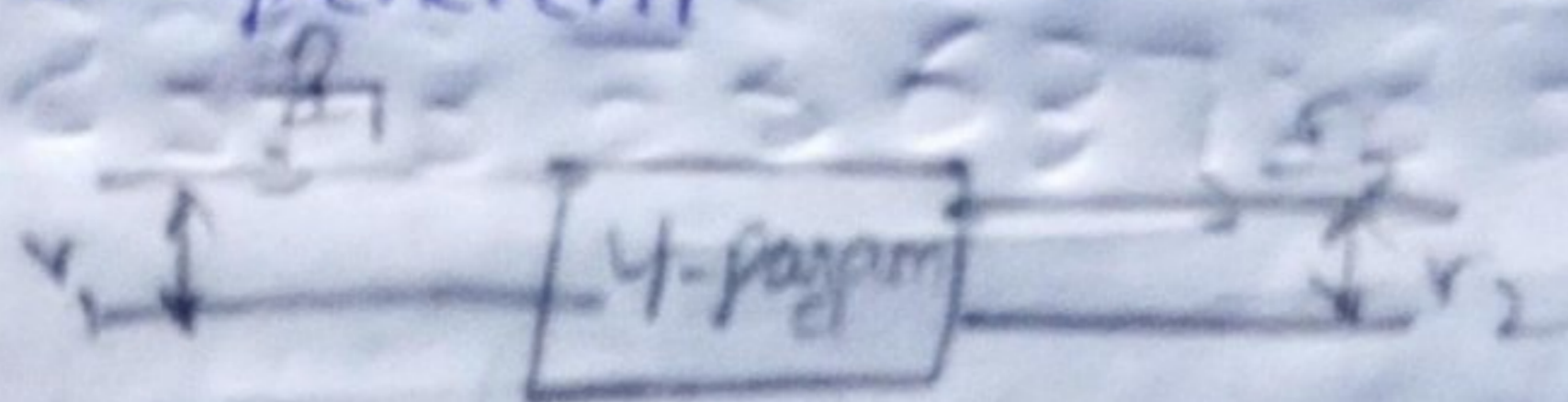

$$V = 12$$

$$\therefore Z = \frac{1}{Y}$$

$$I = 8 \frac{1}{Y}$$


$$\Rightarrow 8 = VY$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

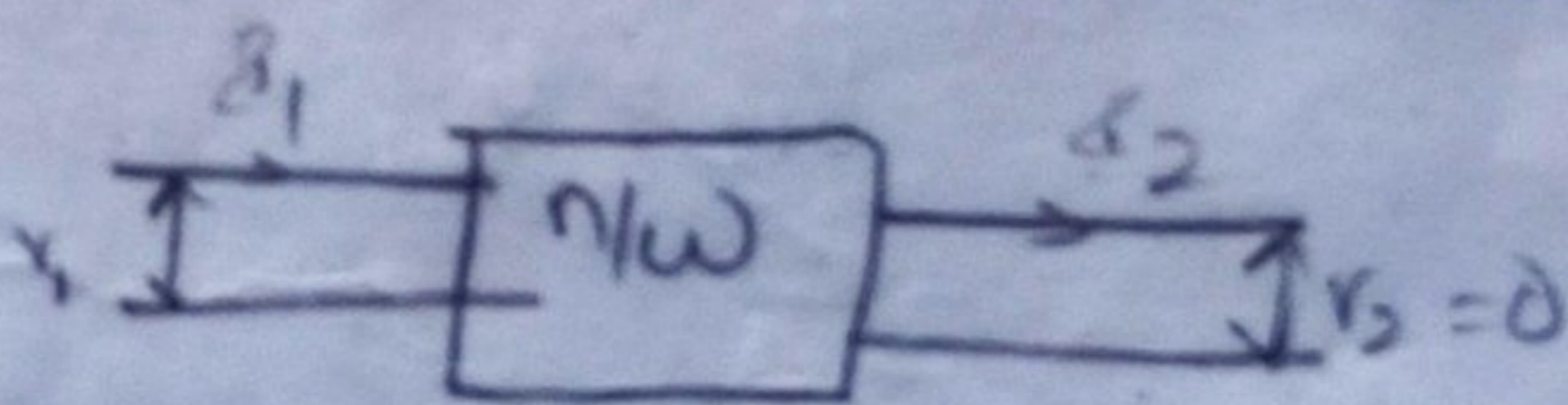case (i) 2nd port is short circuit, i.e. $V_2 = 0$



$$I_1 = Y_{11} V_1 + Y_{12} (0)$$

$$I_1 = Y_{11} V_1 + 0$$

$$Y_{11} = \frac{I_1}{V_1}$$

$\therefore Y_{11}$ driving point admittance at port 1


$$\textcircled{2} \Rightarrow I_2 = Y_{21}V_1 + Y_{22}(V_2)$$

$$I_2 = Y_{21}V_1 + Y_{22}(0)$$

$$I_2 = Y_{21}V_1 + 0$$

$$Y_{21} = \frac{I_2}{V_1}$$

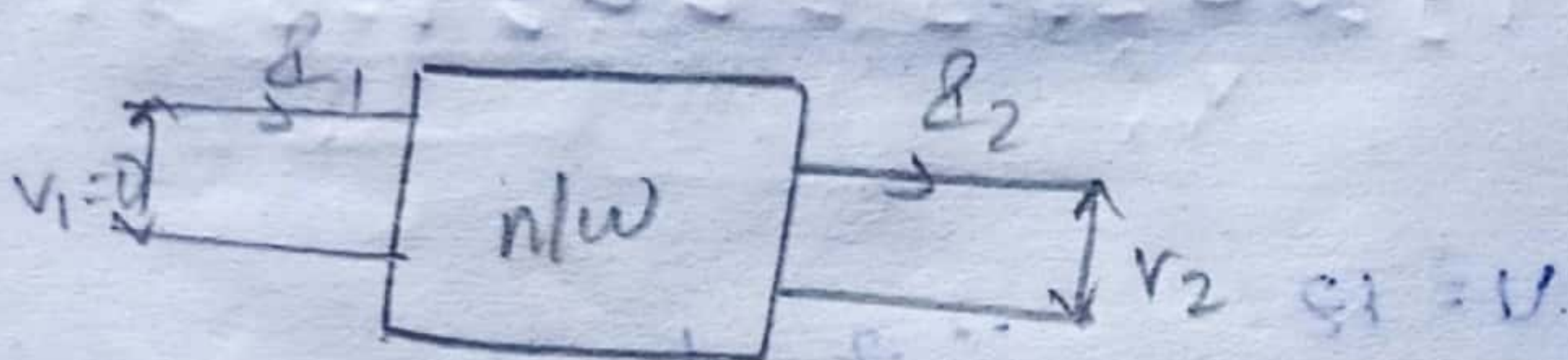$\therefore Y_{21}$ short circuit forward transform admittance
 case ii, 2nd port is short circuit i.e. $V_2 = 0$



$$I_1 = Y_{11}(0) + Y_{12}V_2$$

$$I_1 = Y_{12}V_2$$

$$Y_{12} = \frac{I_1}{V_2}$$

$\therefore Y_{12}$ short circuit reverse transform admittance

$$\textcircled{3} \Rightarrow I_2 = Y_{21}(0) + Y_{22}V_2$$

$$I_2 = Y_{22}V_2$$


$$Y_{12} = Y_{21}$$

$$Y_{22} = \frac{I_2}{V_2}$$

$$\text{or } Y_{11} = Y_{22}$$

Y_{22} driving point admittance at port 2

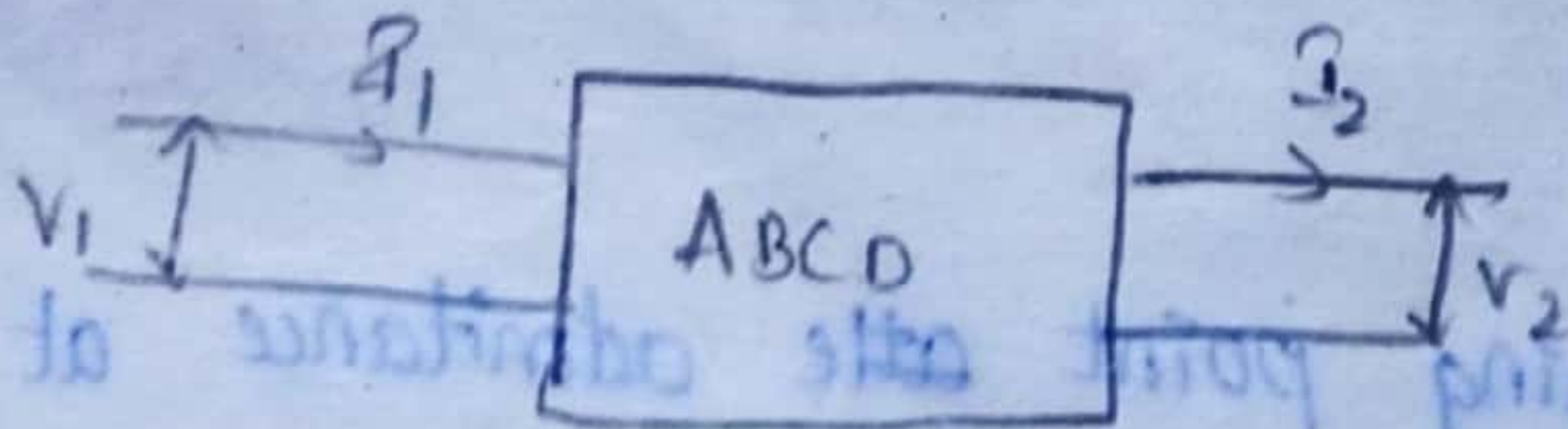$\textcircled{3}$ ABCD parameter / transmission line parameters




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = AV_2 + B(-I_2) \rightarrow (1)$$

$$I_1 = CV_2 + D(-I_2) \rightarrow (2)$$

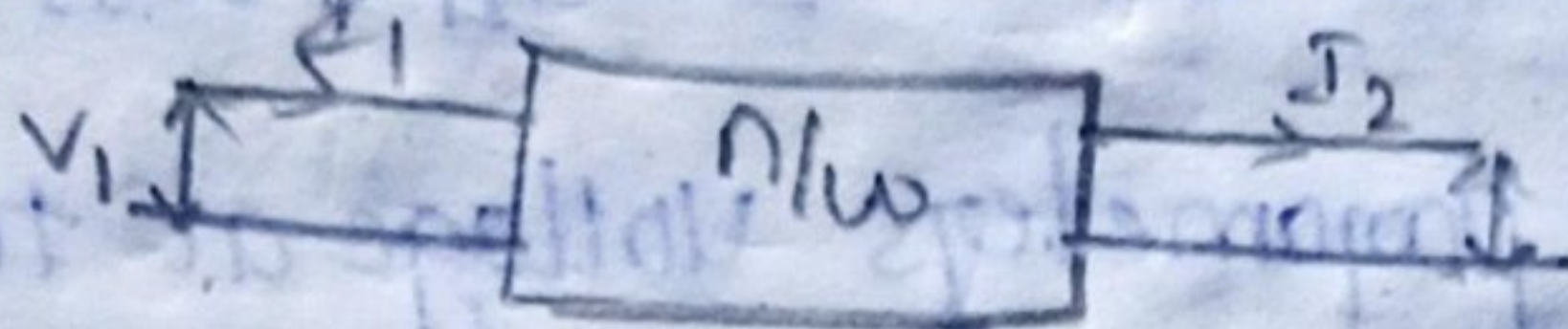case (i) port 2 short circuit i.e. $V_2 = 0$



$$(1) \Rightarrow V_1 = AV_2 + B(-I_2)$$

$$V_1 = 0 + B(-I_2)$$


$$B = \frac{V_1}{-I_2}$$

$$(2) \Rightarrow I_1 = CV_2 + D(-I_2)$$

$$I_1 = 0 + D(-I_2)$$

$$D = \frac{I_1}{-I_2}$$

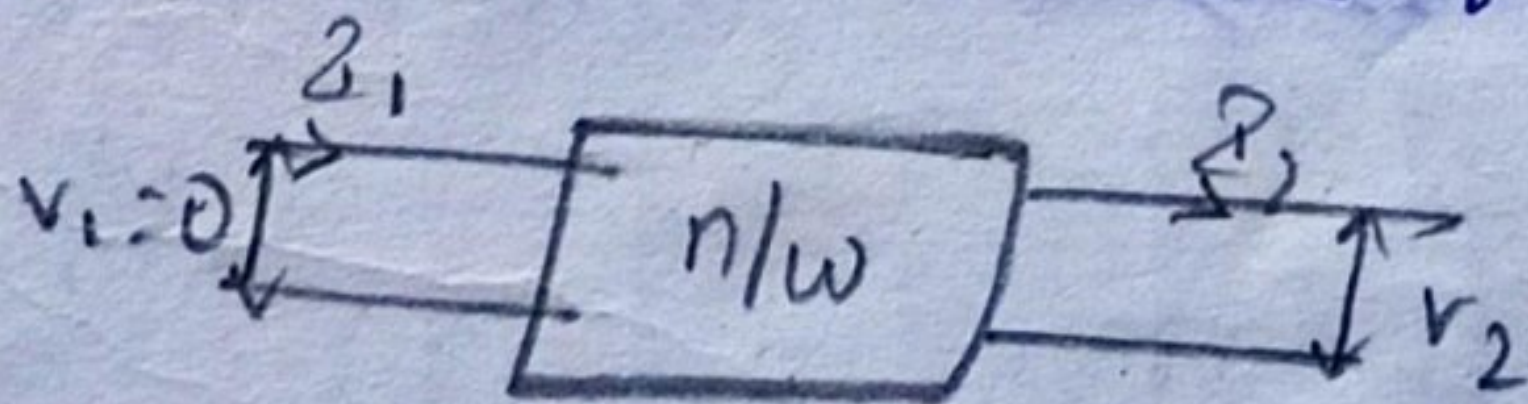case (ii) port 1 is short circuit i.e. $V_1 = 0$



$$(1) \Rightarrow V_1 = AV_2 + B(-I_2)$$

$$V_1 = AV_2 + B(0)$$

$$V_1 = AV_2$$

$$A = \frac{V_1}{V_2}$$

$$AD - BC = 1$$

$$A = 0$$


$$(2) \Rightarrow I_1 = CV_2 + D(-I_2)$$

$$I_1 = CV_2 + D(0)$$

$$I_1 = CV_2$$

$$C = \frac{I_1}{V_2}$$

H-parameters:

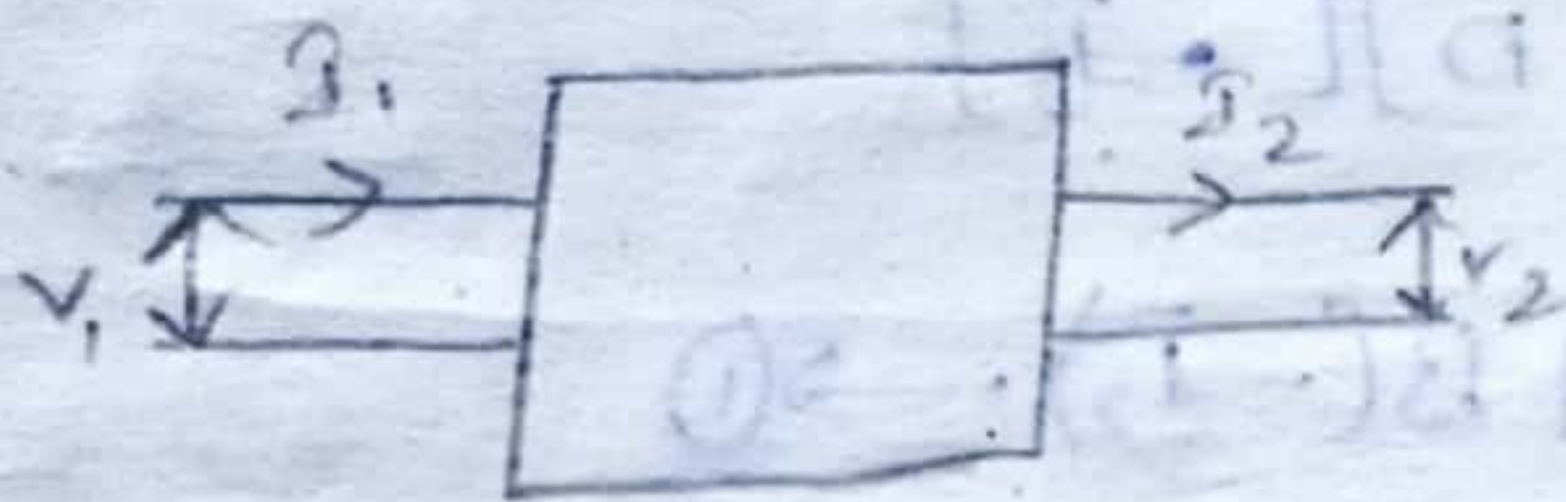

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

In hybrid parameters voltage at the transmitting end & current at the receiving end are expressed in terms of voltage & current at a receiving end and transmitting end respectively

Case (i) and short ckt i.e. $V_2 = 0$

$$\textcircled{1} \rightarrow V_1 = h_{11} I_1 + h_{12}(0)$$

$$V_1 = h_{11} I_1$$

$$h_{11} = \frac{V_1}{I_1}$$

$$\textcircled{2} \Rightarrow I_2 = h_{21} I_1 + h_{22}(0)$$

$$I_2 = h_{21} I_1$$

$$h_{21} = \frac{I_2}{I_1}$$

Case (ii) 1st port is open $I_1 = 0$

$$\textcircled{1} \Rightarrow V_1 = h_{11} I_1 + h_{12} V_2$$

$$V_1 = h_{12} V_2$$

$$h_{12} = \frac{V_1}{V_2}$$

$$\textcircled{2} \Rightarrow I_2 = h_{21} I_1 + h_{22} V_2$$

$$I_2 = h_{22} V_2$$

3-11-22

$$h_{22} = \frac{I_2}{V_2}$$

Inverse transmission line / inverse ABCD parameters

$$V_2 = A'V_1 + B'(-I_1) \rightarrow (1)$$

$$I_2 = C'V_1 + D'(-I_1) \rightarrow (2)$$

case (i) port is short $V_1 = 0$

$$V_2 = A'(0) - B'I_1$$

$$B' = \frac{-V_2}{I_1}$$

$$(2) \Rightarrow I_2 = C'(0) - D'I_1$$

$$D = \frac{-I_2}{I_1}$$

case (ii) $I_1 = 0$

$$(1) \Rightarrow V_2 = A'V_1 + B'(0)$$

$$V_2 = A'V_1$$

$$A' = \frac{V_2}{V_1}$$


$$(2) \Rightarrow I_2 = C'V_1 - D'(0)$$

$$A'O' - B'C' = 1$$

$$A' = O'$$

$$C' = \frac{I_2}{V_1}$$

Inverse H parameters

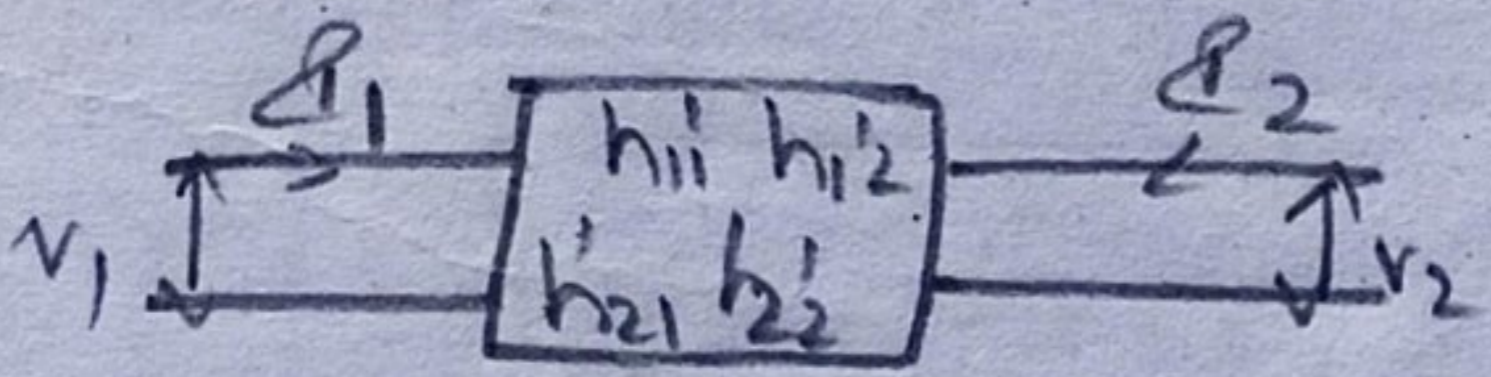

$$I_1 = h_{11}'V_1 + h_{12}'I_2$$

$$V_2 = h_{21}'V_1 + h_{22}'I_2$$

case (i) 1st port is short $V_1 = 0$

$$(1) \Rightarrow I_1 = h_{11}'(0) + h_{12}'I_2$$

$$h_{12}' = \frac{I_1}{I_2}$$

$$\textcircled{2} \Rightarrow v_2 = h'_{21}(0) + h'_{22} \delta_2$$

$$v_2 = h'_{22} \delta_2$$

$$h'_{22} = \frac{v_2}{\delta_2}$$

Case (ii) δ_2 and port is open $v_2 = 0$

$$\textcircled{1} \Rightarrow \delta_1 = h'_{11} v_1 + h'_{12} \delta_2$$

$$v_2 = h'_{21} v_1 + h'_{22} \delta_2$$

$$\textcircled{1} \Rightarrow \delta_1 = h'_{11}(v_1) + h'_{12}(0)$$

$$h'_{11} = \frac{\delta_1}{v_1}$$

$$\textcircled{2} \Rightarrow v_2 = h'_{21}(v_1) + h'_{22}(0)$$

$$h'_{21} = \frac{v_2}{v_1}$$

Inter relationship between different parameters:

1. Y-parameters in terms of Z-parameters:

$$V = Z I \Rightarrow V = Z \left[\frac{1}{Y} \right] \therefore Z = \frac{1}{Y}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

$$\therefore \delta_1 = \frac{\begin{bmatrix} V_1 & z_{12} \\ V_2 & z_{22} \end{bmatrix}}{\Delta Z}$$

$$\delta_1 = \frac{V_1 z_{22} - V_2 z_{12}}{\Delta Z}$$

$$\delta_1 = V_1 \left[\frac{z_{22}}{\Delta Z} \right] + V_2 \left[\frac{-z_{12}}{\Delta Z} \right] \Rightarrow V_1 \left[\frac{z_{22}}{\Delta Z} \right] \pm V_2 \left[\frac{-z_{12}}{\Delta Z} \right]$$

$$I_1 = v_1 y_{11} + v_2 y_{12}$$

$$\therefore y_{11} = \frac{z_{22}}{\Delta z} \quad y_{12} = \frac{-z_{12}}{\Delta z}$$

$$\text{from } \bar{I}_2 = \frac{\begin{vmatrix} z_{11} & v_1 \\ z_{21} & v_2 \end{vmatrix}}{\Delta z}$$

$$\bar{I}_2 = \frac{z_{11}v_2 - z_{21}v_1}{\Delta z}$$

$$\bar{I}_2 = v_2 \left[\frac{z_{11}}{\Delta z} \right] + v_1 \left[\frac{-z_{21}}{\Delta z} \right]$$

$$\bar{I}_2 = v_1 \left[\frac{-z_{21}}{\Delta z} \right] + v_2 \left[\frac{z_{11}}{\Delta z} \right]$$

$$\therefore \bar{I}_2 = v_1 y_{21} + v_2 y_{22}$$

$$\therefore y_{21} = \frac{-z_{21}}{\Delta z} \quad y_{22} = \frac{z_{11}}{\Delta z}$$

$$Y = \frac{1}{z}$$

$$z^{-1} = Y$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}^{-1}$$

$$= \frac{1}{\Delta z} \begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} \frac{z_{22}}{\Delta z} & \frac{-z_{12}}{\Delta z} \\ \frac{-z_{21}}{\Delta z} & \frac{z_{11}}{\Delta z} \end{bmatrix}$$

$$y_{11} = \frac{z_{22}}{\Delta z} \quad y_{12} = \frac{-z_{12}}{\Delta z}$$

$$y_{21} = \frac{-z_{21}}{\Delta z} \quad y_{22} = \frac{z_{11}}{\Delta z}$$

2 parameters in terms of Y-parameters

$$V = IZ \Rightarrow V = Z \frac{1}{Y}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$V_1 = \frac{\begin{vmatrix} I_1 & Y_{12} \\ I_2 & Y_{22} \end{vmatrix}}{\Delta Y}$$

$$V_1 = \frac{I_1 Y_{22} - I_2 Y_{12}}{\Delta Y}$$

$$V_1 = Z_1 \left[\frac{Y_{22}}{\Delta Y} \right] + Z_2 \left[\frac{-Y_{12}}{\Delta Y} \right]$$

$$V_1 = Z_1 z_{11} + Z_2 z_{12}$$

$$\therefore z_{11} = \frac{Y_{22}}{\Delta Y} \quad z_{12} = \frac{-Y_{12}}{\Delta Y}$$

$$V_2 = \frac{\begin{vmatrix} Y_{11} & I_1 \\ Y_{21} & I_2 \end{vmatrix}}{\Delta Y}$$

$$V_2 = \frac{Y_{11} I_2 - I_1 Y_{21}}{\Delta Y}$$

$$V_2 = Z_1 \left[\frac{-Y_{21}}{\Delta Y} \right] + Z_2 \left[\frac{Y_{11}}{\Delta Y} \right]$$

$$V_2 = Z_1 z_{21} + Z_2 z_{22}$$

$$\therefore z_{21} = \frac{-Y_{21}}{\Delta Y} \quad z_{22} = \frac{Y_{11}}{\Delta Y}$$

Z parameters in terms of ABCD - parameters.

ABCD parameters

$$V_1 = AV_2 + B(-I_2) \rightarrow (1)$$

$$I_1 = CV_2 + D(-I_2) \rightarrow (2)$$

Converts Z-parameters.

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow (3)$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \rightarrow (4)$$

$$(2) \Rightarrow CV_2 = I_1 + DI_2$$

$$V_2 = I_1 \left(\frac{1}{C}\right) + I_2 \frac{D}{C} \rightarrow (5)$$

Compare above eq (5) into eq (4)

$$Z_{21} = \frac{1}{C} \quad Z_{22} = \frac{D}{C}$$

(1) \Rightarrow Sub eq (5) in eq (1)

$$V_1 = A \left[I_1 \left(\frac{1}{C}\right) + I_2 \left(\frac{D}{C}\right) \right] + B(-I_2)$$

$$V_1 = A I_1 \left(\frac{1}{C}\right) + I_2 \left(\frac{AD}{C} - B\right)$$

$$V_1 = I_1 \left(\frac{A}{C}\right) + I_2 \left(\frac{AD}{C} - B\right)$$

$$Z_{11} = \frac{A}{C} \quad Z_{12} = \frac{AD}{C} - B$$

Z parameters in terms of H-parameters

$$V_1 = h_{11}I_1 + h_{12}V_2 \rightarrow (1)$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \rightarrow (2)$$

Converts Z-parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow (3)$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \rightarrow (4)$$

$$(2) \Rightarrow h_{22}V_2 = I_2 - h_{21}I_1$$

$$h_{22}V_2 = I_1[-h_{21}] + I_2$$

$$V_2 = Z_{11} \left[\frac{-h_{21}}{h_{22}} \right] + Z_{22} \left[\frac{1}{h_{22}} \right] \rightarrow (5)$$

$$\therefore Z_{21} = \frac{-h_{12}}{h_{22}}$$

$$Z_{22} = \frac{1}{h_{22}}$$

(1) \Rightarrow sub eq (5) in eq (1)

$$V_1 = h_{11} I_1 + h_{12} \left[Z_{11} \left(\frac{-h_{21}}{h_{22}} \right) + Z_{22} \left(\frac{1}{h_{22}} \right) \right]$$

$$V_1 = \left(h_{11} - \frac{h_{12} h_{21}}{h_{22}} \right) I_1 + \left(\frac{h_{12}}{h_{22}} \right) I_2$$

$$Z_{11} = h_{11} - \frac{h_{12} h_{21}}{h_{22}}$$

$$Z_{22} = \frac{h_{12}}{h_{22}}$$

Y-parameters in ABCD-parameters:

ABCD parameters.

$$V_1 = AV_2 + B(-I_2) \rightarrow (1)$$

$$I_1 = (V_2 + 0)(-I_2) \rightarrow (2)$$

converts of Y-parameters

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow (3)$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow (4)$$

$$(1) \rightarrow V_1 = AV_2 + B(-I_2)$$

$$V_1 - AV_2 = -BI_2$$


$$BI_2 = AV_2 - V_1$$

$$I_2 = V_1 \left(\frac{-1}{B} \right) + V_2 \left(\frac{A}{B} \right) \rightarrow (5) \text{ compare with eq (3)}$$

$$I_2 = V_1 Y_{21} + Y_{22} V_2$$

$$Y_{21} = \frac{-1}{B} \quad Y_{22} = \frac{A}{B}$$

eq (5) in eq (1)

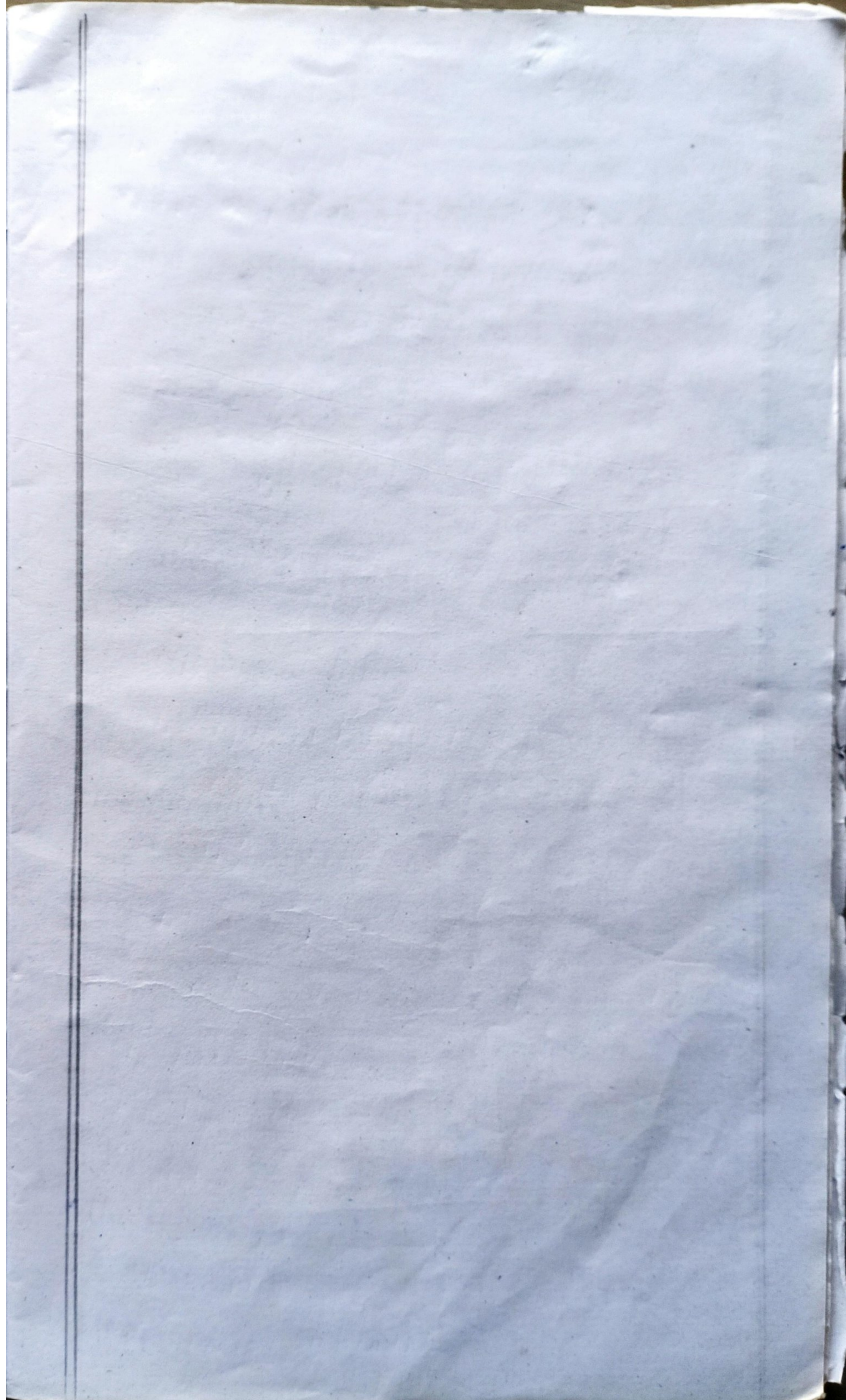

28-11-22

UNIT - V

FILTERS

Definition:-



An electric filter is a circuit which can be design to Modify, reshape or reject all the undesired ^{desired} frequency of an Electrical signal and pass only the desired signals (or)

We can define that an electrical filter usually frequency selective network. That passes a specify band of frequencies and ~~large~~ ^{log} signals of frequencies outside the band block

Classification of filters:-

- (a) low pass filter (b) High pass filter (c) Band pass filter ^{stop}
(d) Band stop filter

Low pass filter:-

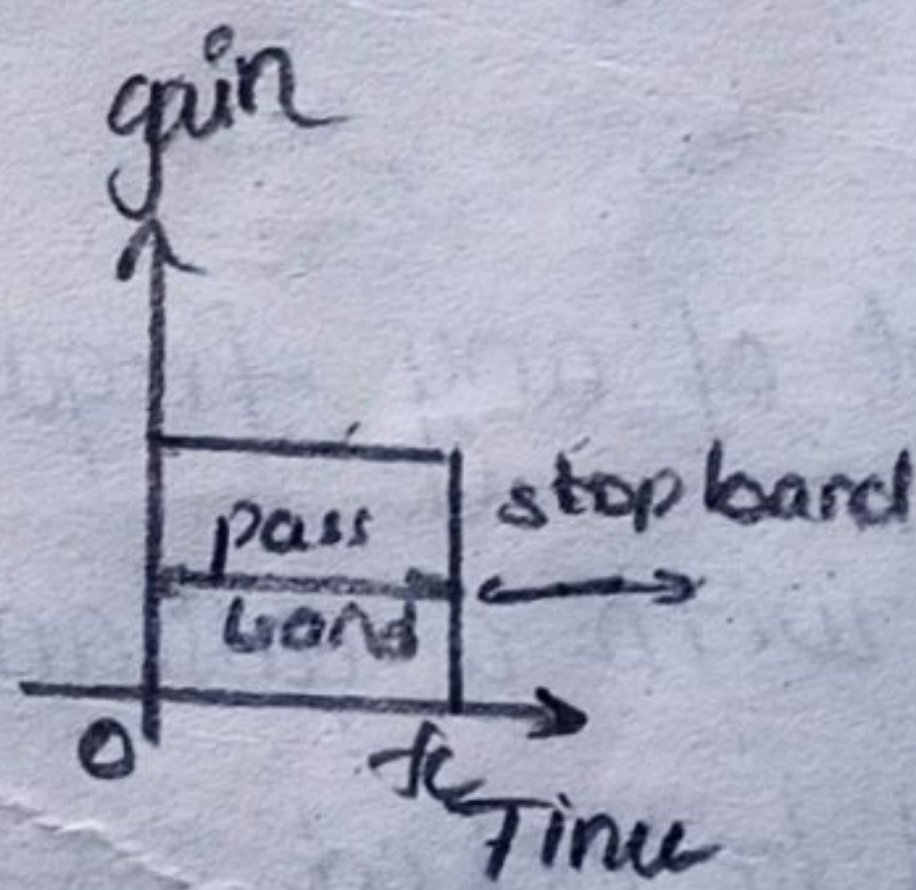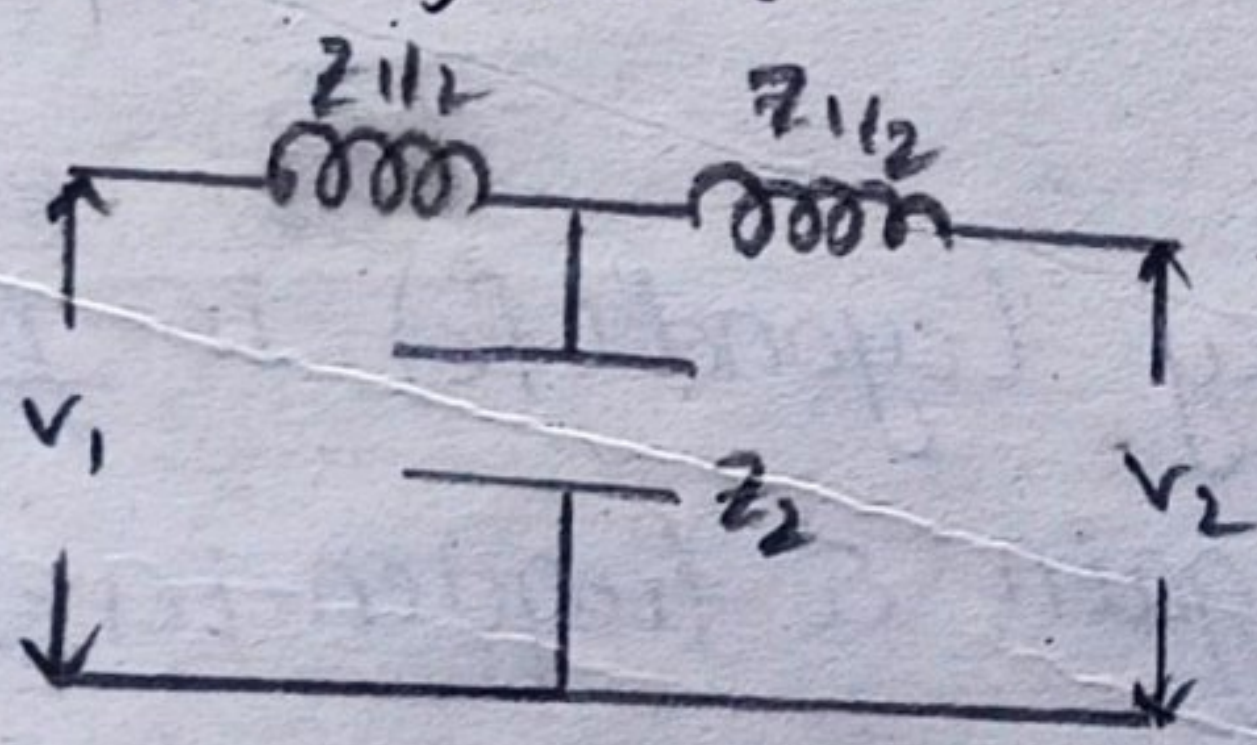

A filter that provides a constant o/p from DC upto a cutt off frequency (f_c) & then passes ^{no signal} above the frequency is called. ideal low pass filter



The voltage gain that is the ratio of output voltage to input voltage is constant over a frequency range from 0 to cutt off frequency (f_c). Hence the output

will be available from 0 to f_c with constant gain

The frequency between 0 & f_c are called as pass band frequency, by the frequency is above f_c are called as stop band frequency

\therefore The Bandwidth of low pass frequency is f_c

High pass filters:-

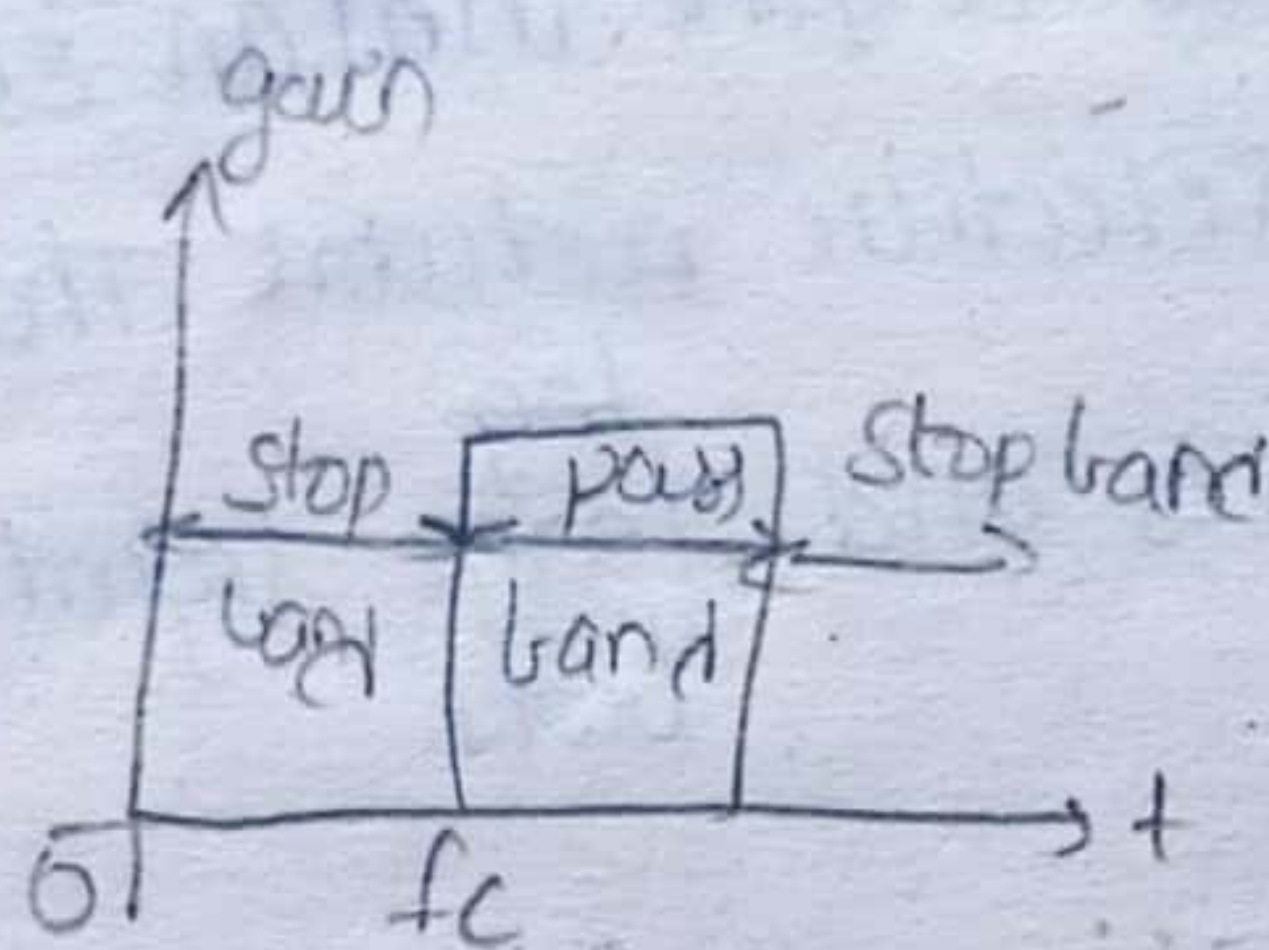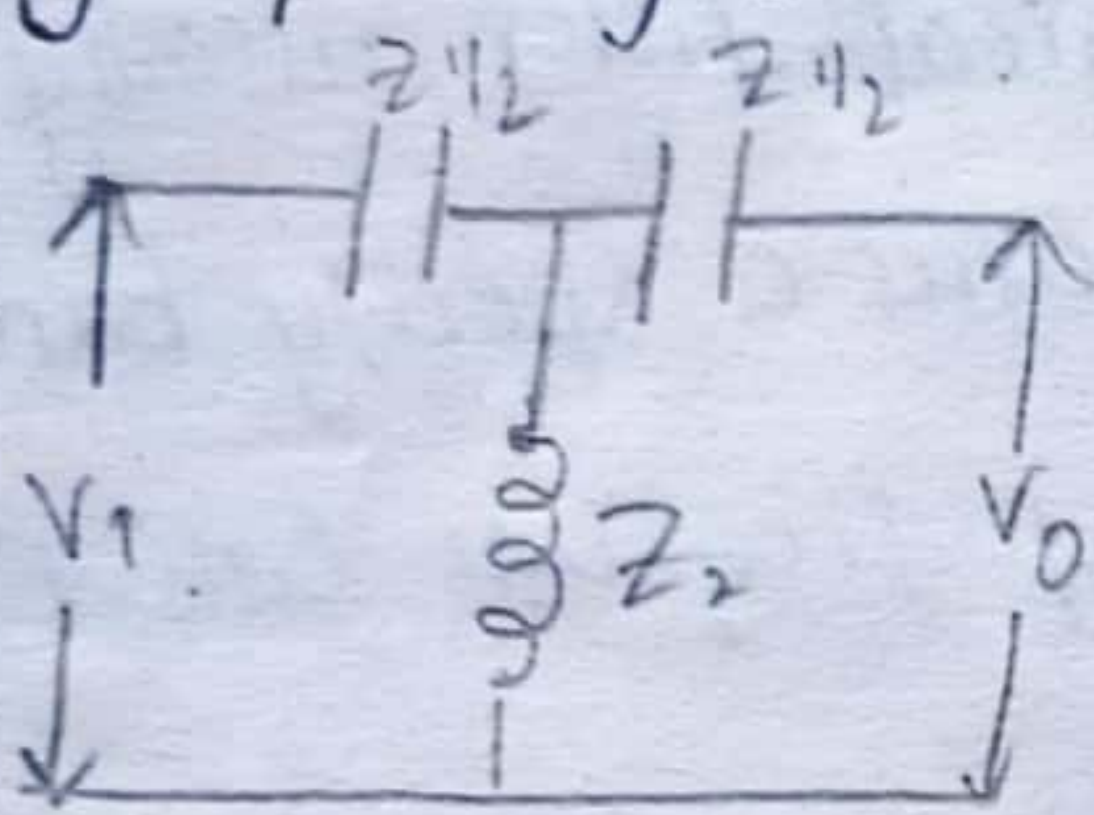


A filter that provides signal above a cut off frequency is a high pass filter

NOTE:-

Hence signal of any frequency beyond f_c is faithfully reproduced with a constant gain & frequencies from 0 to f_c will be 'locked dropped'

Band pass filters:-

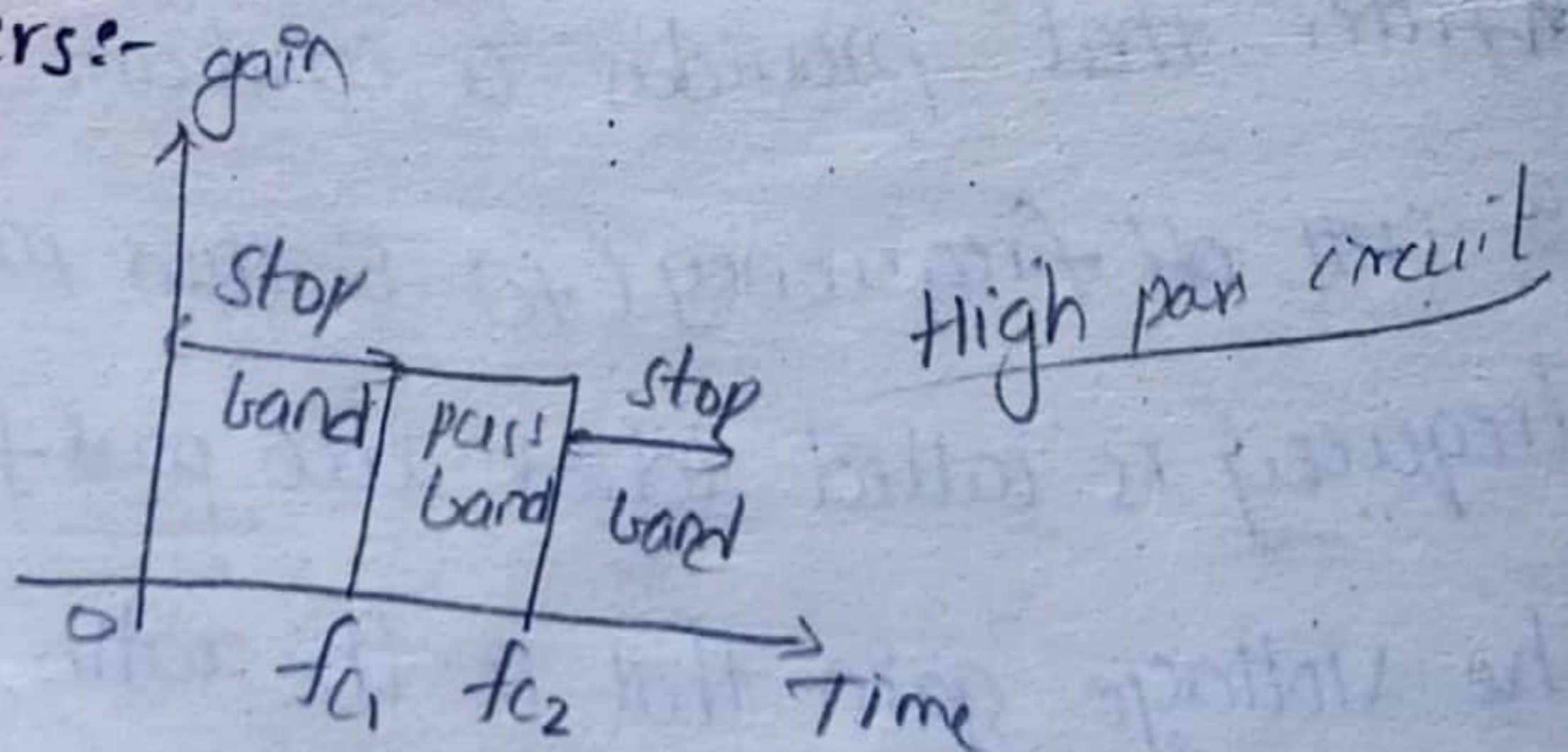

Band pass filters has a pass band b/w two cut off frequencies f_{c2} & f_{c1} & ~~two~~ where $f_{c2} > f_{c1}$


And two stop bands 0 to f_{c1} , $\Rightarrow 0 < f < f_{c1}$ &

$f > f_{c2}$

Band width of band pass filter is $f_{c2} - f_{c1}$

Where f_{c1} & f_{c2} are lower & higher cut off frequencies respectively

Band stop filters:-


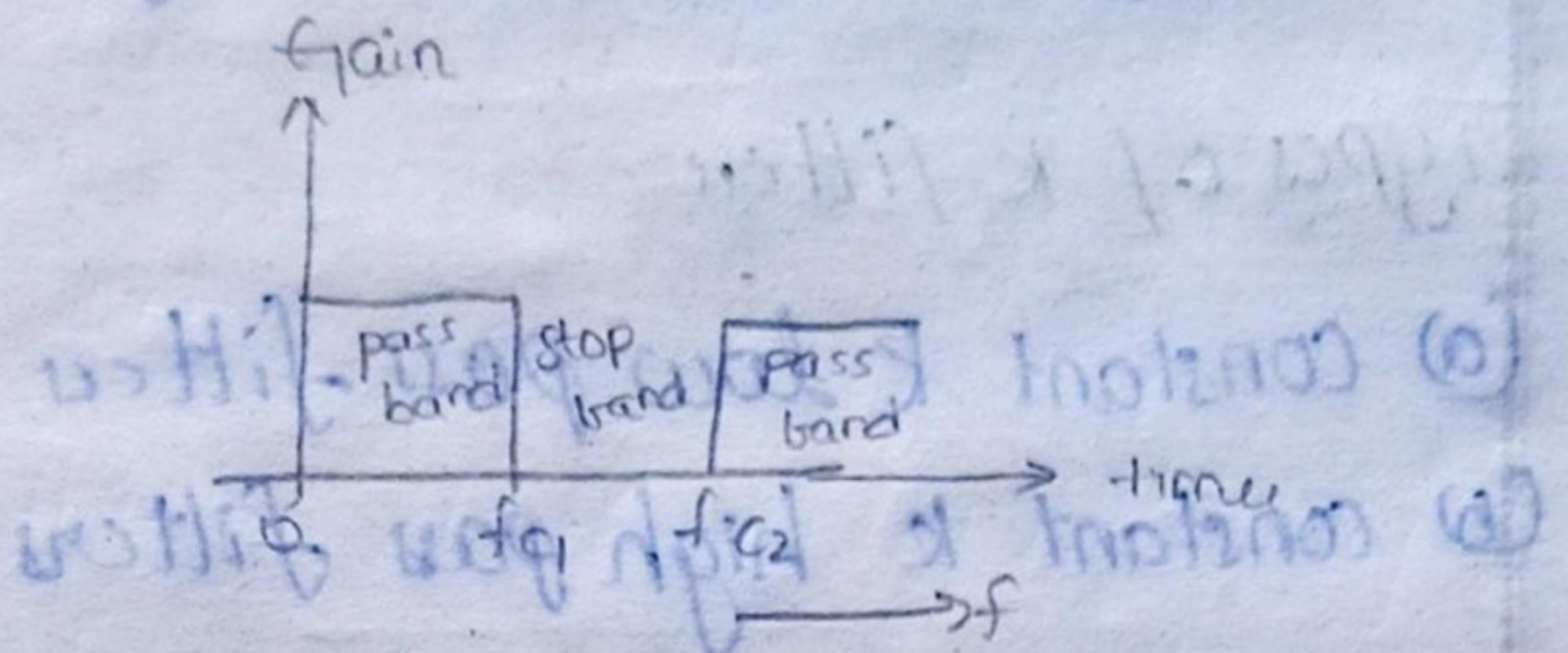


It has band stop between two cut off frequencies f_{c2} & f_{c1} . And two pass band $0 < f < f_{c1}$ & $f > f_{c2}$

This is called as band elimination or notch filter

Need of filter circuit:-

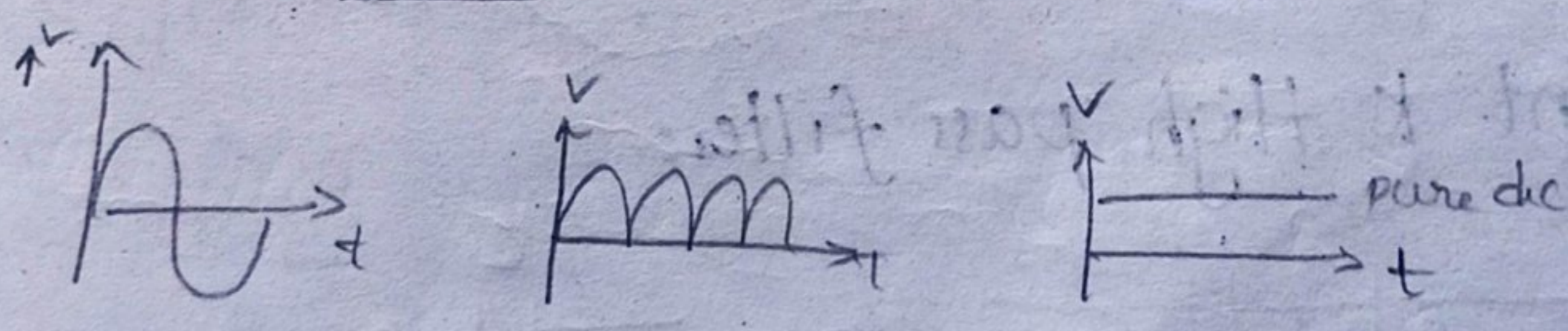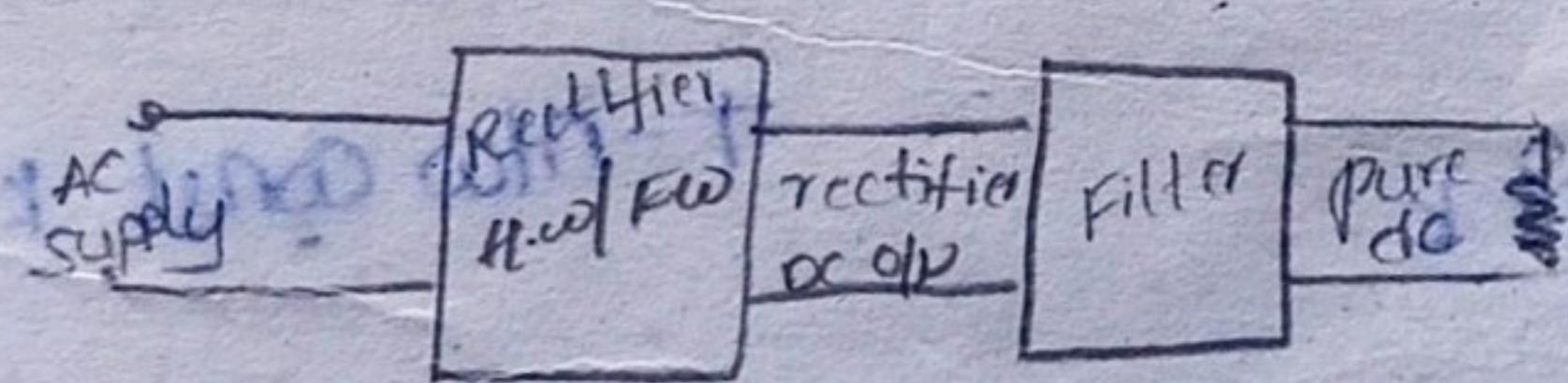- * Output obtain by rectifier circuit is pulsating dc
- * AC component present in o/p voltage is called as ripple
- * Our aim is to output should be ripple free (pure dc)




* capacitors and inductors are used for filter circuits

* Applications of filters

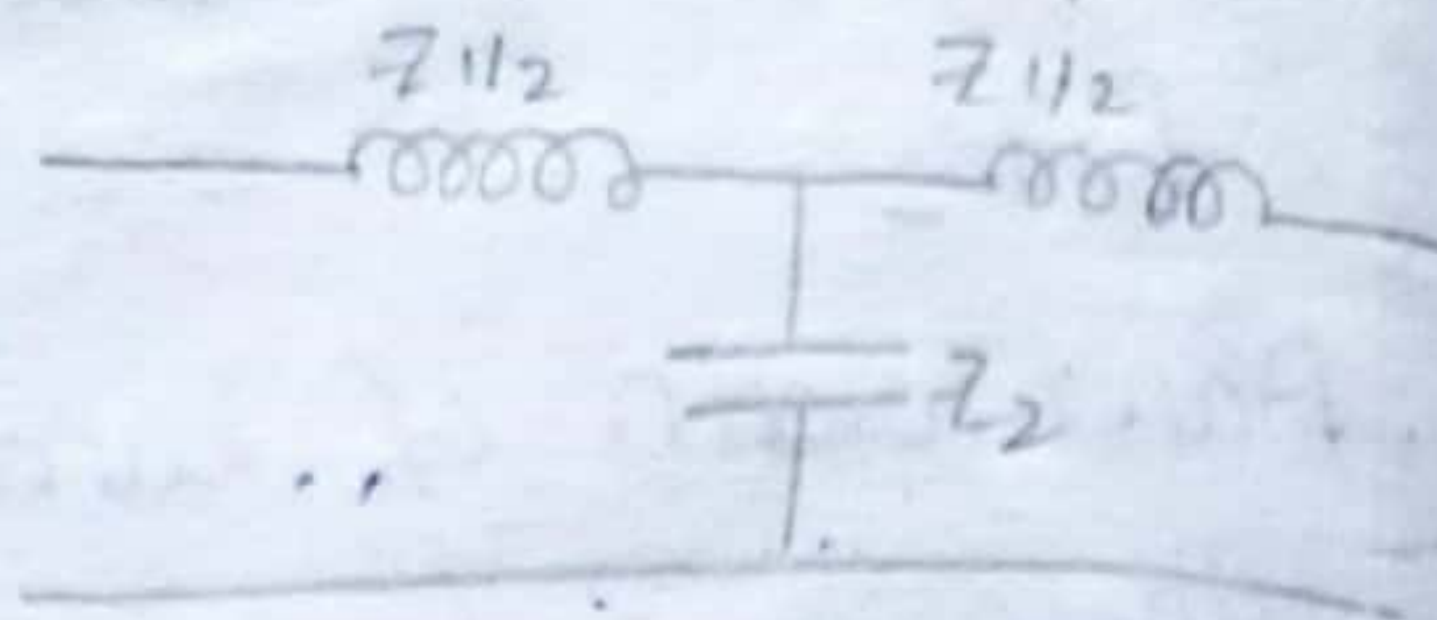- (1) constant \times filters.
- (2) M derive filters.
- (3) composite filters.

Constant k filters:

In this filter, the series & shunt impedances are such that



$$Z_1 \times Z_2 = R_0^2 = k [\text{constant}]$$

where R_0 = Real number & independent of frequency


→ This is called as designed/desired impedance.

Types of k filters:-


- (a) constant k low pass filters
- (b) constant k high pass filters

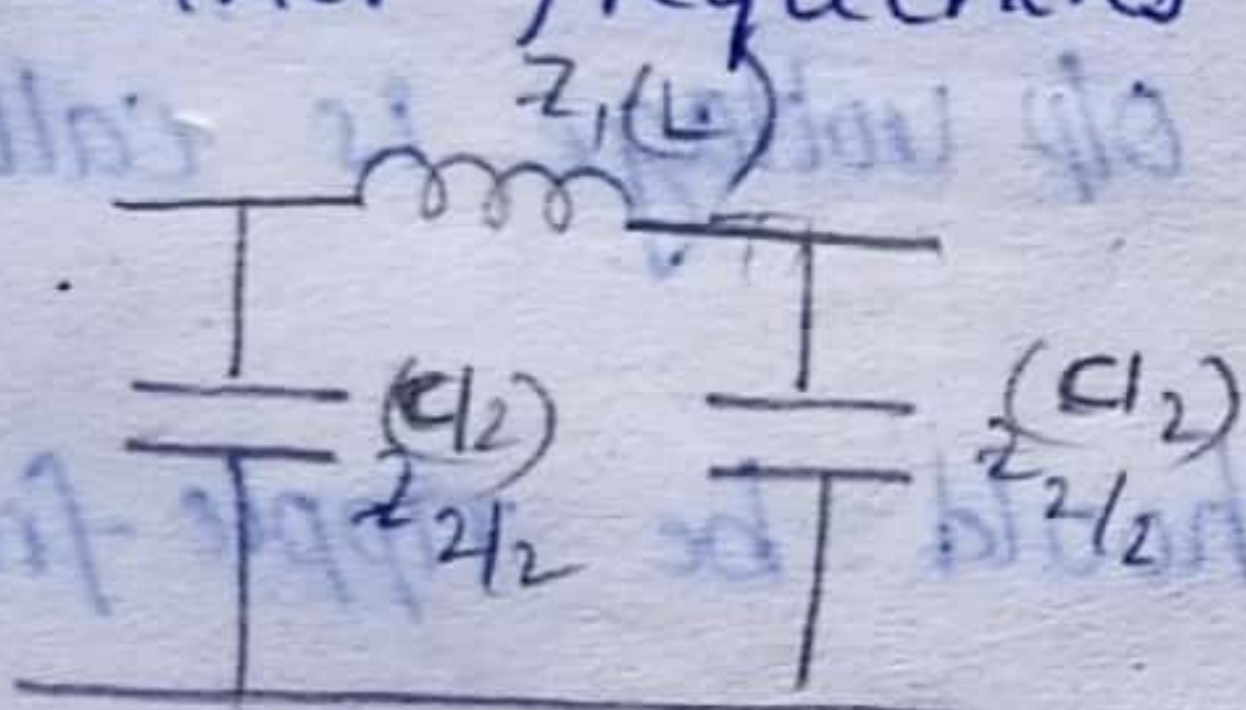(a) constant k low pass filters:-

It is the simplest type of filter which allows the all frequencies upto the specify cut off frequencies to pass through it and attenuates attenuation all the other frequencies above the cut off frequency.





π network of const k LPF

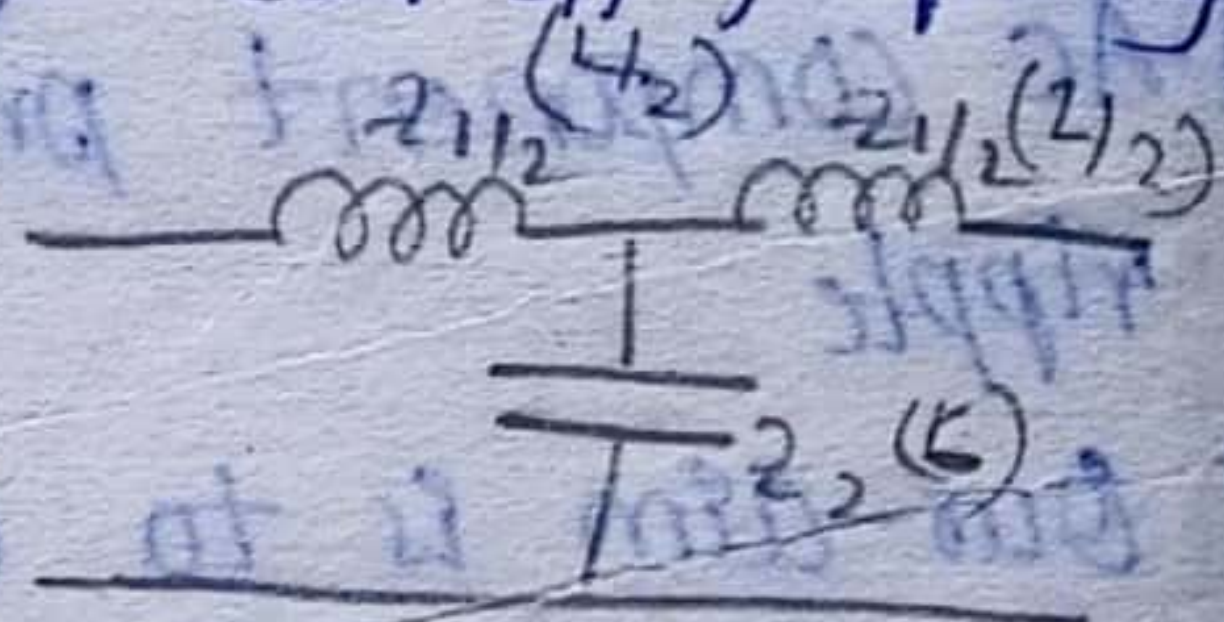


T-network const k LPF

Constant k High pass filter:-

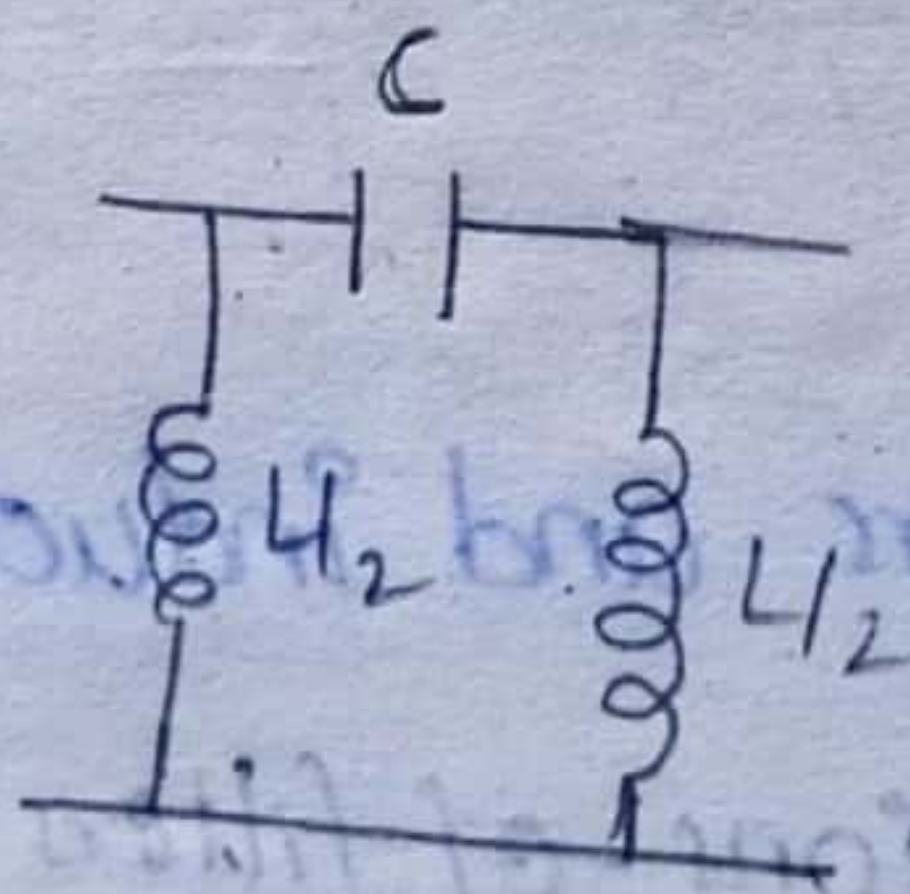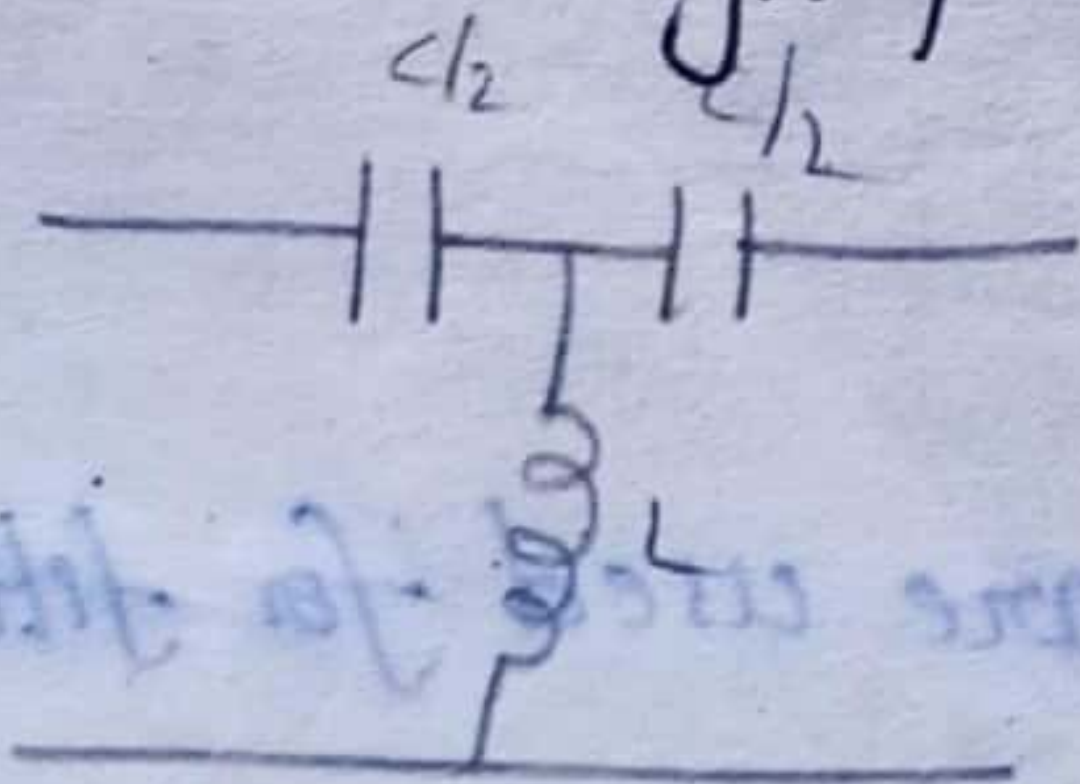


*] This filter attenuates all frequency below the cut off frequency and allow to pass all other frequencies above cut off frequency.

Analysis of constant k low pass filters:

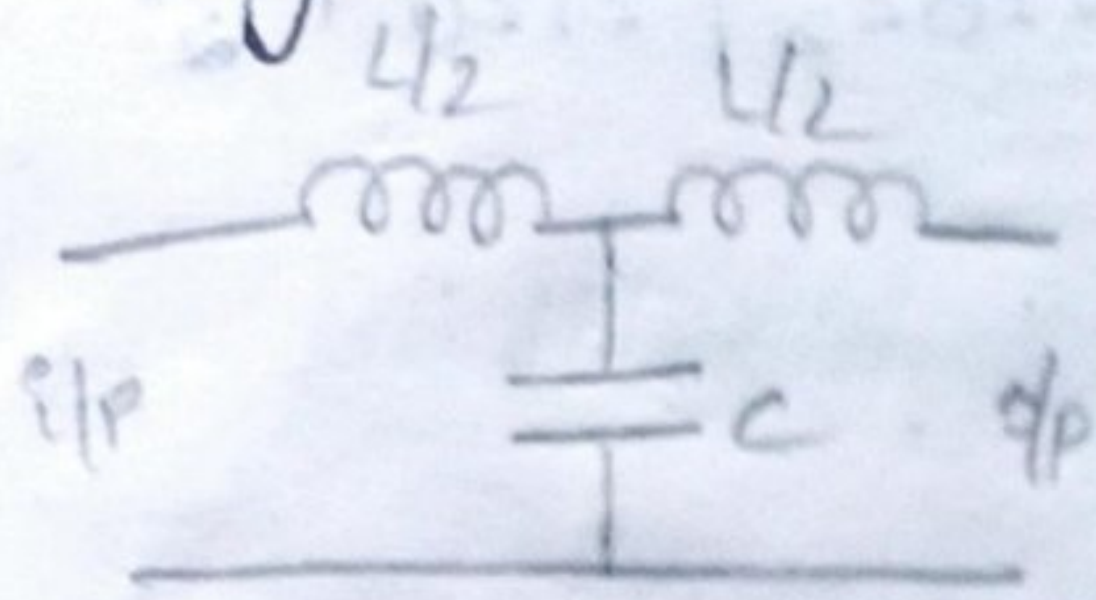

T network constant k

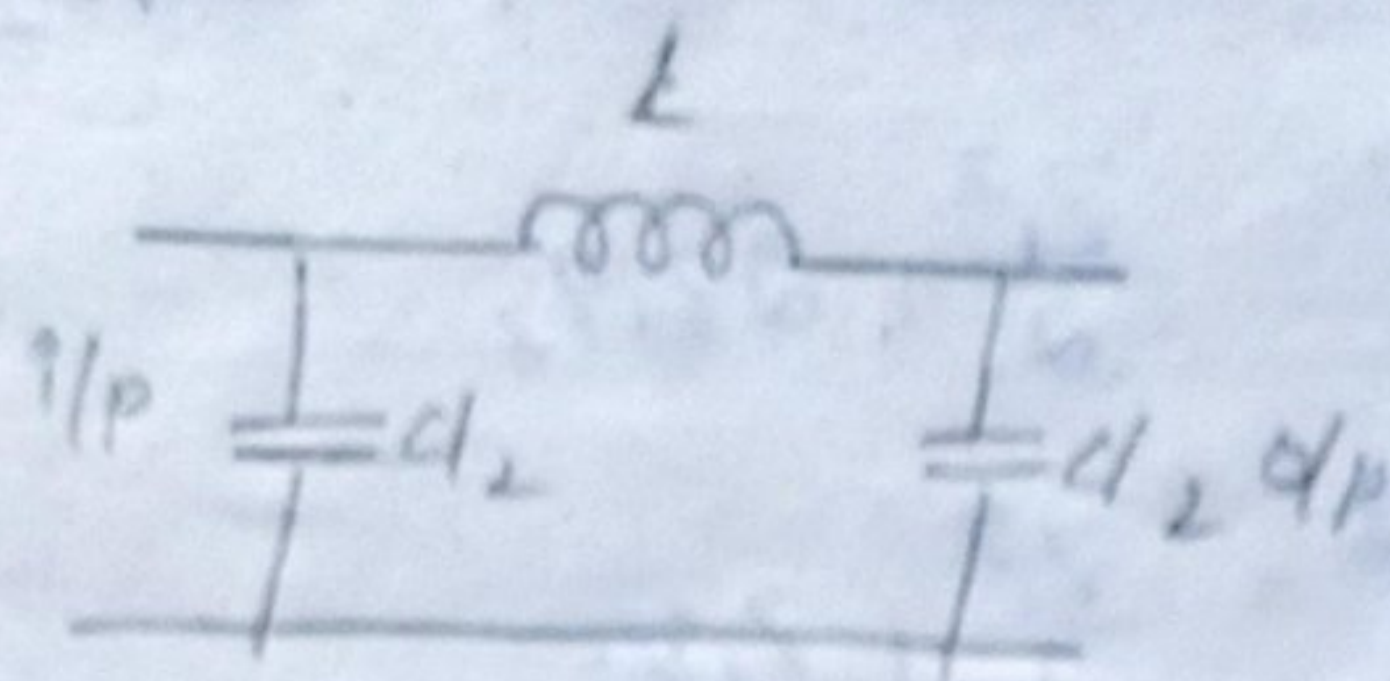


Π network constant k

-] from the figure T & Π section of low pass filters
-] Total Series impedance $Z_1 = j\omega L \times \frac{L}{2} \Rightarrow Z_1 = \frac{j\omega L^2}{2} \rightarrow (1)$
-] Total Shunt impedance $Z_2 = \frac{1}{j\omega C} = \frac{j}{\omega C} = \frac{-j}{\omega C} \rightarrow (2)$



Multiply eq (1) & eq (2)

$$\Rightarrow Z_1 \times Z_2 = j\omega L \times \frac{-j}{\omega C}$$
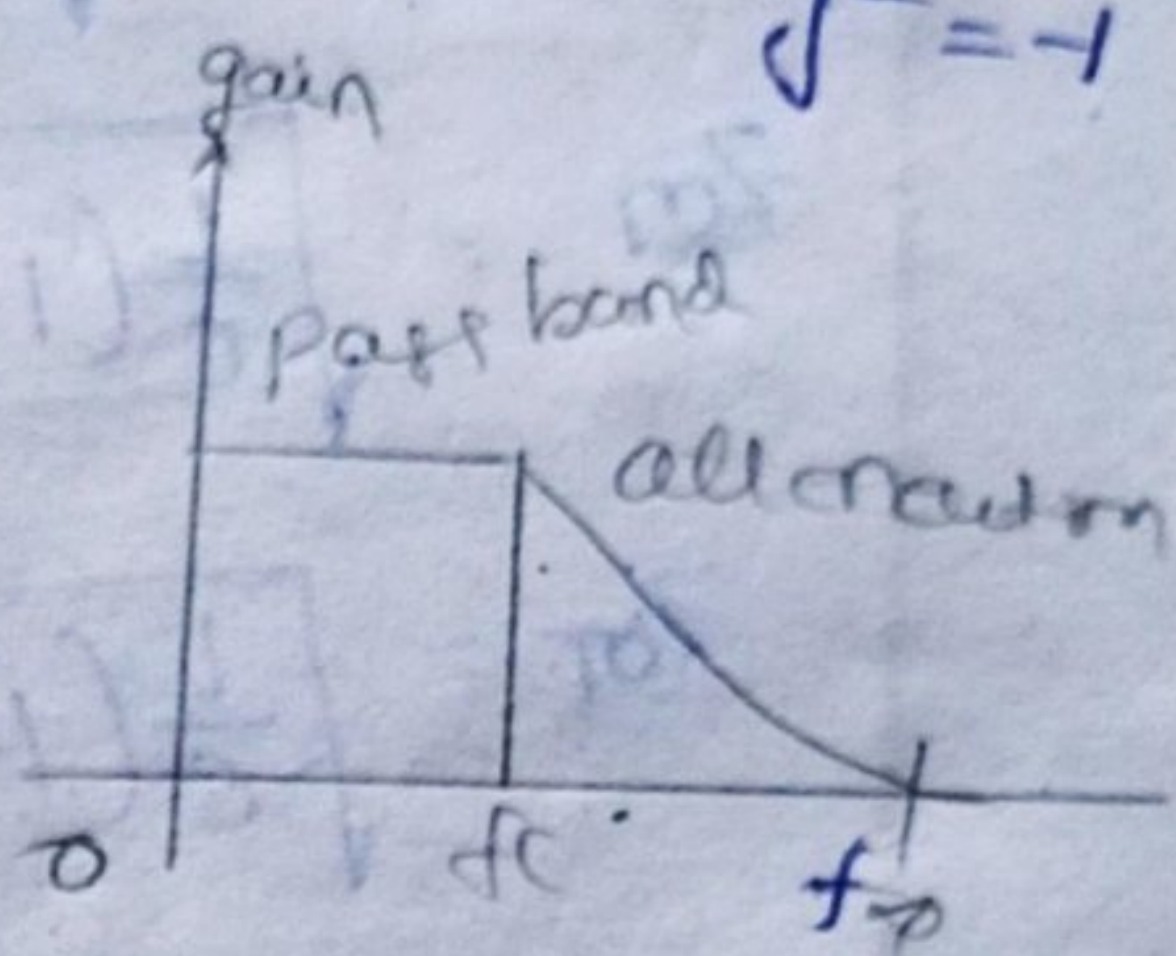
$$\boxed{Z_1 Z_2 = \frac{L}{C} = R_0^2 = k} \rightarrow (1)$$



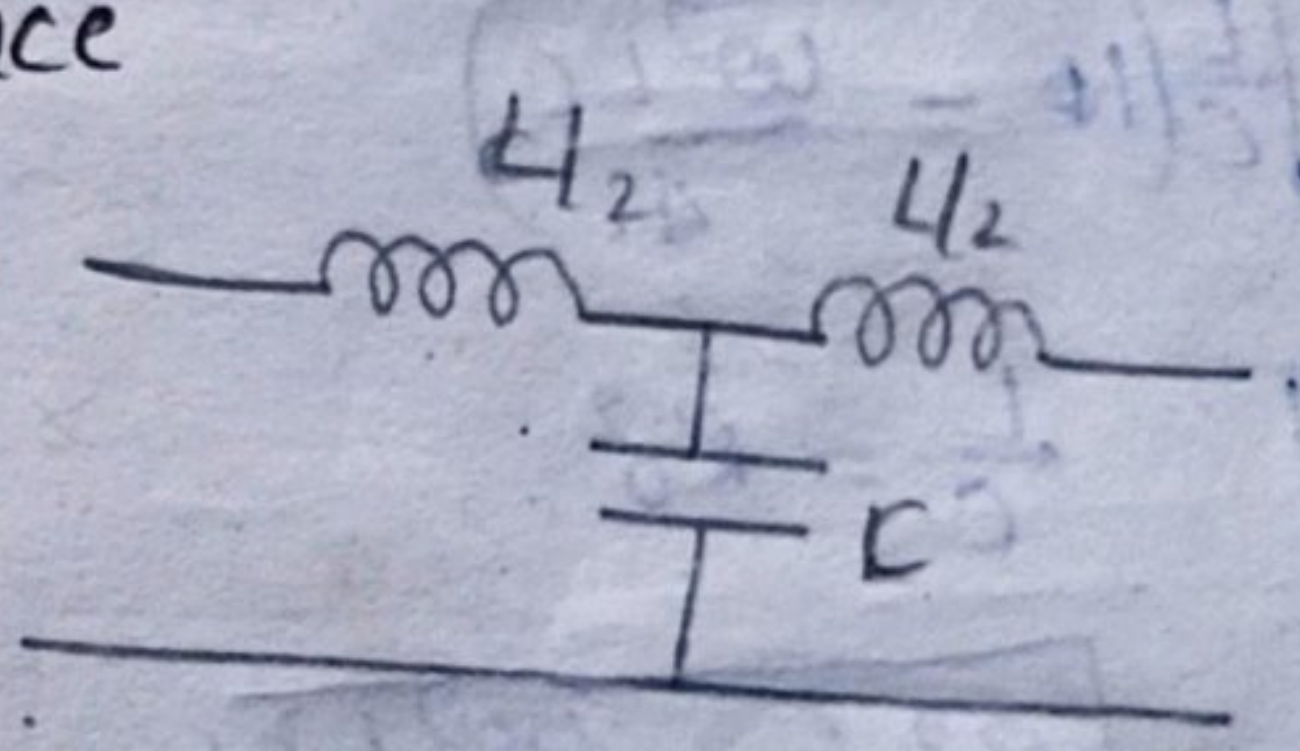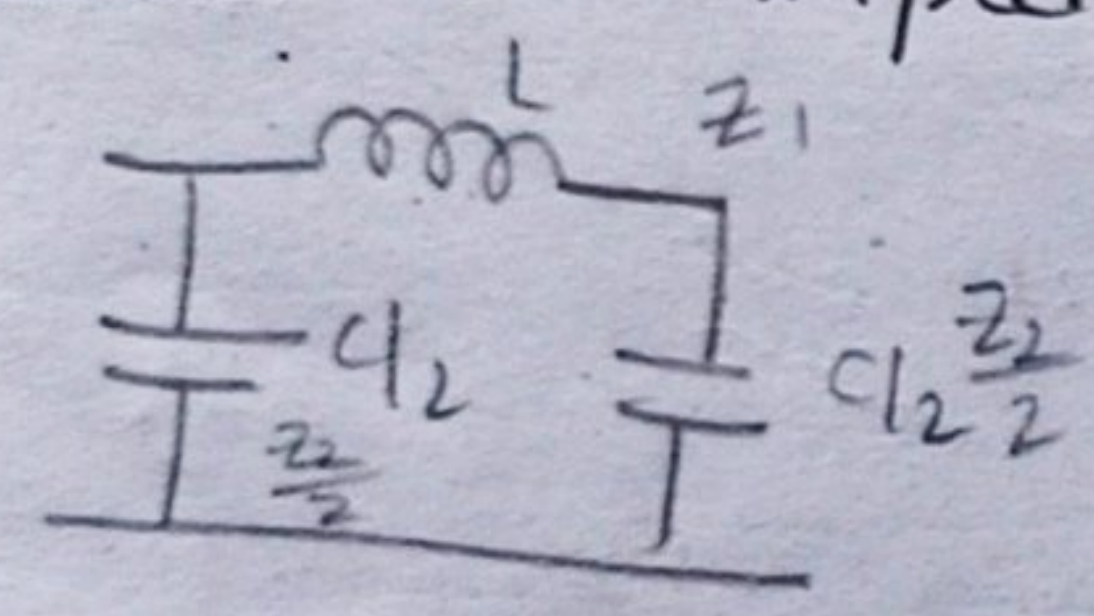Since $\frac{L}{C} = \text{Real quantity}$
characteristic impedance



$$Z_0 = \left[\left(Z_L + \frac{Z_1}{2} \right) \parallel Z_2 \right] + \frac{Z_1}{2}$$

$$Z_0 = \frac{\left(Z_L + \frac{Z_1}{2} \right) Z_2}{Z_L + \frac{Z_1}{2} + Z_2} + \frac{Z_1}{2}$$

$$Z_0 = \frac{2Z_L Z_2 + Z_1 Z_2 + Z_1 Z_L + \frac{Z_1^2}{2} + Z_1 Z_2}{2Z_L + 2Z_2 + Z_1}$$

$$Z_0 = \frac{2Z_1 Z_2 + 2Z_L Z_2 + Z_1 Z_L + \frac{Z_1^2}{2}}{2Z_L + 2Z_2 + Z_1}$$

$$2Z_0 Z_L + 2Z_0 Z_2 + Z_0 Z_1 = 2Z_1 Z_2 + 2Z_L Z_2 + Z_1 Z_L + \frac{Z_1^2}{2}$$

$$2z_0^2 + 2z_0z_2 + z_0z_1 = 2z_1z_2 + 2z_0z_2 + z_1z_0 + \frac{z_1^2}{2}$$

$$2z_0^2 = \frac{z_1^2}{2} + 2z_1z_2$$

$$z_0^2 = \frac{z_1^2}{4} + z_1z_2$$

$$z_0^2 = z_1z_2 \left(1 + \frac{z_1}{4z_2} \right)$$

$$z_0 = \sqrt{z_1z_2 \left(1 + \frac{z_1}{4z_2} \right)}$$

Characteristic impedance for T network z_0

$$z_{0T} = \sqrt{z_1z_2 \left(1 + \frac{z_1}{4z_2} \right)} \rightarrow \textcircled{4}$$

$$z_{0T} = \sqrt{\frac{L}{C} \left(1 + \frac{z_1}{z_2} \right)}$$

$$z_{0T} = \sqrt{\frac{L}{C} \left(1 + \frac{j\omega L}{4} \frac{1}{j\omega C} \right)}$$

$$z_{0T} = \sqrt{\frac{L}{C} \left(1 - \frac{\omega^2 LC}{4} \right)}$$

$$\omega L \cdot k \cdot T \quad \frac{L}{C} = R_0^2$$

$$z_{0T} = \sqrt{R_0^2 \left(1 - \frac{\omega^2 LC}{4} \right)}$$

$$z_{0T} = R_0 \sqrt{\left(1 - \frac{\omega^2 LC}{4} \right)}$$

$$= R_0 \sqrt{1 - \frac{\omega^2}{4/LC}}$$

$\omega_c^2 = \frac{4}{LC}$ Angular cut off frequency

$$= R_0 \sqrt{1 - \frac{\omega^2}{\omega_c^2}}$$

cut off frequency will be at particular condition

$$1 - \frac{\omega^2}{\omega_c^2} = 0$$

$$1 = \frac{\omega^2}{\omega_c^2}$$

$$\omega^2 = \frac{4}{LC}$$

$$\omega_c^2 = \frac{4}{LC}$$

$$Z_{01} = R_0 \sqrt{1 - \frac{(2\pi f)^2}{(2\pi f_c)^2}}$$

$$Z_{01} = R_0 \sqrt{1 - \left(\frac{f}{f_c}\right)^2}$$

$$Z_0 = \left[\left(Z_L \parallel \frac{Z_2}{2} \right) + Z_1 \right] \parallel \frac{Z_2}{2}$$

$$Z_0 = \left[\frac{\left(Z_L \frac{Z_2}{2} \right)}{\left(Z_L + \frac{Z_2}{2} \right)} + Z_1 \right] \parallel \frac{Z_2}{2}$$

$$Z_0 = \frac{\frac{Z_L Z_2}{2} + Z_1 \left(Z_L + \frac{Z_2}{2} \right)}{\left(Z_L + \frac{Z_2}{2} \right)} \parallel \frac{Z_2}{2}$$

$$Z_0 = \left[\frac{Z_L \frac{Z_2}{2} + Z_1 Z_L + \frac{Z_1 Z_2}{2}}{Z_L + \frac{Z_2}{2}} \right] \parallel \frac{Z_2}{2}$$

$$Z_0 = \frac{\left(Z_L \frac{Z_2}{2} + Z_1 Z_L + \frac{Z_1 Z_2}{2} \right) \frac{Z_2}{2}}{\left(Z_L + \frac{Z_2}{2} \right)}$$

$$\frac{Z_L \frac{Z_2}{2} + Z_1 Z_L + \frac{Z_1 Z_2}{2}}{Z_L + \frac{Z_2}{2}} + \frac{Z_2}{2}$$

$$Z_0 = \frac{Z_L Z_2^2 + Z_1 Z_2 Z_L + Z_1 Z_2^2}{2 \left(Z_L + \frac{Z_2}{2} \right)}$$


$$\frac{2 \left[\left(Z_L \frac{Z_2}{2} \right) + \left(Z_1 Z_L \right) + \left(\frac{Z_1 Z_2}{2} \right) \right] + Z_2 \left(Z_L + \frac{Z_2}{2} \right)}{2 \left(Z_L + \frac{Z_2}{2} \right)}$$

$$Z_0 = \frac{Z_L Z_2^2 + Z_1 Z_2 Z_L + Z_1 Z_2^2}{2 \left(Z_L + \frac{Z_2}{2} \right)}$$

$$Z_0 \left(\frac{Z_2^2}{2} + 2 Z_1 Z_2 + 2 Z_1 Z_1 \right) = Z_L Z_2^2 + Z_1 Z_2 Z_L + Z_1 Z_2^2$$

$$Z_0 \left(\frac{Z_2^2}{2} + 2 Z_1 Z_2 + 2 Z_1 Z_1 \right) = Z_L Z_2^2 + Z_1 Z_2 Z_L + Z_1 Z_2^2$$
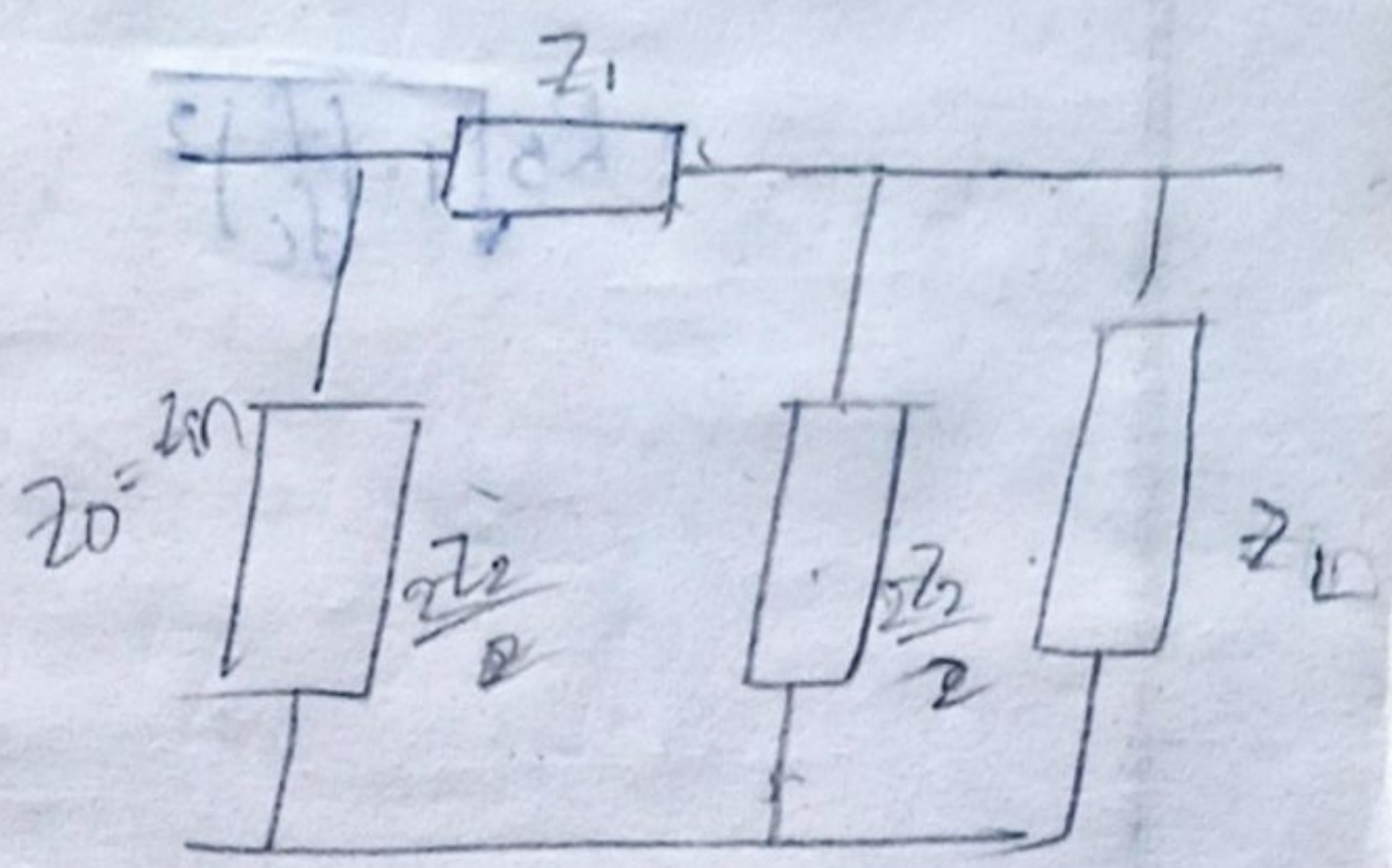
$$Z_0 \frac{Z_2^2}{2} + 2 Z_0 Z_2 + 2 Z_0 Z_1 = Z_L Z_2^2 + Z_1 Z_2 Z_L + Z_1 Z_2^2$$



Value of Z_{0T} for T system condition

$$Z_{0T} = R_0 \sqrt{1 - \frac{\omega^2 LC}{4}}$$

$$= R_0 \sqrt{1 - \left(\frac{f}{f_c}\right)^2}$$

If $\frac{\omega^2 LC}{4}$ is less than 1, Z_{0T} will be real and if $\frac{\omega^2 LC}{4}$ is greater than 1, Z_{0T} will be imaginary

Hence Z_{0T} will be characteristic impedance of pass band

When $\frac{\omega^2 LC}{4} < 1$ i.e. when Z_{0T} is real and Z_{0T} will be characteristic impedance for stop band when $\frac{\omega^2 LC}{4} > 1$ i.e. when Z_{0T} is imaginary.

for π system

$$Z_{0\pi} = \frac{Z_1 Z_2}{Z_{0T}}$$

$$Z_1 Z_2 = R_0^2$$

$$Z_{0T} = R_0 \sqrt{1 - \left(\frac{f}{f_c}\right)^2}$$

$$Z_{0\pi} = \frac{R_0^2}{R_0 \sqrt{1 - \left(\frac{f}{f_c}\right)^2}}$$

$$Z_{0\pi} = \frac{R_0}{\sqrt{1 - \left(\frac{f}{f_c}\right)^2}}$$


sharp

sharp

sharp

M-derived filters:-

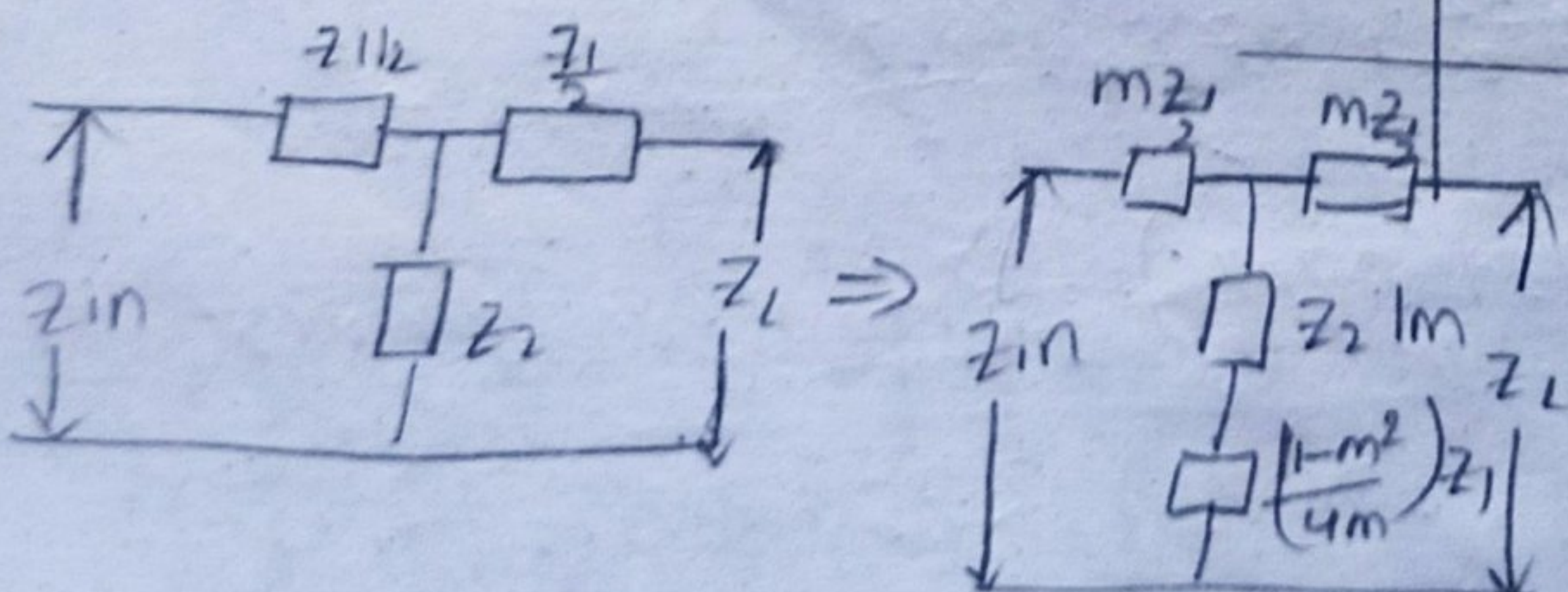- *] No sharp cut off between pass band & stop band
- *] characteristic impedance varies widely in the pass band from the derived value



Characteristic of M-derived filter:

When we find out R_o & f_c values we can easily design m-derived filter for T-network.

k
 $\frac{Z_1}{2}$

m-derived filter

$\frac{mZ_1}{2}$

Z_2

$\frac{Z_2}{m} + \left(\frac{1-m^2}{4m}\right)Z_1$

for π network

k
 Z_1

m-derived filter

$mZ_1 \parallel \left(\frac{4m}{1-m^2}\right)Z_2$


$2Z_2$

$\frac{2Z_2}{m}$

Composite filters: - (const k filter + m-derived filter +

Composite filter is made up of by cascading constant of k & m derived filters getting purified signal in addition with matching sections also

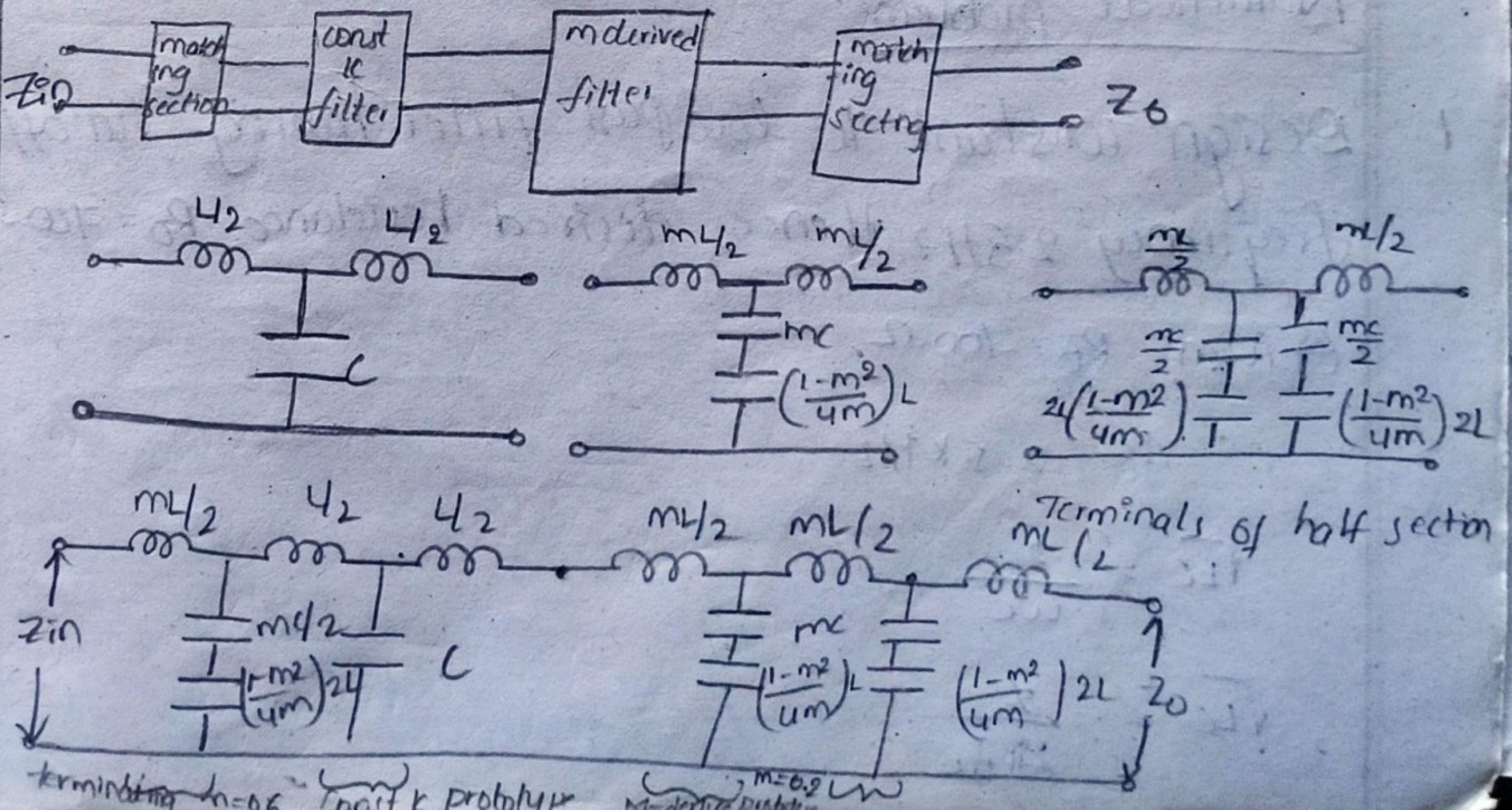Note that, the purpose matching section is to provide desired impedance statistics



Terminating half section with $m=0.6$


constant k prototype

Applications of low pass filters

- * They are used in electronic & power supply because they allow direct current but not the variations of the current & voltage
- * They are also used in voice frequency circuits which passes frequency upto 3kHz
- * They are used in transmitter & antenna for preventing high frequency from appearing field in antenna.
- * Uses of High pass filter:
 - * Modern digital image processing
 - * Sharpening the image

Sharpening

characteristics of composite filters

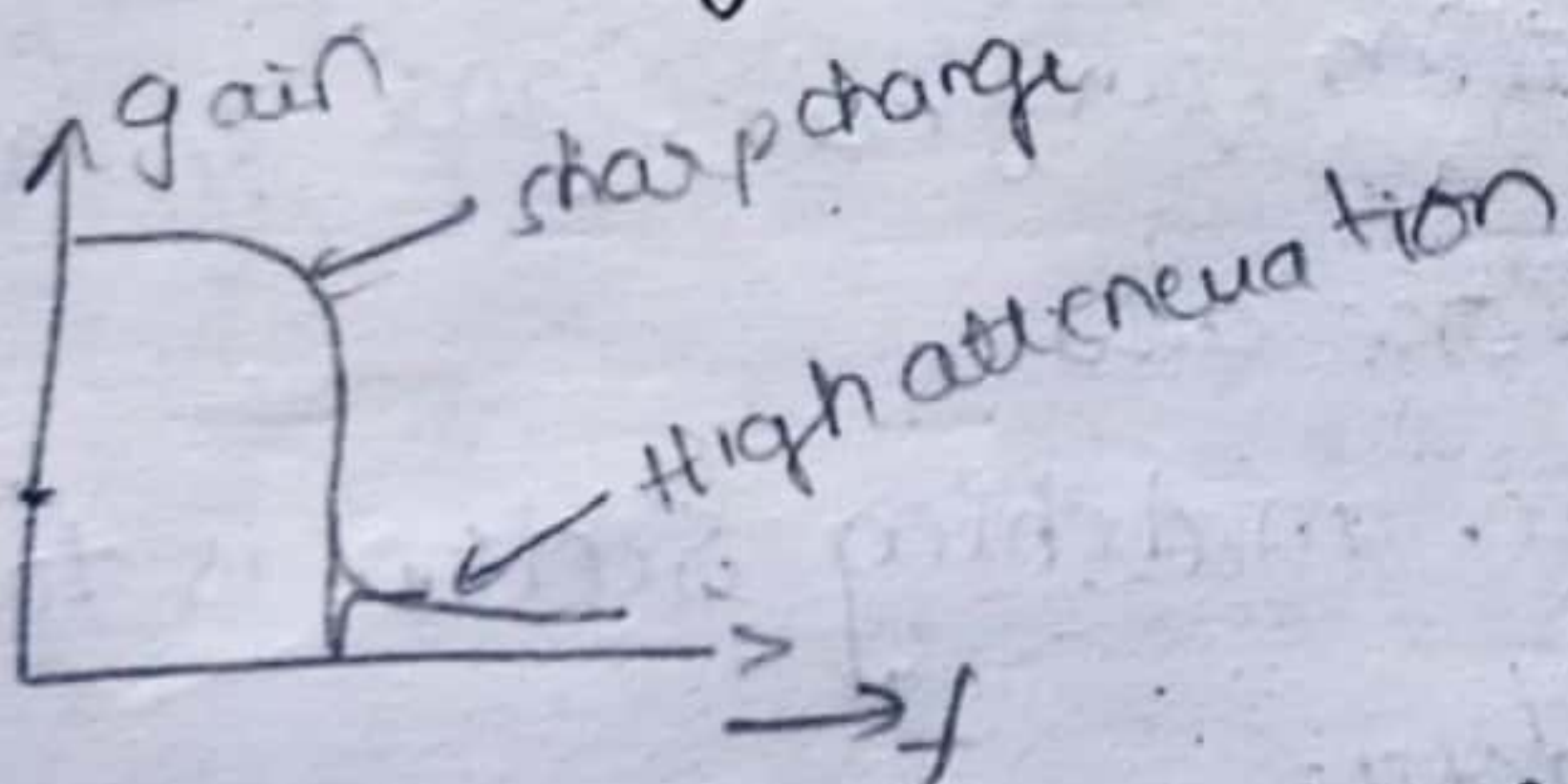

Numerical problems

800 827 3231

- 1 Design constant k low pass filter having cut'off frequency 2.5kHz Hence desired resistance $R_0 = 700 \Omega$

Given $R_0 = 700 \Omega$

$$f_c = 2.5 \text{ kHz}$$

$$\sqrt{LC} = \frac{2}{\omega c}$$

$$\sqrt{LC} = \frac{2}{2\pi f_c}$$

$$R_0^2 = L^2 = \frac{L}{C}$$

$$R_0 = \sqrt{\frac{L}{C}} \rightarrow (1)$$

$$\omega_c^2 = \frac{4}{LC}$$

$$\omega_c = \frac{2}{\sqrt{LC}}$$

$$\sqrt{\frac{L}{C}} \times \sqrt{LC} = R_0 \times \frac{1}{\pi f_c}$$

$$\sqrt{L^2} = \frac{R_0}{\pi f_c}$$

$$L = \frac{R_0}{\pi f_c} \quad \Bigg| \quad C = \frac{1}{\pi f_c R_0}$$

$$= R_0 \times \frac{1}{\pi f_c}$$

$$= \frac{700}{\pi \times 2.5 \times 10^3}$$

$$= \frac{1400}{\pi \times 2.5 \times 10^3}$$

$$= \frac{14}{\pi \times 2.5 \times 10} = \frac{14}{\pi(25)}$$

$$= 0.1782$$

② Design a low pass composite filter to operate with a desired impedance 500Ω , $m = 0.2$ & cut frequency = 2000 Hz

Step 1:- ~~do~~ L, C from characteristic impedance

Step 2:- Draw const k-type filter

Step 3:- Draw the modified ^{derived} filter with given value 0.2

Step 4:- Modifying filter to half sections with $m = 0.6$


Steps:

$$R_0 = 500 \Omega$$

$$m = 0.2$$


$$f_c = 2000 \text{ Hz}$$
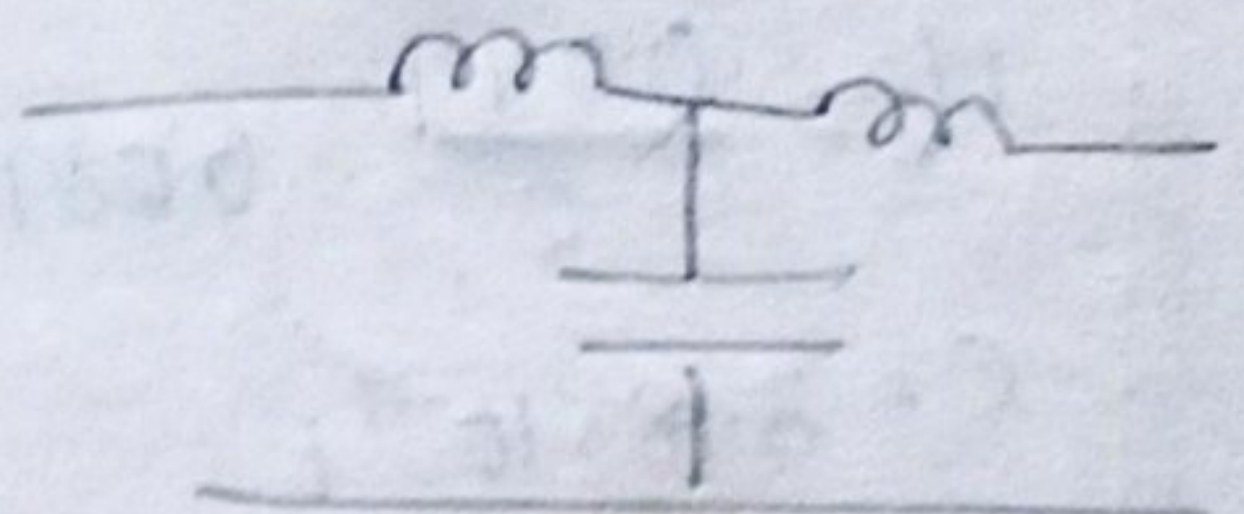
$$L = \frac{R_0}{\pi f_c} = \frac{500}{\pi \times 2000} = 0.0794$$



$$C = \frac{1}{R_0 \omega_c} = \frac{1}{500 \times 11 \times 2000} = 3.18 \times 10^{-7} \text{ F}$$

k type filter

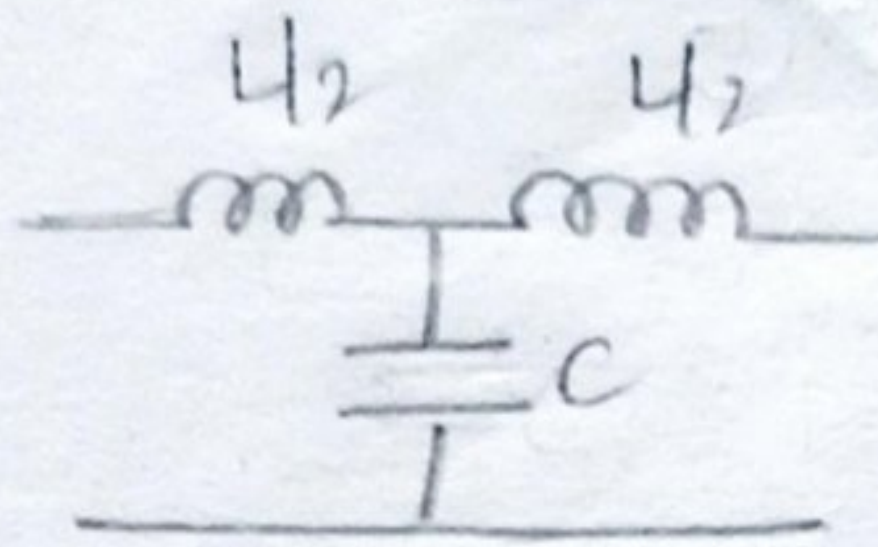

$$L/2 = \frac{0.079}{2} = 0.0395 \text{ H}$$

$$C = 3.18 \times 10^{-7} \text{ F}$$


M-derived filter

$$mL/2 = 0.2 \times 0.0395 \text{ H}$$

$$= 7.9 \text{ mH}$$

$$mC = 0.2 \times 3.18 \times 10^{-7}$$

$$= 6.36 \times 10^{-8} \text{ F}$$

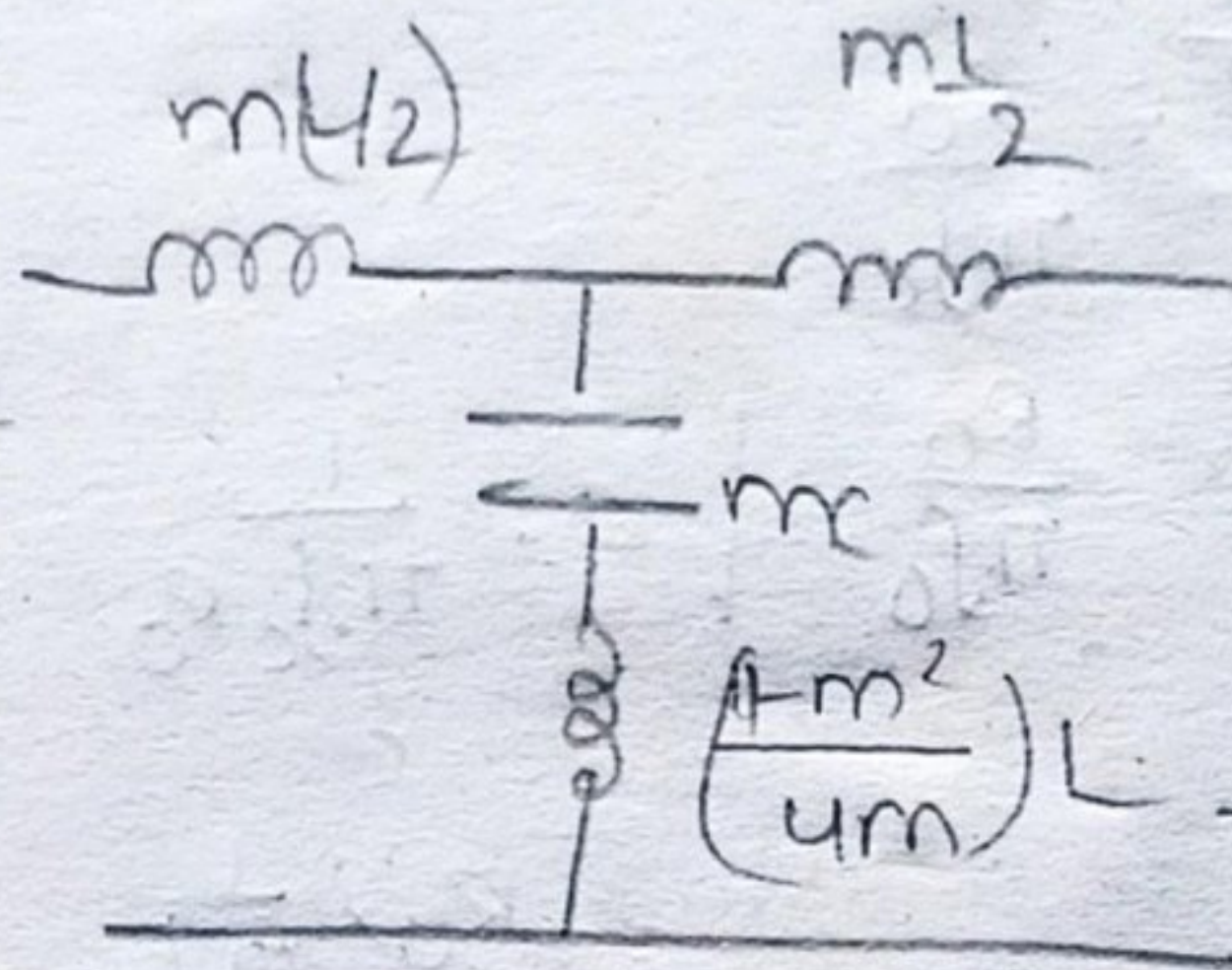


$$\left(\frac{1-m^2}{4m}\right) 2L = 0.095 \text{ H}$$


Half terminating section

$$mC/2 = 3.18 \times 10^{-8} \text{ F}$$


$$m = 0.6$$

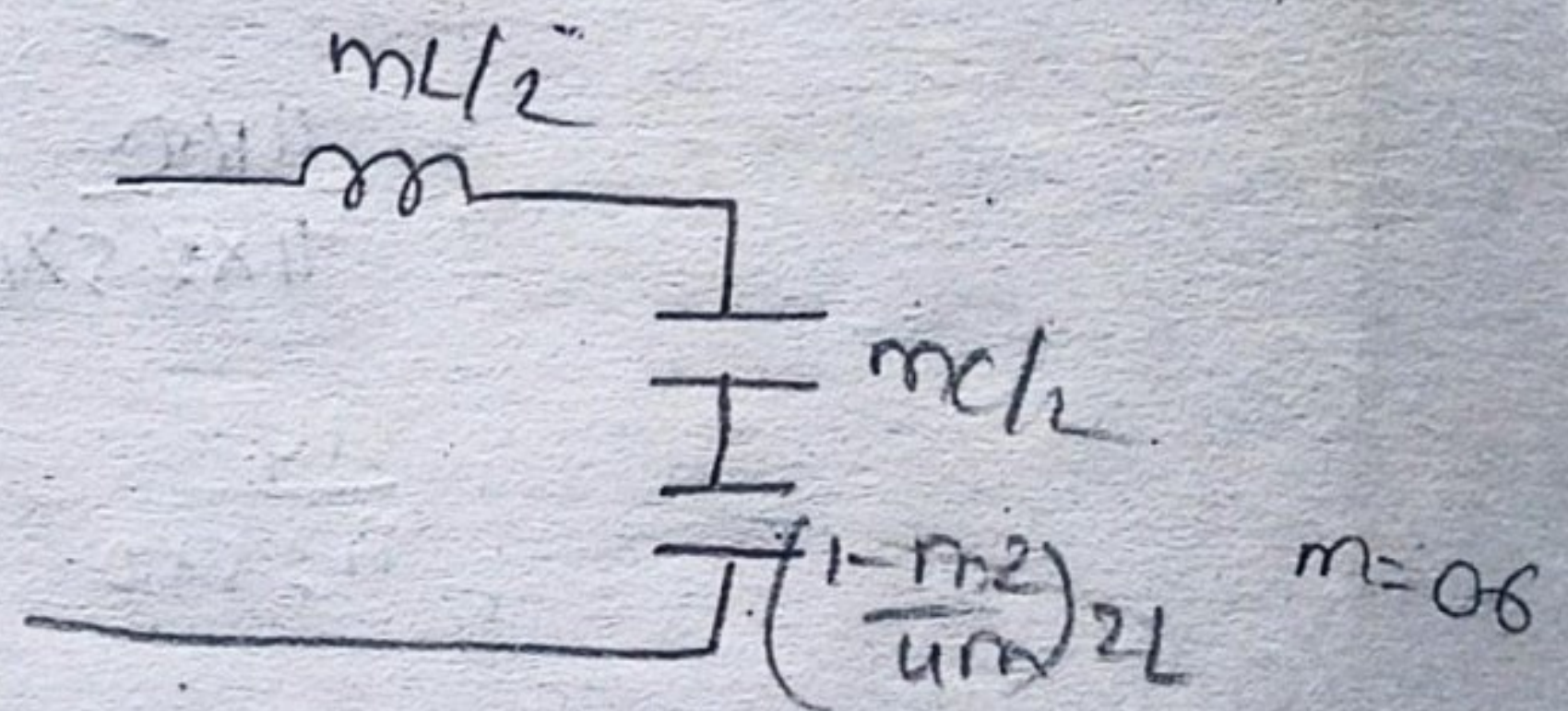

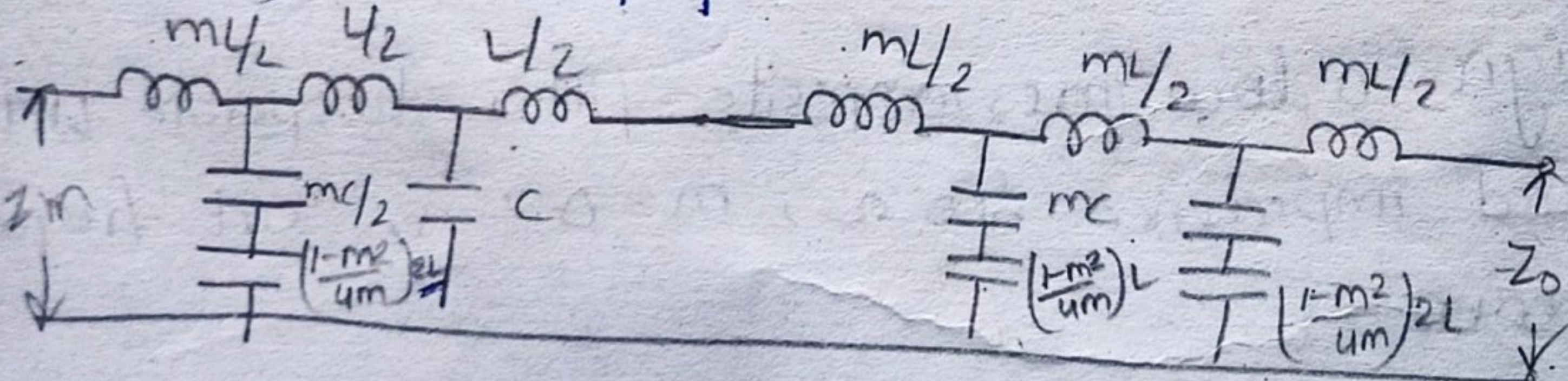
$$\left(\frac{1-m^2}{4m}\right) 2L = 0.0424$$



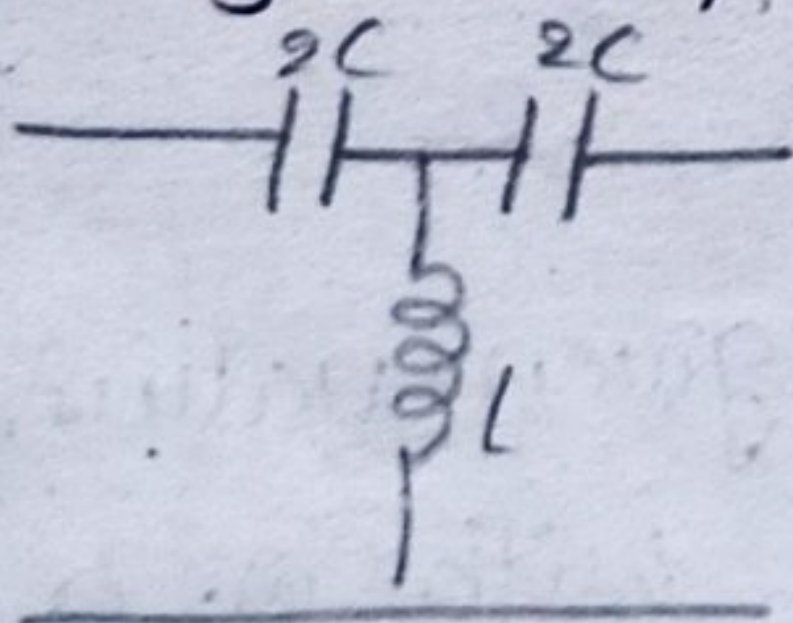
Design concept of high pass concept filter:-



const k filter

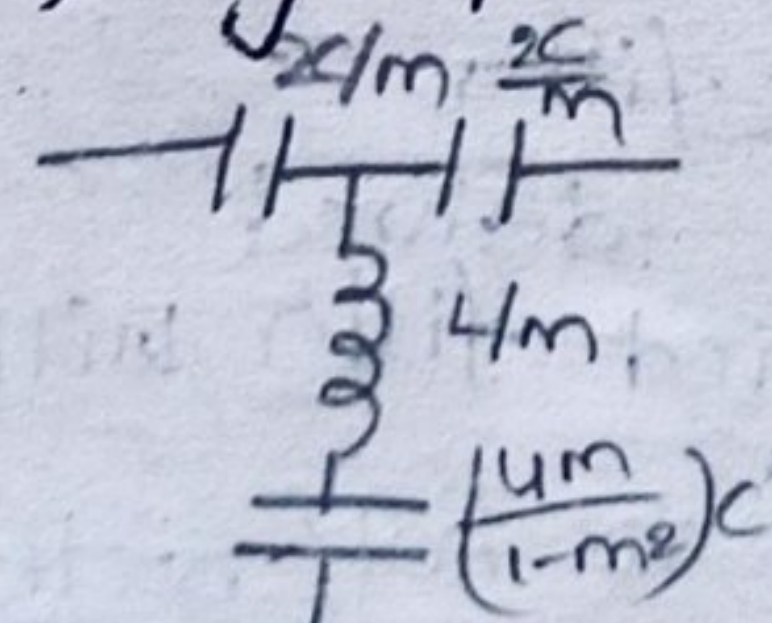

M-derived high pass

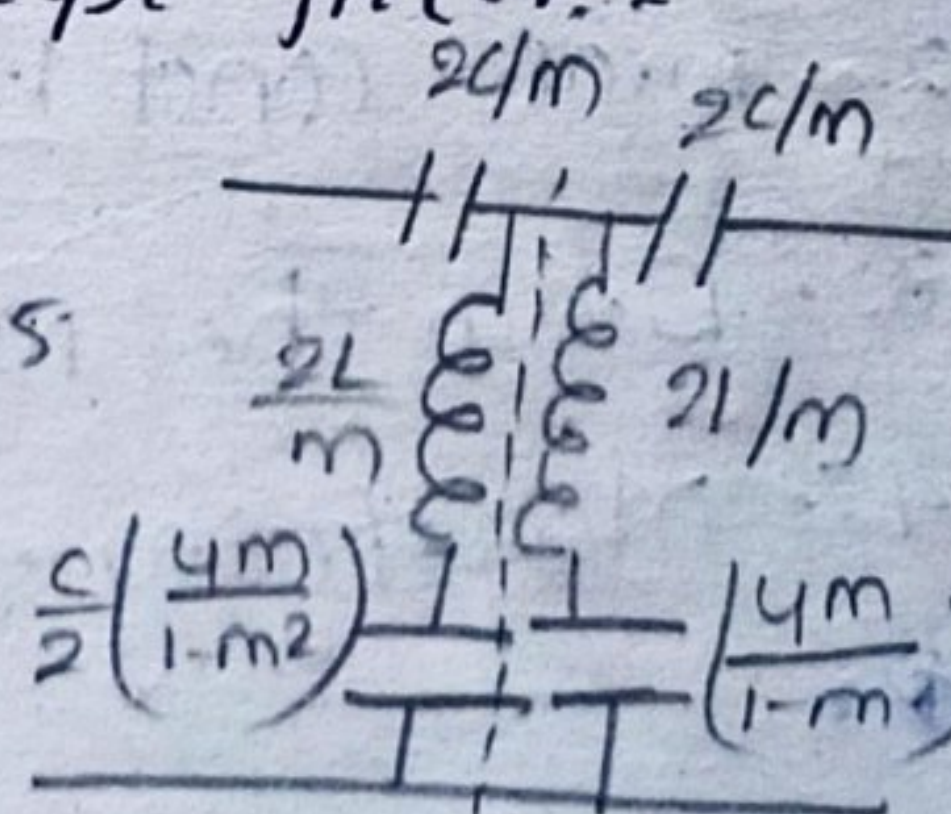

terminating half section

① M-derive section with $m=0.4$, terminating half section with $m=0.6$ design a complete high pass filter composite filter having the inductance of $L=40\text{mH}$, $C=0.1\text{ }\mu\text{F}$

$$Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)} \rightarrow (1)$$

$$Z_{OT}' = \sqrt{mZ_1 Z_2' \left(1 + \frac{mZ_1}{4Z_2'}\right)} \rightarrow (2)$$

$$\text{eq (1)} = \text{eq (2)}$$

$$Z_{OT} = Z_{OT}'$$

$$\sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)} = \sqrt{mZ_1 Z_2' \left(1 + \frac{mZ_1}{4Z_2'}\right)}$$

$$Z_2 \left(1 + \frac{Z_1}{4Z_2}\right) = mZ_2' \left(1 + \frac{mZ_1}{4Z_2'}\right)$$

$$Z_2 + \frac{Z_1}{4} = mZ_2' + \frac{m^2 Z_1}{4}$$


$$\frac{m^2 Z_1}{4} - \frac{Z_1}{4} = Z_2 - mZ_2'$$

$$\frac{Z_1}{4} (m^2 - 1) = Z_2 - mZ_2'$$



$$-Z_2 + mZ_2' = (1 - m^2) \frac{Z_1}{4}$$

$$mZ_2' = Z_2 + (1 - m^2) \frac{Z_1}{4}$$
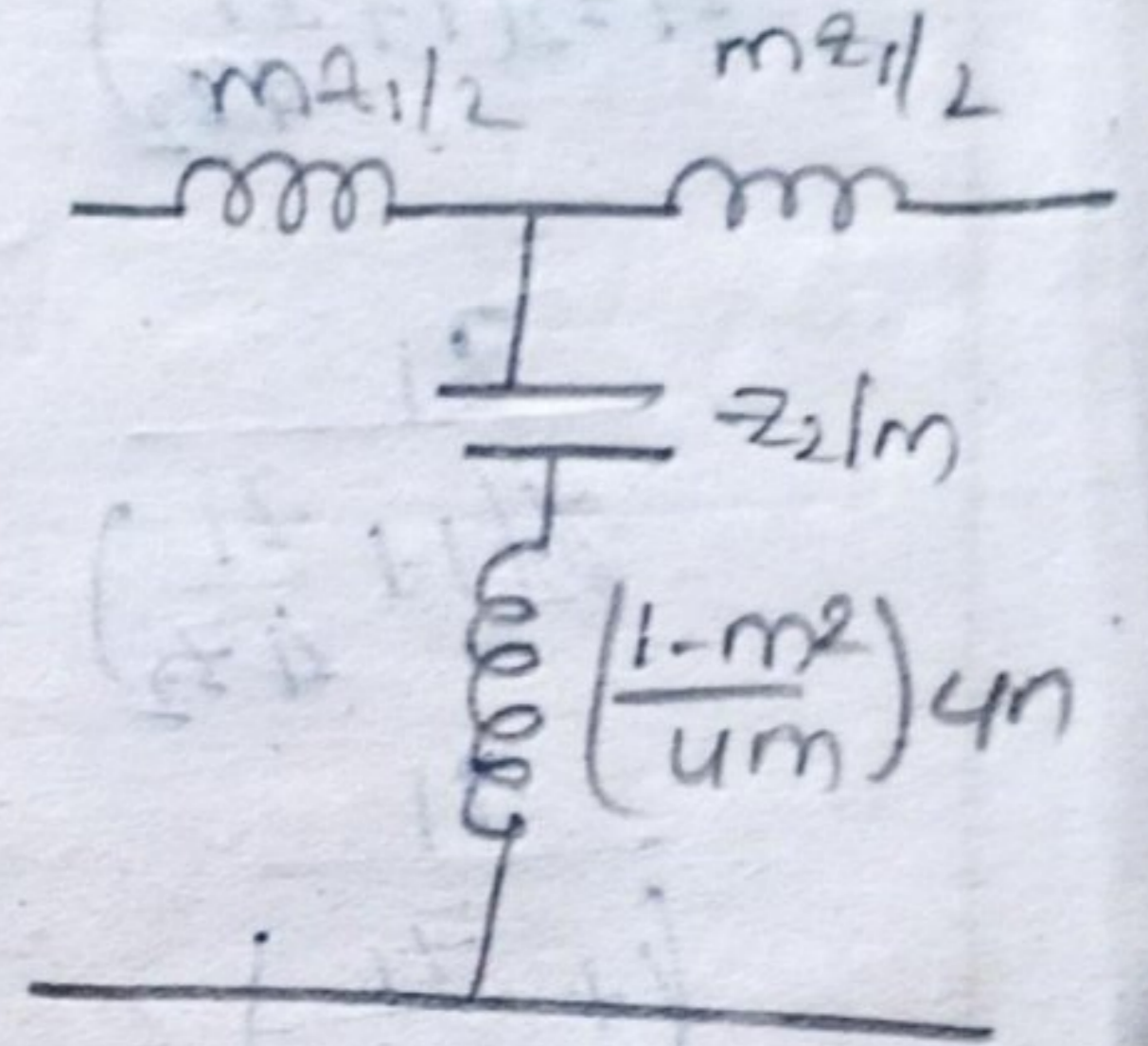
$$Z_2' = \frac{Z_2}{m} + \left(\frac{1 - m^2}{4m}\right) Z_1$$



For π Section:-

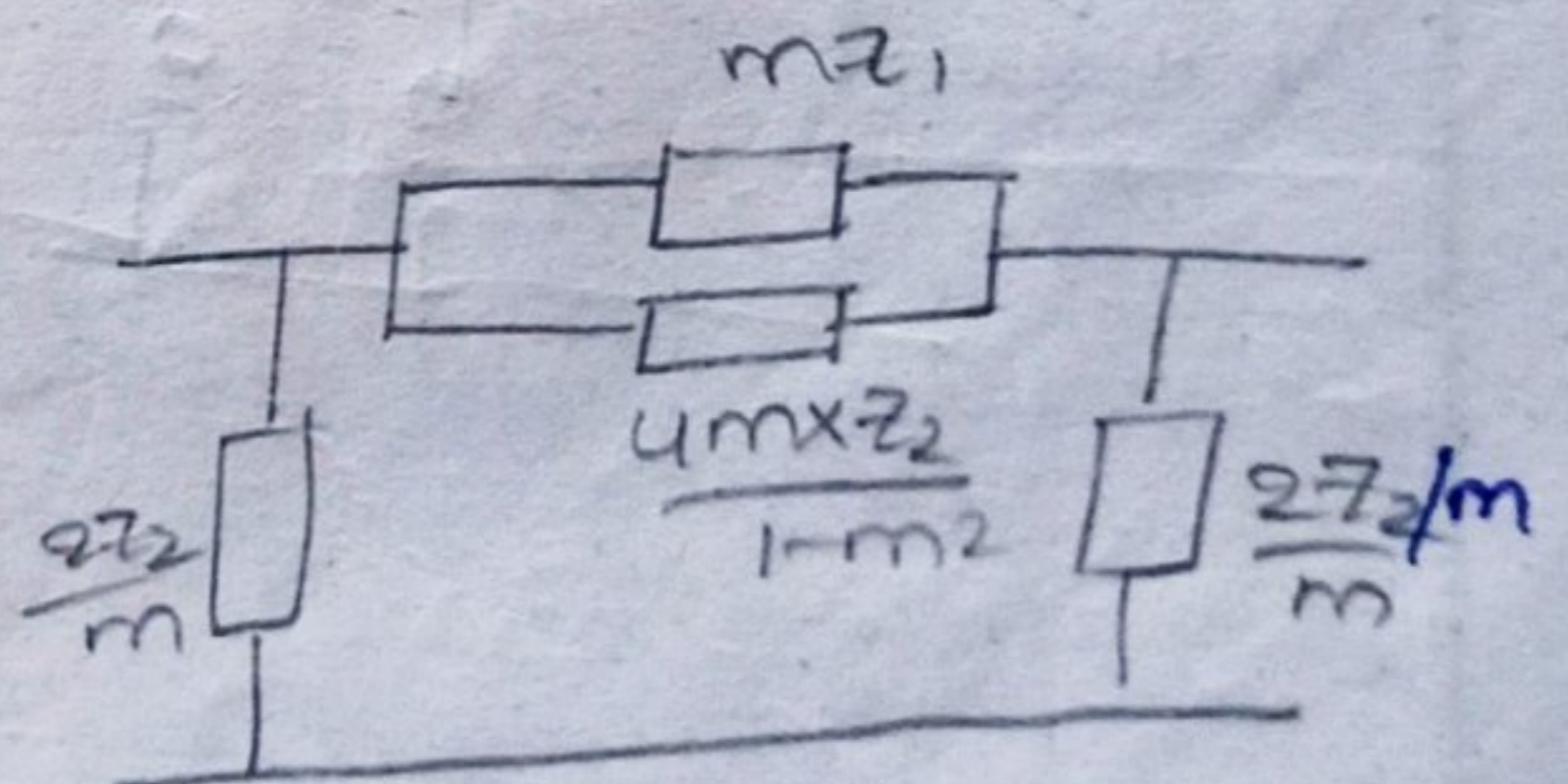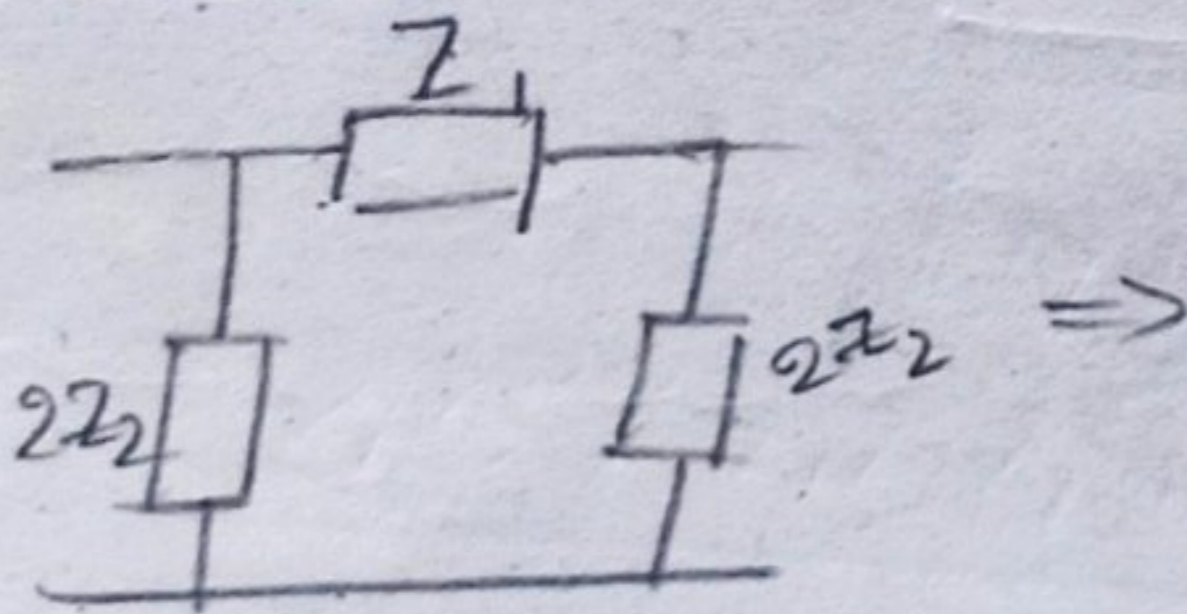

$$Z_{OT} = \frac{Z_1 Z_2}{\sqrt{Z_{OT}}} = \frac{Z_1 Z_2}{\sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}} \rightarrow (1)$$

$$Z_{OT}' = \frac{Z_1' Z_2' m}{Z_1' m Z_2' \left(1 + \frac{Z_1'}{4m Z_2'}\right)} \rightarrow (2)$$

$$\text{eq (1)} = \text{eq (2)}$$

$$\frac{z_1 z_2}{\sqrt{z_1 z_2 \left(1 + \frac{z_1}{4z_2}\right)}} = \frac{z_1' m z_2}{\sqrt{z_1' m z_2 \left(1 + \frac{z_1'}{4z_2 m}\right)}}$$

$$\frac{z_1^2}{z_1 z_2 \left(1 + \frac{z_1}{4z_2}\right)} = \frac{z_1'^2 m^2}{z_1' m z_2 \left(1 + \frac{z_1'}{4z_2 m}\right)}$$

$$\frac{z_1}{z_2 \left(1 + \frac{z_1}{4z_2}\right)} = \frac{m z_1'}{z_2 \left(1 + \frac{z_1'}{4z_2 m}\right)}$$

$$\frac{z_1}{\left(1 + \frac{z_1}{4z_2}\right)} = \frac{m z_1'}{\left(1 + \frac{z_1'}{4z_2 m}\right)}$$

$$z_1 \left(1 + \frac{z_1'}{4z_2 m}\right) = m z_1' \left(1 + \frac{z_1}{4z_2}\right)$$

$$\frac{z_1 (4z_2 m + z_1')}{4z_2 m} = \frac{m z_1' (4z_2 + z_1)}{4z_2}$$

